

## BJT Modeling and AC Equivalent Circuit

### Basic Concepts:

The key to the transistor small-signal analysis is the use of ac equivalent circuits or models. A model is the combination of circuit elements, properly chosen, that best approximates the actual behavior of a semiconductor device (BJT) under specific operating conditions. Once the ac equivalent circuit has been determined, the graphical symbol of the device can be replaced in the schematic by this circuit and the basic methods of ac circuit analysis (mesh analysis, nodal analysis, and Thevenin's theorem) can be applied to determine the response of the circuit. There are two schools of thought in prominence today regarding the equivalent circuit to be substituted for the transistor: **hybrid** and  **$r_e$  model**. In summary, the ac equivalent circuit of the BJT amplifier is obtained by (see Fig. 12-1):

1. Setting all dc sources to zero and replacing them by a short-circuit equivalent.
2. Replacing all capacitors by a short-circuit equivalent.
3. Removing all elements bypassed by the short-circuit equivalents introduced by stapes 1 and 2.
4. Redrawing the circuit in a more convenient and logical form.
5. Use the **hybrid** or  **$r_e$**  equivalent circuit of the BJT to complete the equivalent circuit of the amplifier.
6. Finally, the following parameters are determined for the amplifier:
  - a. Input impedance ( $Z_i$ ).
  - b. Output impedance ( $Z_o$ ).
  - c. Voltage gain ( $A_v$ ).
  - d. Current gain ( $A_i$ ).
  - e. Phase relationship ( $\theta$ ).

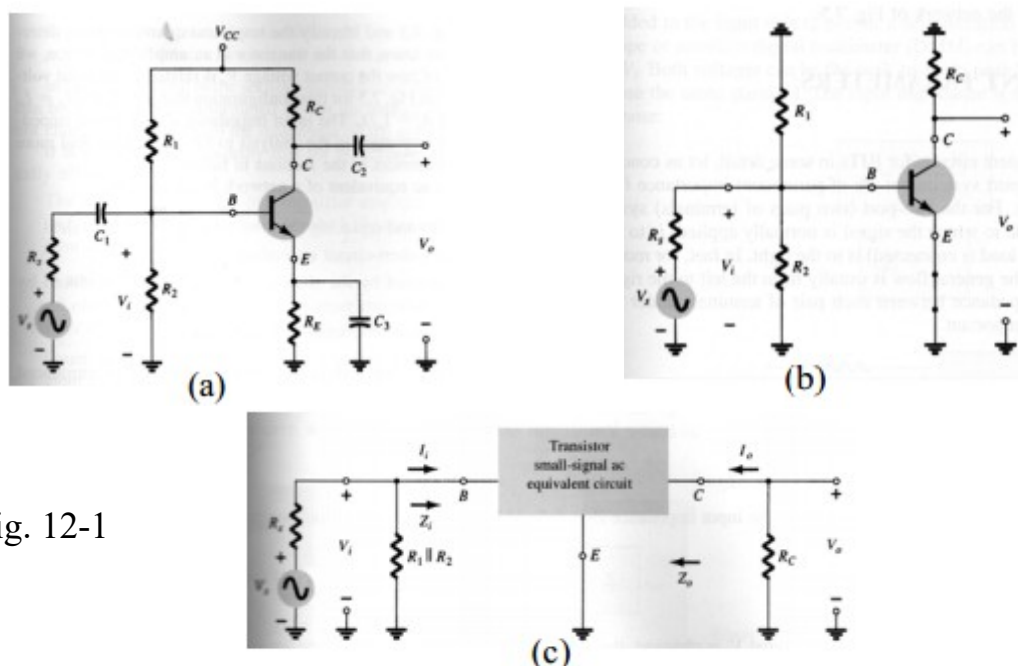


Fig. 12-1

**The Hybrid (h-parameters) Equivalent Model:**

For the general hybrid two-port system of Fig. 12-2:

$$V_i = h_{11} I_i + h_{12} V_o \quad [12.1a]$$

$$I_o = h_{21} I_i + h_{22} V_o \quad [12.1b]$$

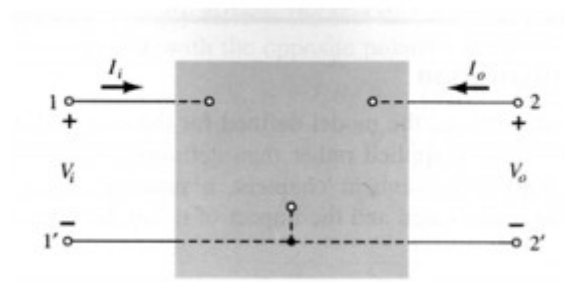


Fig. 12-2

where

$$h_{11} = \frac{V_i}{I_i} \Big|_{V_o=0} = h_i \text{ (}\Omega\text{)}, \text{ at } V_o = 0 \text{ short-circuit input impedance parameter.}$$

$$h_{12} = \frac{V_i}{V_o} \Big|_{I_i=0} = h_r \text{ (unitless)}, \text{ at } I_i = 0 \text{ open-circuit reverse transfer voltage ratio parameter.}$$

$$h_{21} = \frac{I_o}{I_i} \Big|_{V_o=0} = h_f \text{ (unitless)}, \text{ at } V_o = 0 \text{ short-circuit forward transfer current ratio parameter.}$$

$$h_{22} = \frac{I_o}{V_o} \Big|_{I_i=0} = h_o \text{ (S)}, \text{ at } I_i = 0 \text{ open-circuit output admittance parameter.}$$

From the BJT hybrid equivalent circuit of Fig. 12-3, Eqs. [12.1a] and [12.1b] becomes:

$$V_i = h_i I_i + h_r V_o \quad [12.2a]$$

$$I_o = h_f I_i + h_o V_o \quad [12.1b]$$

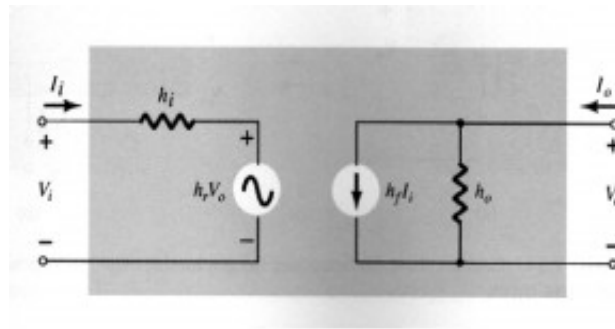


Fig. 12-3

**Gain and Impedance Computation of the Complete Hybrid Equivalent Circuit:**

For the circuit of Fig. 12-4,

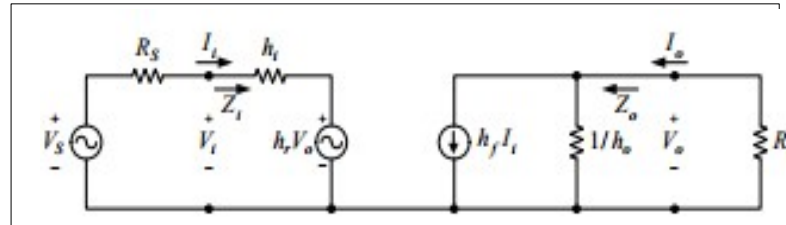


Fig. 12-4

the voltage gain  $\frac{A}{V}$

$$I_i = \frac{V_i - h_r V_o}{h_i}, I_o = \frac{-V_o}{R_L}, I_o = h_f I_i - h_o V_o \Rightarrow$$

$$A_V = \frac{V_o}{V_i} = \frac{-h_f R_L}{h_i + h_i h_o - h_f h_r + h_o R_L} \quad [12.3a]$$

the current gain  $\frac{A}{I}$

$$I_o = h_f I_i - h_o V_o, V_o = -I_o R_L \Rightarrow I_o = h_f I_i + h_o R_L I_o$$

$$A_I = \frac{I_o}{I_i} = \frac{h_f}{1 - h_o R_L} \quad [12.3b]$$

the input impedance  $Z$

$$\frac{V_i}{I_i} = h_i + h_r \frac{V_o}{I_i}, V_o = -I_o R_L \Rightarrow \frac{V_i}{I_i} = h_i - h_r R_L \frac{I_o}{I_i} = h_i - h_r R_L A_I$$

$$Z_i = \frac{V_i}{I_i} = h_i - \frac{h_f h_r R_L}{1 + h_o R_L} \quad [12.3c]$$

the output impedance  $Z_o = \frac{V_o}{I_o}$ ;

$$V_s = I_i R_s + h_i V_o \Rightarrow I_i = \frac{-h_r V_o}{R_s + h_i}, \quad I_o = h_f I_i + h_o V_o$$

$$I_o = h_o V_o - \frac{h_f h_r}{R_s + h_i} V_o \Rightarrow$$

$$Z_o = \frac{V_o}{I_o} = \frac{1}{h_o - \frac{h_f h_r}{R_s + h_i}} \quad [12.3d]$$

## Types of Hybrid Parameters:

Since there are three types of BJT configuration (CE, CC, and CB), there are three different ways that the input and output can be defined and therefore three corresponding sets of  $h$ -parameters as shown in Table 12-1. If all of the  $h$ -parameters values in one configuration are known, then the values corresponding to any other configuration can be determined. The common-emitter values of the  $h$ -parameters are the ones most often given.

Table 12-1

BJT configuration		h-parameters sets
1-	Common-Emitter	$h_{ie}, h_{fe}, h_{re}, h_{oe}$
2-	Common-Collector	$h_{ic}, h_{fc}, h_{rc}, h_{oc}$
3-	Common-Base	$h_{ib}, h_{fb}, h_{rb}, h_{ob}$

The hybrid equivalent circuits of the CE and CB transistor configuration are shown in Fig. 12-5 (a) and (b) respectively.

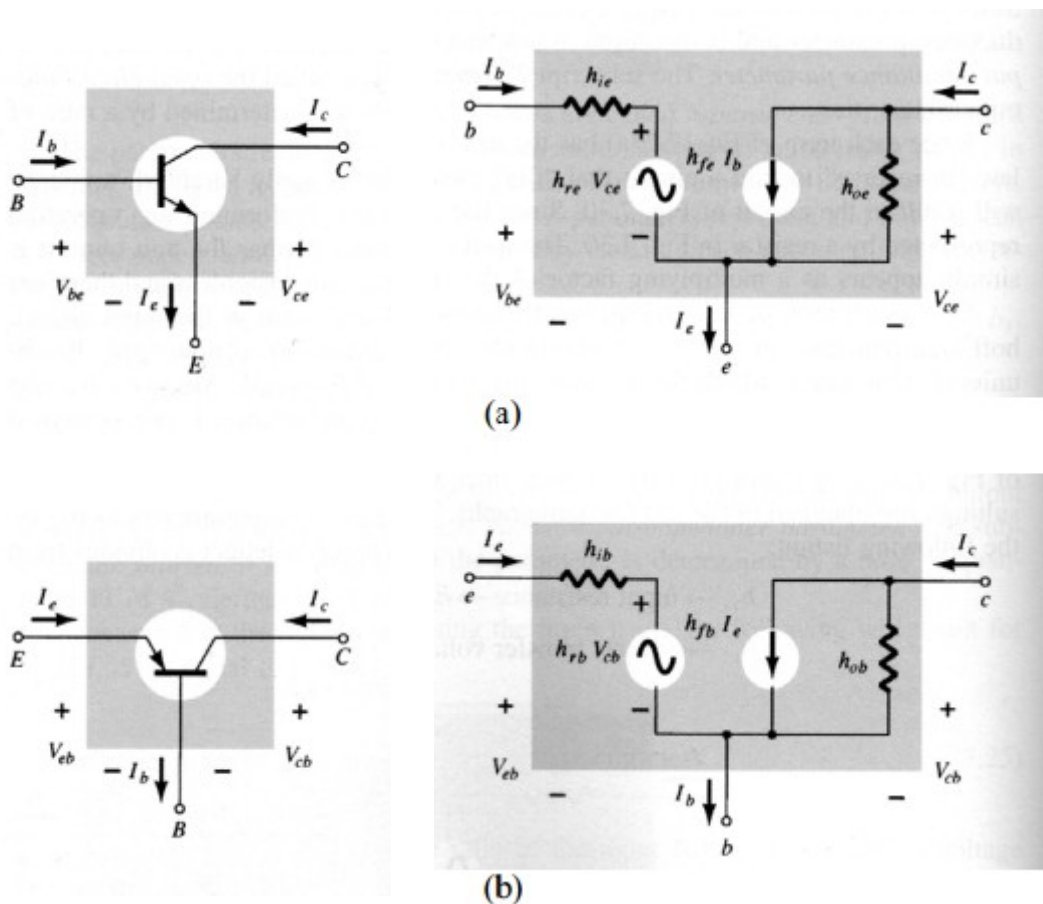


Fig. 12-5


Table 12-2 lists typical parameter values in each of the three transistor configurations (CE, CC, and CB) for the broad range of transistors available today.

Table 12-2


h-parameters	CE	CC	CB
$h_i$	1kΩ	1kΩ	20kΩ
$h_r$		≈ 1	
$h_f$	50	-50	-0.98
$h_o$	25 μS	25 μS	0.5 μS
1/ $h_o$	40 kΩ	40 kΩ	2 MΩ

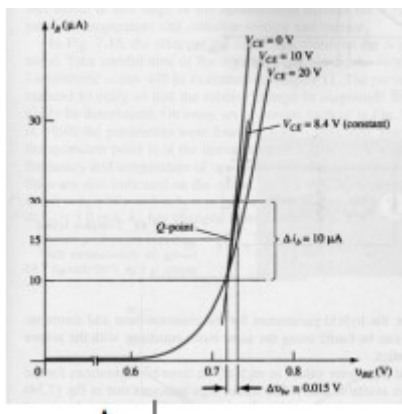**Graphical Determination of the CE Hybrid Parameters:**


The parameters  $h_{ie}$  and  $h_{re}$  are determined from the input or base characteristics, while the parameters  $h_{fe}$  and  $h_{oe}$  are obtained from the output or collector characteristics as shown in Fig. 12-6.



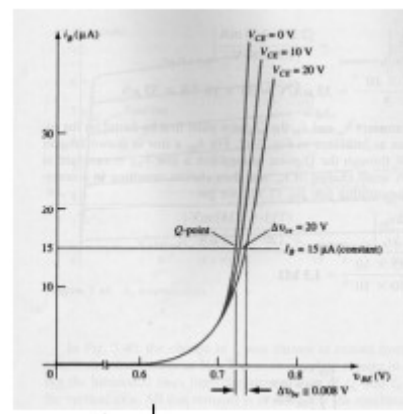
$$h_{ie} = \frac{\Delta V_{be}}{\Delta i_b} = 1.5 \text{ k}\Omega \text{ at } V_{CE} = \text{const.}$$


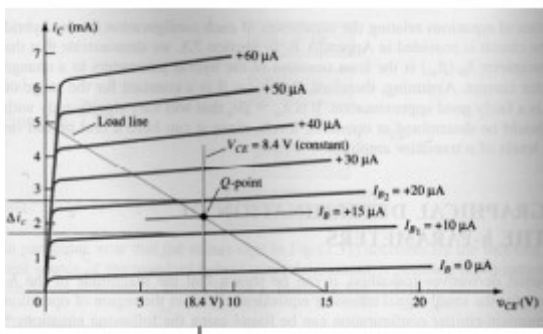
$$h_{re} = \frac{\Delta V_{be}}{\Delta v_{ce}} = 4 \times 10^{-4} \text{ at } I_B = \text{const.}$$


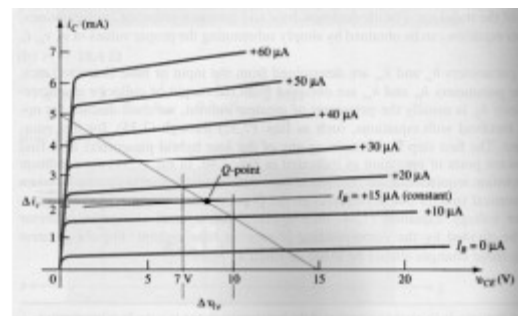
$$h_{fe} = \frac{\Delta i_c}{\Delta i_b} = 100 \text{ at } V_{CE} = \text{const}$$



$$h_{oe} = \frac{\Delta i_c}{\Delta v_{ce}} = 33 \mu\text{S} \text{ at } I_B = \text{const.}$$

Fig. 12-5

For the transistor whose characteristics have appeared in Fig. 12-6, the resulting hybrid small-signal equivalent circuit is shown in Fig. 12-7.

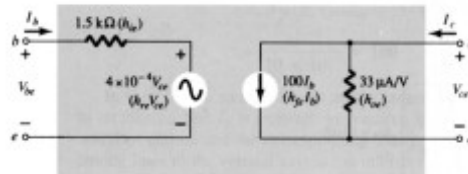


Fig. 12-7

The typical values of  $h$ -parameters for CE transistor configuration are shown in Table 12-3.

Table 12-3

$h_{xe}$ parameters		Min.	Max	Unit
Input impedance	$h_{ie}$	0.5	7.5	$k\Omega$
Voltage feedback ratio	$h_{re}$	0.1	8.0	$\times 10^{-4}$
Small-signal current gain	$h_{fe}$	20	250	-
Output admittance	$h_{oe}$	1.0	30	$\mu S$

**Approximate CE Hybrid Equivalent Model:**

Since  $h_{re}$  is normally a relatively small quantity, its removal is approximated by  $h_{re} \approx 0$  and  $h_{re}V_{ce} = 0$ , resulting in a short-circuit equivalent for the feedback element. The resistance determined by  $1/h_{oe}$  is often large enough to be ignored in comparison to a parallel load permitting its replacement by an open-circuit equivalent for the CE model as shown in Fig. 12-8.

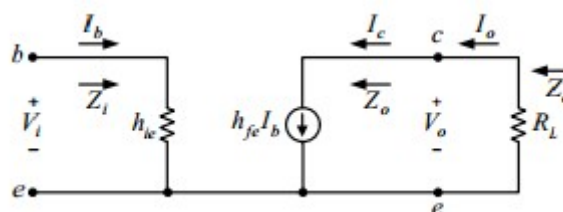


Fig. 12-8

For the circuit of Fig. 12-8

$$Z_i \approx h_{ie}, \quad Z_o \approx \infty.$$



$$A_i \approx \frac{I_c}{I_b} h_{fe} A_v \approx \frac{V_o}{V_i} \approx \frac{-I_o R_L}{I_b h_{ie}} \approx \frac{-I_c R_L}{I_b h_{ie}} - h_{fe} \frac{R_L}{h_{ie}} - A_i \frac{Z_o}{Z_i}$$

### The $r_e$ Equivalent Model:

#### CB Transistor Configuration:

From Fig. 12-9, the input impedance at the emitter of CB transistor configuration (dynamic resistance of the forward diode) can be determined by:

$$r_e \approx \frac{26mV}{I_E} \quad [12.4]$$

the output impedance at the collector (dynamic resistance of the reverse diode) is:

$$r_o \approx \infty$$

Also;

$$Z_i \approx r_e \parallel Z_o \approx \infty$$

$$V_o \approx -I_o R_L \approx -I_c R_L \approx \alpha I_e Z_i, \quad V_i \approx I_e Z_i \approx I_e r_e \Rightarrow$$

$$A_v \approx \frac{V_o}{V_i} \approx \frac{\alpha R_L}{r_e} \approx \frac{R_L}{r_e}$$

$$I_c \approx \alpha I_e, \quad A_i \approx \frac{I_c}{I_i} \approx -A_v \frac{I_c}{I_e} \Rightarrow$$

$$A_i \approx -\alpha \approx -1$$

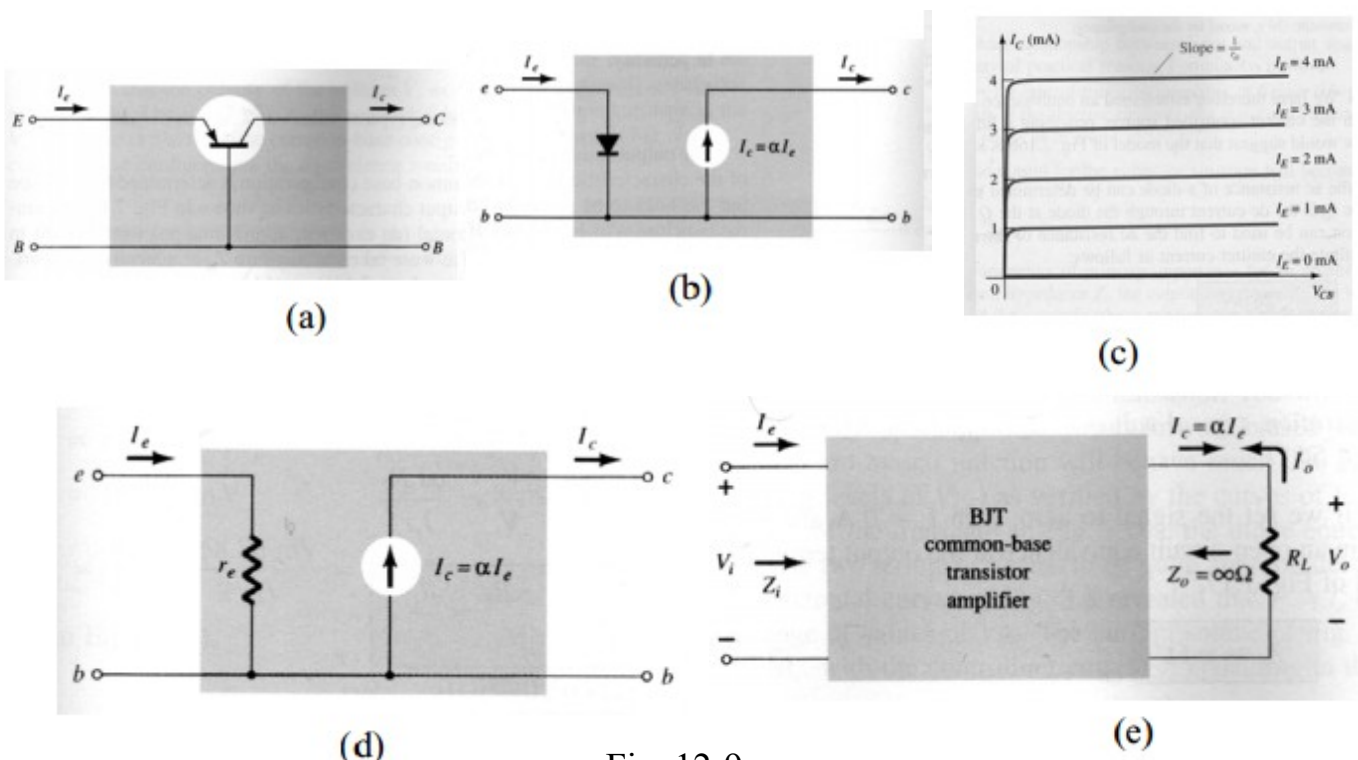


Fig. 12-9

### CE Transistor Configuration:

From Fig. 12-10;

$$I_c \approx \beta I_b, I_e \approx I_c \approx I_b \approx \beta I_b \approx I_b \beta \approx 1 \Rightarrow I_b \approx \beta I_b, \oplus$$

$$V_{be} \approx I_e r_e \approx \beta I_b r_e$$

$$Z_i \approx \frac{V_i}{I_i} \approx \frac{V_{be}}{I_b} \approx \beta \cdot r_e$$

$$Z_o \approx r_o \approx \infty$$

$$V_o \approx -I_o R_L \approx -I_c R_L \approx -\beta I_b R_L$$

$$A_v \approx \frac{V_o}{V_i} \approx \frac{V_o}{V_{be}} \approx \frac{-\beta I_b R_L}{\beta I_b r_e} \approx \frac{-R_L}{r_e}$$

$$A_i \approx \frac{I_o}{I_b} \approx \frac{I_c}{I_b} \approx \beta \approx \beta$$


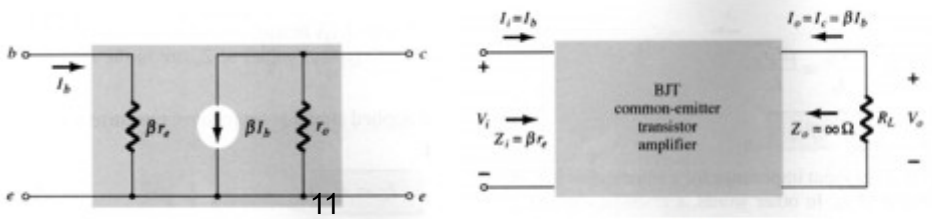
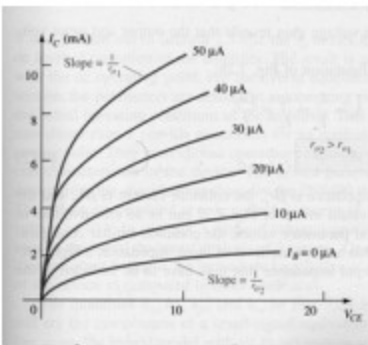
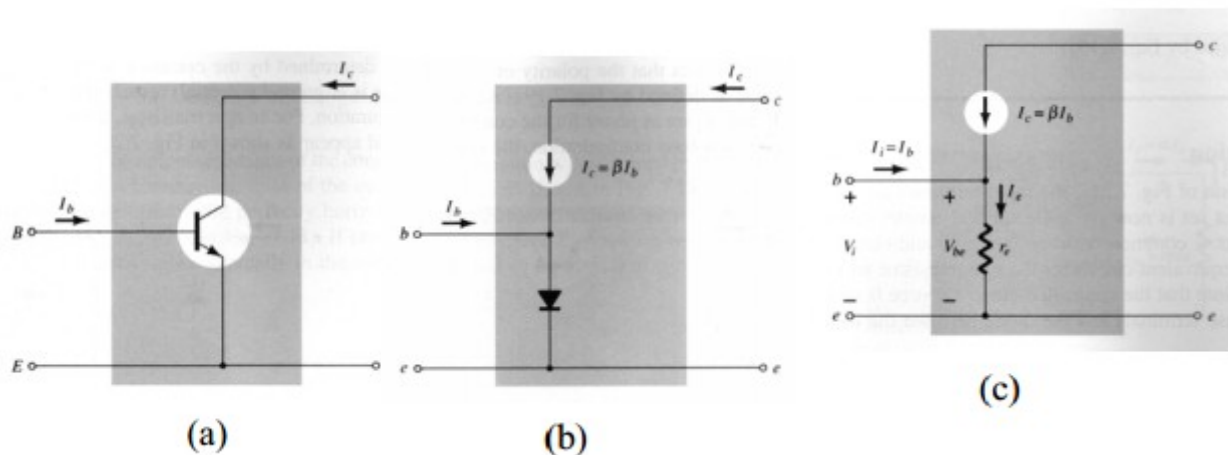


Fig. 12-10

**Variations of Transistor Parameter:**

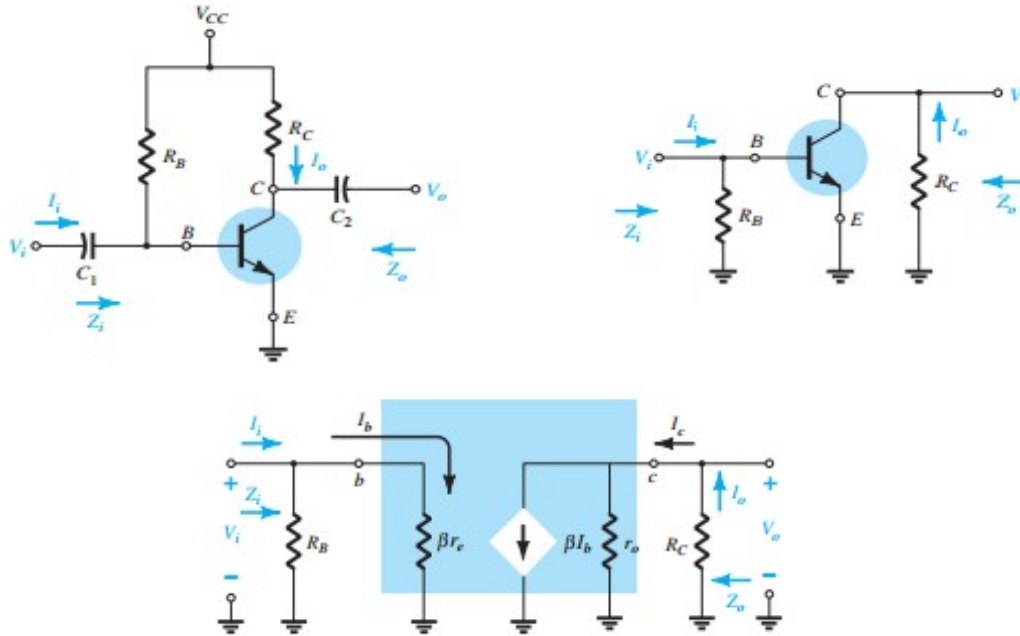**1- Common-Emitter Fixed-bias Configuration:**



- 1)  $Z_i \approx R_B \parallel \beta r_e \Omega$  if  $R_B \ll \beta r_e$  then  $Z_i \approx \beta r_e$
- 2)  $V_i \approx 0, I_b \approx 0, \beta I_b \approx 0$  open CCT. ✱

$Z_o \approx R_C \parallel r_o \Omega$  if  $r_o \geq 10 R_C$  then  $R_C \parallel r_o \approx R_C \approx Z_o \approx R_C$


3)  $A_v \dots \dots V_o \approx -\beta I_b (R_C \parallel r_o)$

$I_b \approx \frac{V_i}{\beta r_e} \approx V_o \approx -\beta \frac{V_i}{\beta r_e} (R_C \parallel r_o)$

$A_v \approx \frac{V_o}{V_i} \approx \frac{-R_C \parallel r_o}{r_e}$  if  $r_o \geq 10 R_C \approx A_v \approx \frac{-R_C}{r_e}$

**Example:** For the network Determine

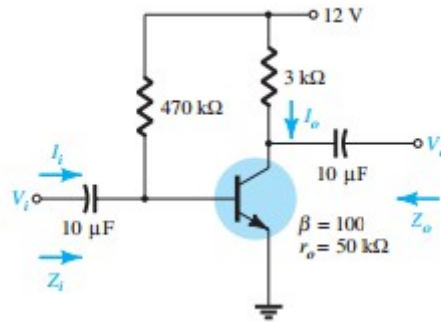- a.  $r_e$
- b.  $Z_i$  (with  $r_o \approx \infty \Omega$ ).
- c.  $Z_o$  (with  $r_o \approx \infty \Omega$ ).
- d.  $A_v$  (with  $r_o \approx \infty \Omega$ ).
- e. Repeat parts (c) and (d) including  $r_o \approx 50 \text{ k} \Omega$



**Solution:**

a. DC analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.7}{470k} = 24.04 \mu A.$$

$$I_E = (\beta + 1) I_B = 101 \times 24.04 \mu = 2.428 mA.$$

$$r_e = \frac{26 mV}{I_E} = \frac{26 mV}{2.428 m} = 10.71 \Omega$$

b.  $\beta r_e = 100 \times 10.71 = 1.071 K \Omega.$

$$Z_i = R_B \parallel \beta r_e = 470 \parallel 1.071 K = 1.07 k \Omega.$$



c.  $Z_o = R_C = 3 k \Omega.$

d.  $A_v = \frac{-R_C}{r_e} = \frac{-3k}{10.71 \Omega} = -280.11$

e.  $Z_o = R_C \parallel r_o = 3k \parallel 50k = 2.83 k \Omega.$

$$A_v = \frac{-R_C \parallel r_o}{r_e} = \frac{-2.83k}{10.71} = -264.24$$

## 2-Voltage-Divader Bias

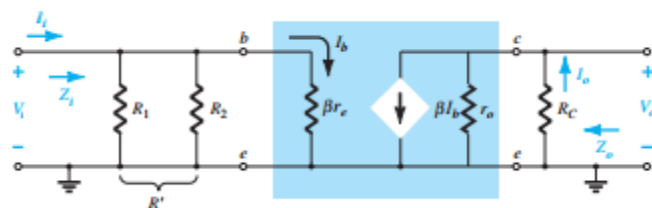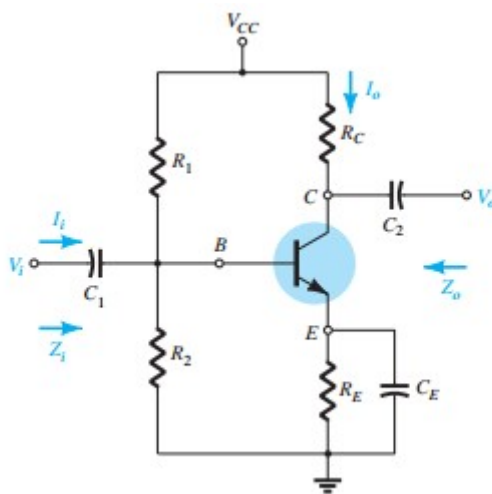

$$1) \quad Z_i \approx R \parallel \beta r_e \text{ where } R \approx R_1 \parallel R_2 \approx \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$2) \quad V_i \approx 0, I_b \approx 0, \beta I_b \approx 0 \text{ open CCT.}$$

$$Z_o \approx R_C \parallel r_o \text{ if } r_o \geq 10 R_C \text{ then } R_C \parallel r_o \approx R_C \Rightarrow Z_o \approx R_C$$


$$3) \quad A_v \dots \dots V_o \approx -\beta I_b (R_C \parallel r_o)$$

$$I_b \approx \frac{V_i}{\beta r_e} \Rightarrow V_o \approx -\beta \frac{V_i}{\beta r_e} (R_C \parallel r_o)$$

$$A_v \approx \frac{V_o}{V_i} \approx \frac{-R_C \parallel r_o}{r_e} \text{ if } r_o \geq 10 R_C \Rightarrow A_v \approx \frac{-R_C}{r_e}$$

**Example:** For the network Determine

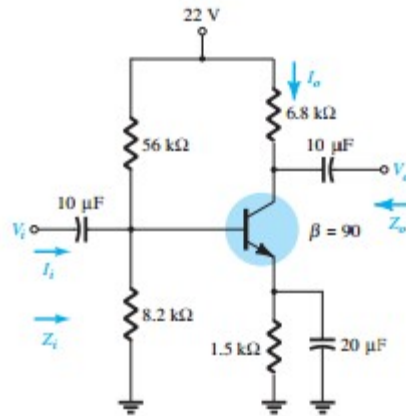- a.  $r_e$     b.  $Z_i$  (with  $r_o \rightarrow \infty \Omega$ ).    c.  $Z_o$  (with  $r_o \rightarrow \infty \Omega$ ).    d.  $A_v$  (with  $r_o \rightarrow \infty \Omega$ ).
- e. Repeat parts (c) and (d) including  $r_o = 50 \text{ k}\Omega$



**Solution:**

a. DC : Testing  $\beta R_E \gg 10 R_2$

$$90 \gg 1.5 \text{ k} \gg 10 \times 8.2 \text{ k}$$

$$135 \gg 82 \text{ k}$$

Using the approximate approach, we obtain

$$\text{a) } V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{8.2 \text{ k}}{56 \text{ k} + 8.2 \text{ k}} \times 22 \text{ V} = 2.81 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.81 - 0.7 = 2.11 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{2.11 \text{ V}}{1.5 \text{ k}} = 1.41 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.41 \text{ mA}} = 18.44 \Omega$$

$$\text{b) } R_{th} = R_1 \parallel R_2 = 56 \text{ k} \parallel 8.2 \text{ k} = 7.15 \text{ k}\Omega$$

$$Z_i = R_{th} \parallel \beta r_e = 7.15 \text{ k} \parallel 90 \times 18.44 \Omega = 1.35 \text{ k}\Omega$$

c)  $Z_o \approx R_C \approx 6.8 k \Omega$ .



d)  $A_v \approx \frac{-R_C}{r_e} \approx \frac{-6.8 k}{18.44 \Omega} \approx -368.76$

e)  $Z_o \approx R_C \parallel r_o \approx 6.8 k \parallel 50 k \approx 5.98 k \Omega$ .

f)  $A_v \approx \frac{-R_C \parallel r_o}{r_e} \approx \frac{-5.98 k}{18.44} \approx -324.3$

There was a measurable difference in the results for  $Z_o$  and  $A_v$ , because the condition  $r_o \geq 10R_C$  was not satisfied.

### 3-CE-Emitter bias configuration

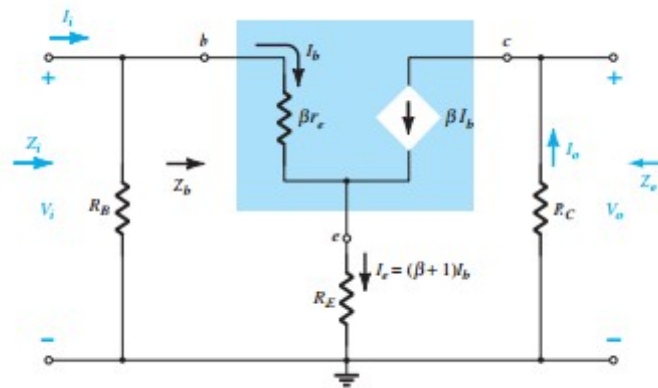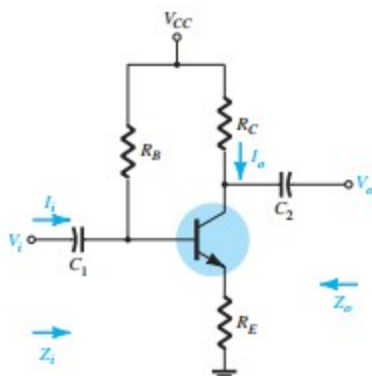

1)  $V_i \approx I_b \beta r_e \approx I_e R_E$

$V_i \approx I_b \beta r_e \approx (\beta + 1) I_b R_E$

$Z_b \approx \frac{V_i}{I_b} \approx \beta r_e \approx (\beta + 1) R_E$  then  $Z_b \approx \beta r_e \approx (\beta + 1) R_E$

$r_e \approx \frac{V_T}{I_E} \approx \frac{26 mV}{I_E}$   
 since  $\beta \gg 1$ ,  $Z_b \approx \beta r_e$

$r_e \approx \frac{V_T}{I_E} \approx \frac{26 mV}{I_E}$ , since  $R_E \gg r_e$  then  $Z_b \approx \beta R_E$   
 $Z_b \approx \beta R_E$

$Z_i \approx R_B \parallel Z_b$



2)  $V_i \neq 0, I_b \neq 0, \beta I_b \neq 0$  open CCT.

$$Z_o \neq R_C$$

3)  $I_b \neq \frac{V_i}{Z_b}, V_o \neq -I_o R_C \neq -\beta I_b R_C \neq -\beta \frac{V_i}{Z_b} R_C$

$$A_v \neq \frac{V_o}{V_i} \neq \frac{-\beta R_C}{Z_b}$$

**Effect of  $r_o$**

$$Z_i : Z_b \neq \beta r_e \neq \frac{\beta (1) R_C \parallel r_o}{1 \neq R_C \neq R_E \neq r_o} R_E$$

Since the ratio  $\frac{R_C}{r_o} \neq \beta \neq 1$

$$Z_b \neq \beta r_e \neq r_o \neq \frac{\beta (1) R_E}{1 \neq R_C \neq R_E \neq r_o}$$

For  $r_o \geq 10 R_C \neq R_E$

$$Z_b \neq \beta r_e \neq \beta (1) R_E$$

$$Z_o : Z_o \neq R_C \parallel r_o \neq \frac{\beta r_o \neq r_e}{1 \neq \beta r_e \neq R_E}$$

However  $r_o \gg r_e$

$$Z_o \neq R_C \parallel r_o \neq \frac{\beta}{1 \neq \beta r_e \neq R_E}$$

which can be written as

$$Z_o \neq R_C \parallel r_o \neq \frac{1}{\frac{1}{\beta} \neq \frac{r_e}{R_E}}$$

$$\oplus Z_o \cong R_C$$

$$A_v : A_v = \frac{V_o}{V_i} = \frac{\frac{-\beta R_C}{Z_b} \cdot \frac{r_e}{r_o} \cdot \frac{R_C}{r_o}}{1 + \frac{R_C}{r_o}}$$

The ratio  $\frac{r_e}{r_o} \ll 1$


$$A_v = \frac{V_o}{V_i} = \frac{\frac{-\beta R_C}{Z_b} \cdot \frac{R_C}{r_o}}{1 + \frac{R_C}{r_o}}$$

For  $r_o \geq 10 R_C$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta R_C}{Z_b}$$

**Example:** For the network Determine

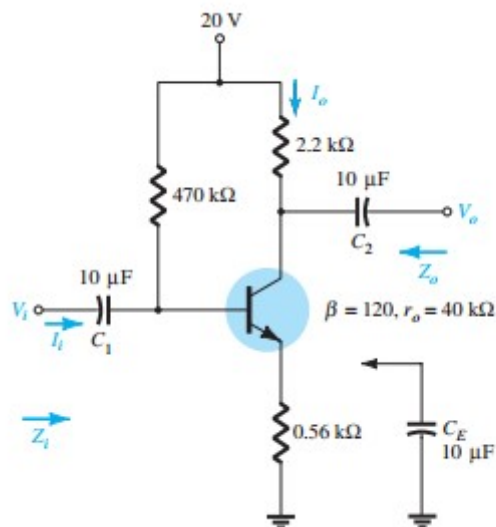- a.  $r_e$    b.  $Z_i$    c.  $Z_o$    d.  $A_v$



**Solution:**

- a. DC:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_E} = \frac{20 - 0.7}{470 \text{ k} + 121 \cdot 0.56 \text{ k}} = 35.89 \mu\text{A}$$

$$I_E = \beta I_B = 121 \cdot 35.89 \mu\text{A} = 4.34 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{4.34 \text{ mA}} = 5.99 \Omega$$

b. Testing the condition  $r_o \geq 10 R_C$

$$40 \text{ k} \geq 2.2 \text{ k} + 0.56 \text{ k} \Rightarrow 40 \text{ k} \geq 27.6 \text{ k} \text{ Satisfied}$$

Therefore,

$$Z_b = \beta (r_e + R_E) = 121 (5.99 \Omega + 560 \Omega) = 67.92 \text{ k} \Omega$$

$$Z_i = R_B \parallel Z_b = 470 \text{ k} \parallel 67.92 \text{ k} = 59.34 \text{ k} \Omega$$

c.  $Z_o = R_C = 2.2 \text{ k} \Omega$


d.  $r_o \geq 10 R_C$  is satisfied

$$A_v = \frac{V_o}{V_i} = \frac{-\beta R_C}{Z_b} = \frac{-120 \cdot 2.2 \text{ k}}{67.92 \text{ k}} = -3.89$$


compared to 3.93 using Eq.  $A_v = R_C / R_E$

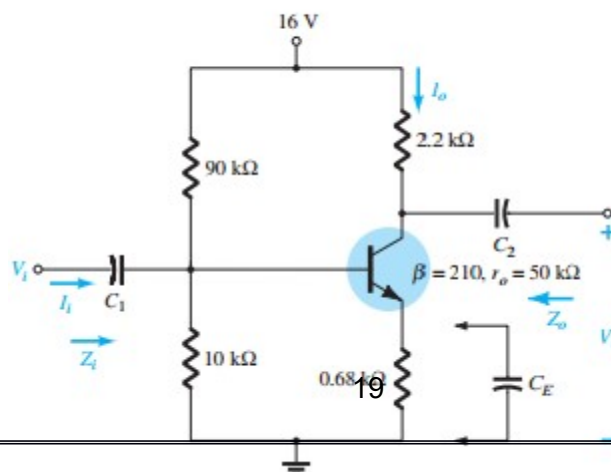**Home Work :**

- 1- Repeat the analysis of last Example with CE in place.
- 2- For the network determine a.  $r_e$ . b.  $Z_i$ . c.  $Z_o$ . d.  $A_v$  and repeat with CE in place



#### 4-Emitter-Follower Configuration:

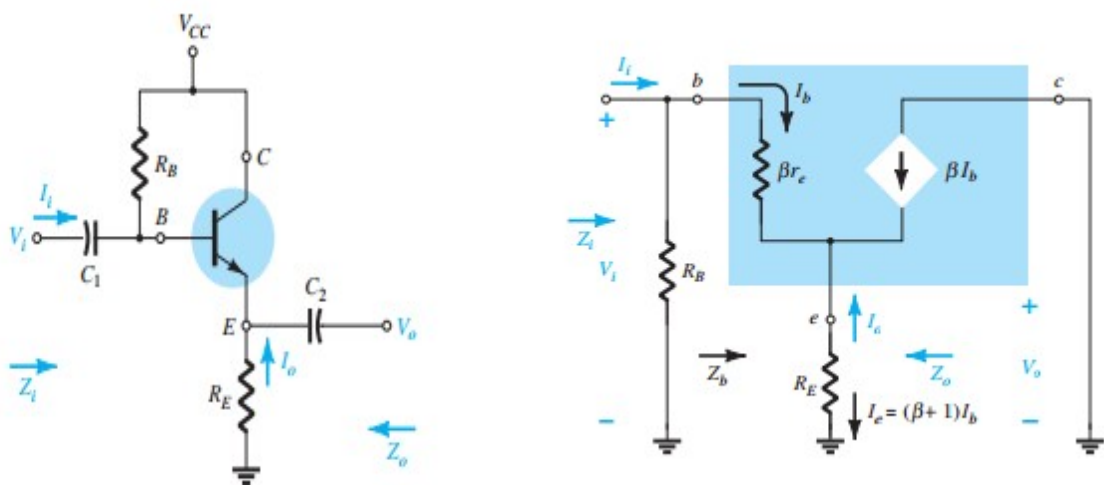

- $Z_i \approx R_C \parallel Z_b$

$$Z_b \approx \beta r_e \parallel (\beta + 1) R_E$$

at  $R_E \gg r_e$

$$Z_b \approx \beta r_e \parallel R_E \parallel Z_b \approx \beta R_E$$

- $Z_o$ :

$$I_b \approx \frac{V_i}{Z_b}, I_e \approx (\beta + 1) I_b \approx (\beta + 1) \frac{V_i}{Z_b}$$


$$I_e \approx (\beta + 1) \frac{V_i}{\beta r_e \parallel (\beta + 1) R_E}$$

$$I_e \approx \frac{V_i}{\beta r_e \parallel (\beta + 1) R_E} \text{ But } \beta + 1 \approx \frac{\beta + \beta r_e}{\beta + 1} \approx r_e$$

$$I_e \approx \frac{V_i}{r_e \parallel R_E}$$

To determine  $Z_o$ ,  $V_i$  is set to zero
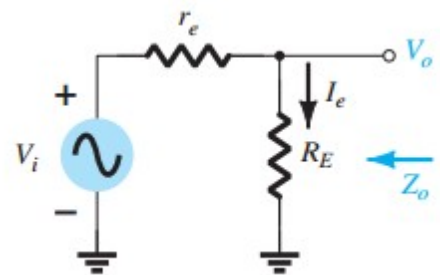
$$Z_o \approx R_E \parallel r_e \text{ then } Z_o \approx r_e$$



- $A_v$ :

$$V_o \approx \frac{R_E V_i}{r_e \parallel R_E} \approx A_v \frac{V_o}{V_i} \frac{R_E}{r_e \parallel R_E}$$

Since  $R_E \gg r_e$  then  $r_e \parallel R_E \approx R_E$

$$A_v \approx \frac{V_o}{V_i} \approx 1$$

### Effect of $r_o$

$$Z_i \approx Z_b \parallel \beta r_e \parallel \frac{\beta + 1}{1 \parallel R_E} r_o$$

if  $r_o \geq 10 R_E$

$$Z_b \approx \beta r_e \parallel \beta (1) R_E$$

$$Z_b \approx \beta r_e \parallel R_E$$

$$Z_o : Z_o \approx r_o \parallel R_E \parallel \frac{\beta r_e}{\beta (1)}$$

Using  $\beta (1) \approx \beta$

$$Z_o \approx r_o \parallel R_E \parallel r_e \text{ since } r_o \gg r_e$$

$$Z_o \approx r_o \parallel R_E$$

$$A_v : A_v \approx \frac{\beta (1) R_E}{1 \parallel R_E \parallel r_o}, A_i \approx -A_v \frac{Z_i}{R_L}$$


$$\text{If } r_o \geq 10 R_E \text{ } \beta (1) \approx \beta \text{ We find } A_v \approx \frac{\beta R_E}{Z_b}$$

$$\text{But } Z_b \approx \beta r_e \parallel R_E, A_v \approx \frac{\beta R_E}{\beta r_e \parallel R_E} \approx A_v \approx \frac{R_E}{r_e \parallel R_E}$$
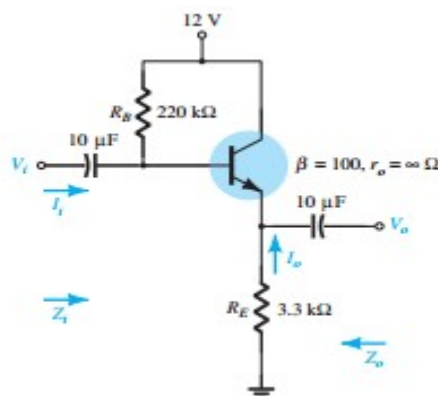
### Example :

For the emitter-follower network, determine:

- re.
- Zi.
- Zo.
- Av.
- Repeat parts (b) through (d) with  $r_o = 25 \text{ k}$  and compare results.



Solution:

$$\text{a. } I_B \approx \frac{V_{CC} - V_{BE}}{R_B \parallel \beta (1) R_E} \approx \frac{12 - 0.7}{220 \text{ k} \parallel 101 \parallel 3.3 \text{ k}} \approx 20.42 \mu A.$$

$$I_E \approx \beta (1) I_B \approx 101 \parallel 20.42 \mu A \approx 2.062 \text{ mA}.$$

$$r_e = \frac{26mV}{I_E} = \frac{26mV}{2.062m} = 12.61 \Omega$$

b.  $Z_b \cong \beta r_e \cong \beta \cong 1 \parallel R_E \cong 100 \parallel 12.61 \cong 101 \parallel 3.3k \cong 334.56k \Omega \cong \beta R_E$   
 $Z_i \cong R_B \parallel Z_b \cong 220k \parallel 334.56k \cong 132.72k \Omega.$

c.  $Z_o \cong R_C \parallel r_e \cong 3.3k \parallel 12.61k \cong 12.56 \Omega \cong r_e.$

d.  $A_v \cong \frac{V_o}{V_i} \cong \frac{R_E}{r_e \cong R_E} \cong \frac{3.3k}{12.61 \cong 3.3k} \cong 0.996 \cong 1$

e.  $r_o \geq 10 R_E$  Checking

$25k \Omega \geq 10 \parallel 3.3k \parallel 33k$  Not satisfied , Therefore


$$Z_b \cong \beta r_e \cong \frac{\beta \cong 1 \parallel R_E}{1 \cong R_E \cong r_o} \cong 100 \parallel 12.61 \cong \frac{100 \cong 1 \parallel 3.3k}{1 \cong \frac{3.3k}{25k}} \cong 295.7k \Omega.$$

$$Z_i \cong R_B \parallel Z_b \cong 220k \parallel 295.7k \Omega \cong 126.15k \Omega.$$


$$Z_o \cong R_C \parallel r_e \cong 3.3k \parallel 12.61k \cong 12.56 \Omega.$$

$$A_v \cong \frac{\beta \cong 1 \parallel R_E \cong Z_b}{1 \cong R_E \cong r_o} \cong \frac{100 \cong 1 \parallel 3.3k \cong 295.7k}{1 \cong \frac{3.3k}{25k}} \cong 0.996 \cong 1$$

#### 4-Common-Base Configuration:

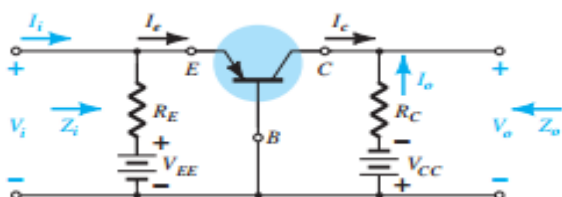

$$Z_i : Z_i \cong R_E \parallel r_e$$

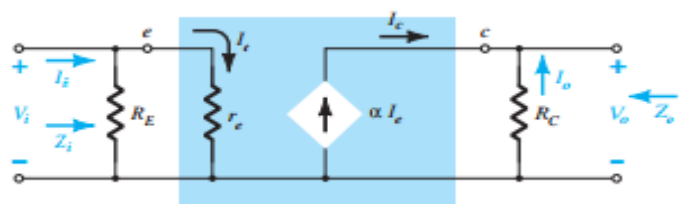

$$Z_o : Z_o \parallel R_C$$

$$A_v : V_o \parallel I_o R_C \parallel -I_C \parallel R_C \parallel \alpha I_C R_C$$

$$I_C \parallel \frac{V_i}{r_e}, V_o \parallel \alpha \left( \frac{V_i}{r_e} \right) R_C$$

$$A_v \parallel \frac{V_o}{V_i} \cong \frac{\alpha R_C}{r_e} \cong \frac{R_C}{r_e}$$

$A_i$  : Assuming  $R_E \parallel r_e$  Yields

$$I_C \parallel I_i$$

$$A_i \parallel \frac{I_o}{I_i} \parallel -\alpha \parallel -1$$

### Effect of $r_o$


$$r_o \parallel \frac{1}{h_{ob}} \parallel R_C, \text{ Then } r_o \parallel R_C \parallel R_C$$



**Example :**

For the emitter-follower network, determine:

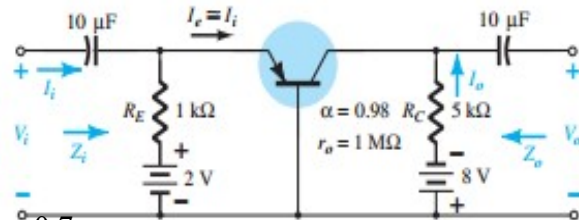- a.  $r_e$ .    b.  $Z_i$ .    c.  $Z_o$ .    d.  $A_v$ .    e.  $A_i$



Solution:

a.  $I_E \approx \frac{V_E - V_{BE}}{R_E} \approx \frac{2 - 0.7}{1k} \approx 1.3mA$

$r_e \approx \frac{26mV}{I_E} \approx \frac{26mV}{1.3m} \approx 20\Omega$



b.  $Z_i \approx R_E \parallel r_e \approx 1k \parallel 20 \approx 19.61\Omega \approx r_e$

c.  $Z_o \approx R_C \approx 5k\Omega$

d.  $A_v \approx \frac{R_C}{r_e} \approx \frac{5k}{20} \approx 250$

e.  $A_i \approx -\alpha \approx -0.98 \approx -1$

**5-Collector Feedback Configuration:**

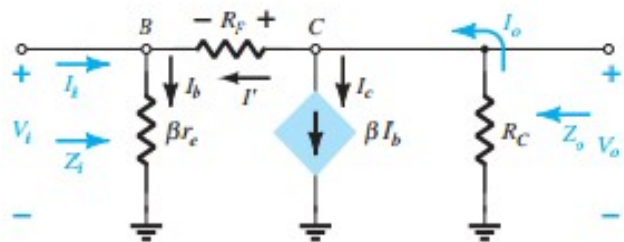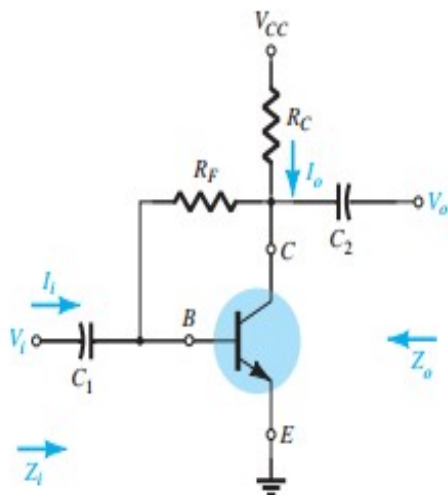

$$Z_i: I_i \frac{V_o - V_i}{R_F} \text{ with } V_o = -I_o R_C = -\beta I_b R_C$$

since  $\beta I_b$  is normally much larger than  $I_i$ ,  $I_o \approx \beta I_b$

$$\oplus V_o = -\beta I_b R_C = -\beta I_b R_C$$

$$\text{but } I_b = \frac{V_i}{\beta r_e}$$

$$\oplus V_o = -\beta \frac{V_i}{\beta r_e} R_C = -\frac{R_C}{r_e} V_i$$

$$\text{Therefore } \frac{V_o - V_i}{R_F} = \frac{V_o}{R_F} - \frac{V_i}{R_F} - \frac{R_C V_i}{r_e R_F} = \frac{V_i}{R_F} \left[ \frac{-1}{R_F} - \frac{R_C}{r_e} \right] V_i$$

$$\text{The result: } V_i = I_i \beta r_e = I_i \beta r_e \left[ \frac{R_C}{R_F} - \frac{1}{\beta r_e} \right]$$


$$V_i = I_i \beta r_e - \frac{1}{R_F} \frac{R_C}{r_e} \beta r_e V_i \Rightarrow V_i \left[ 1 + \frac{\beta r_e}{R_F} \frac{R_C}{r_e} \right] = I_i \beta r_e$$

$$Z_i = \frac{V_i}{I_i} = \frac{\beta r_e}{1 + \frac{\beta r_e}{R_F} \frac{R_C}{r_e}}, \text{ But } R_C \gg r_e \Rightarrow \frac{R_C}{r_e} \approx \frac{R_C}{r_e}$$

$$Z_i = \frac{\beta r_e}{1 + \frac{\beta R_C}{R_F}} \Rightarrow Z_i = \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}$$

$Z_o$ : If we let  $V_i = 0 V$ .

$$Z_o = R_C \parallel R_F$$

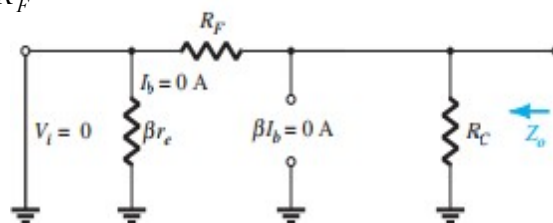

$A_v$ : at node C,  $I_o = \beta I_b = I_i$

For typical value  $\beta I_b \gg I_o$   $I_o \cong \beta I_b$ , we have:

$$V_o = -I_o R_C - \beta I_b R_C, \quad I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) R_C \Rightarrow A_v = \frac{V_o}{V_i} = \frac{-R_C}{r_e}$$

### Phase Relationship

The negative sign indicates a 180° phase shift between  $V_o$  and  $V_i$ .

**Effect of  $r_o$**

$Z_i$ : A complete analysis without applying approximations results  $\oplus$

$$Z_i = \frac{1 \parallel \frac{R_C \parallel r_o}{R_F}}{\frac{1}{\beta r_e} \parallel \frac{1}{R_F} \parallel \frac{R_C \parallel r_o}{R_F r_e}}$$

Recognizing that  $\frac{1}{R_F} \cong 0$  and Applying the condition  $r_o \geq 10 R_C$  we obtain

$$Z_i = \frac{1 \parallel \frac{R_C}{R_F}}{\frac{1}{\beta r_e} \parallel \frac{R_C}{R_F r_e}} \quad \text{but typically } \frac{R_C}{R_F} \ll 1 \quad \text{and}$$

$$Z_i = \frac{1}{\frac{1}{\beta r_e} \parallel \frac{R_C}{R_F r_e}} \quad \text{or} \quad Z_i = \frac{r_e}{\frac{1}{\beta} \parallel \frac{R_C}{R_F}}$$

$Z_o$ : Including  $r_o$   $\oplus$  with  $R_C$

$$Z_o = R_C \parallel R_F \parallel r_o$$

For  $r_o \geq 10 R_C$ ,  $Z_o = R_C \parallel R_F$  as obtained  $R_F \gg R_C$

$$Z_o \cong R_C$$

$$A_i = \frac{h_{fe} R_F}{R_F \parallel h_{fe} R_C} \approx \frac{R_F}{R_C}$$

$$A_v = \frac{r_o \parallel R}{\frac{1}{R_F} \parallel \frac{1}{r_e} \parallel \frac{1}{1 \parallel \frac{r_o \parallel R_C}{R_F}}}$$

$A_v$ :  $A_v$   $\oplus$

Since  $R_F \gg r_e$

$$A_v \approx \frac{r_o \parallel R_C}{1 + \frac{r_o \parallel R_C}{R_F}}$$

For  $r_o \geq 10 R_C$

$$A_v \approx \frac{R_C}{1 + \frac{R_C}{R_F}}$$

And since  $\frac{R_C}{R_F} \ll 1$


$$A_v \approx \frac{-R_C}{r_e}$$

**Example:**

For the network Determine

a.  $r_e$    b.  $Z_i$    c.  $Z_o$    d.  $A_v$

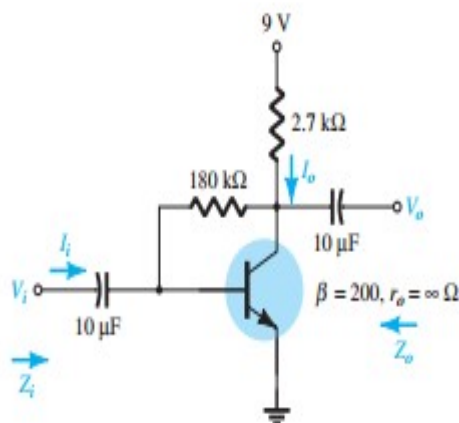e. Repeat parts (b) through (d) with  $r_o = 20 \text{ k}$  .



Solution:

$$a. \quad I_B \approx \frac{V_{CC} - V_{BE}}{R_B + \beta R_E} = \frac{9 - 0.7}{180 \text{ k} + 200 \cdot 2.7 \text{ k}} = 11.53 \mu A.$$

$$I_E \approx \beta + 1 \cdot I_B = 201 \cdot 11.53 \mu A = 2.32 \text{ mA}.$$

$$r_e = \frac{26mV}{I_E} = \frac{26mV}{2.32m} = 11.21 \Omega$$

b. 
$$Z_i = \frac{r_e}{\frac{1}{\beta} \left( \frac{R_C}{R_F} \right)} = \frac{11.21}{\frac{1}{200} \left( \frac{2.7k}{180k} \right)} = \frac{11.21}{0.0075} = 1494.67 \Omega \approx 1.5k \Omega$$

c. 
$$Z_o = R_C \parallel R_F = 2.7k \parallel 180k = 2.66k \Omega$$

d. 
$$A_v = \frac{-R_C}{r_e} = \frac{-27k}{11.21} = -2408.6$$

e. The condition  $r_o \geq 10R_C$  is *not* satisfied. Therefore,

$$Z_i = \frac{1}{\frac{1}{200} \left( \frac{1}{11.21} \left( \frac{1}{180k} + \frac{1}{2.7k \parallel 20k} \right) \right)} = \frac{1}{\frac{1}{200} \left( \frac{1}{11.21} \left( \frac{1}{180k} + \frac{1}{2.35k} \right) \right)}$$

$$Z_o = R_C \parallel R_F \parallel r_o = 2.7k \parallel 180k \parallel 20k = 2.35k \Omega \text{ vs } 2.66k$$

$$A_v = \frac{\frac{1}{R_F} \left( \frac{1}{r_e} \left( \frac{r_o \parallel R_C}{R_F} \right) \right)}{\frac{1}{180k} \left( \frac{1}{11.21} \left( \frac{r_o \parallel R}{2.38k} \right) \right)} = \frac{5.56 \times 10^{-6} - 8.92 \times 10^{-2}}{1 \times 0.013} = -209.56 \text{ vs } -240.8$$


## 6-Collector Feedback Configuration with an emitter resistor $R_E$ :

$$Z_i \approx \frac{R_E}{\frac{1}{\beta} \frac{R_E \parallel R_C}{R_F}}$$

$$Z_o \approx R_C \parallel R_F$$

$$A_v \approx \frac{-R_C}{R_E}$$
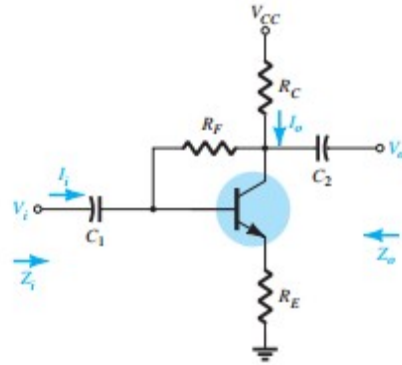
$$A_i \approx \frac{R_F}{R_E \parallel R_F \parallel \frac{R_F}{h_{fe}}}$$



### Feedback CCT

$Z_i$  :

$$I_b \approx I_i \frac{V_o - V_i}{R_F}$$

$$I_b \approx I_i \frac{V_o}{R_F} \quad V_o \approx V_i$$

$$V_i \approx I_b h_{ie} \approx V_i \frac{V_o}{R_F} h_{ie}$$

$$V_i \approx h_{ie} I_i \frac{h_{ie}}{R_F} V_o$$

$$V_o \approx A_v V_i, A_v \approx \frac{V_o}{V_i}$$

$$V_i \approx h_{ie} I_i \frac{h_{ie} A_v V_i}{R_F}$$

$$V_i \left( 1 - \frac{h_{ie} A_v}{R_F} \right) = h_{ie} I_i$$

$$\frac{V_i}{I_i} = \frac{h_{ie}}{1 - \frac{h_{ie} A_v}{R_F}} = Z_i \parallel X \parallel Y = \frac{X \cdot Y}{X + Y} = \frac{Y}{1 + \frac{Y}{X}}$$

$$Z_i = \frac{h_{ie}}{1 - \frac{h_{ie} A_v}{R_F}} \approx Z_i \parallel h_{ie} \parallel \frac{R_F}{A_v}$$

$A_i$ :

$$V_i = V_{R_F} - V_o = 0$$

$$I_b h_{ie} = I_b - I_i \parallel R_F = I_o R_C = 0$$

$$I_o = h_{fe} I_b$$

$$I_b h_{ie} = I_b R_F - I_i R_F = h_{fe} I_b R_C$$

$$I_b h_{ie} = R_F = h_{fe} R_C + I_i R_F$$

$$I_b = \frac{I_o}{h_{fe}} + I_o = h_{fe} I_b$$

$$\frac{I_o}{h_{fe}} h_{ie} = R_F = h_{fe} R_C + I_i R_F$$


$$I_o = \frac{h_{fe} I_i R_F}{h_{ie} R_F + h_{fe} R_C}$$

$$A_i = \frac{I_o}{I_i} = \frac{h_{fe} R_F}{R_F + h_{fe} R_C} h_{ie} \ll$$



$$A_i \approx \frac{R_F}{R_C} \text{ if } h_{fe} R_C \gg R_F$$

### Collector DC Feedback Configuration:

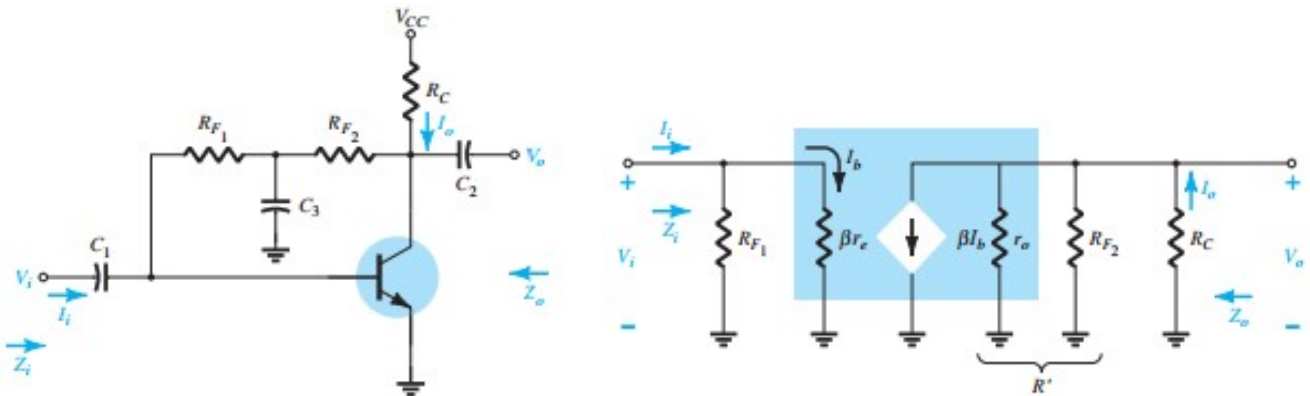

$$Z_i \approx R_{F1} \parallel \beta r_e$$

$$Z_o \approx R_C \parallel R_{F2} \parallel r_o$$

For  $r_o \geq 10 R_C$   $Z_o \approx R_C \parallel R_{F2}$

$$R' \approx r_o \parallel R_C \parallel R_{F2}$$

$$V_o \approx -\beta I_b R' \quad , \quad I_b \approx \frac{V_i}{\beta r_e} \quad , \quad V_o \approx -\beta \left( \frac{V_i}{\beta r_e} \right) R'$$

$$A_v \approx \frac{V_o}{V_i} \approx \frac{-r_o \parallel R_C \parallel R_{F2}}{r_e}$$

For  $r_o \geq 10 R_C$

$$A_v \approx \frac{-R_C \parallel R_{F2}}{r_e}$$


### Phase Relationship :

The negative sign ,clearly reveals a 180° phase shift between input and output voltages.

### Example :

For the network, determine:

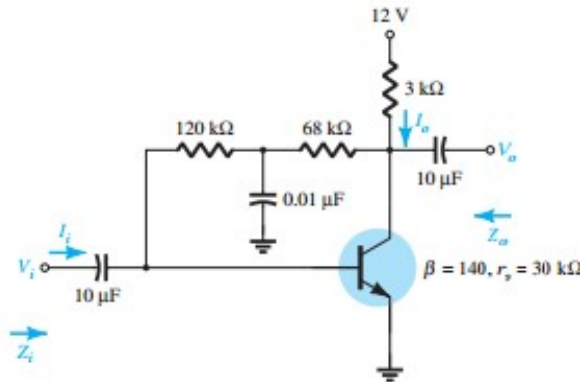- a.  $r_e$ .    b.  $Z_i$ .    c.  $Z_o$ .    d.  $A_v$ .




Solution:

a.  $I_B = \frac{V_{CC} - V_{BE}}{R_F + \beta R_C} = \frac{12 - 0.7}{120k + 60k + 140 \cdot 3k} = 18.6 \mu A$

$I_E = \beta + 1 I_B = 141 \cdot 18.6 \mu A = 2.62 mA$

$r_e = \frac{26mV}{I_E} = \frac{26mV}{2.62mA} = 9.92 \Omega$

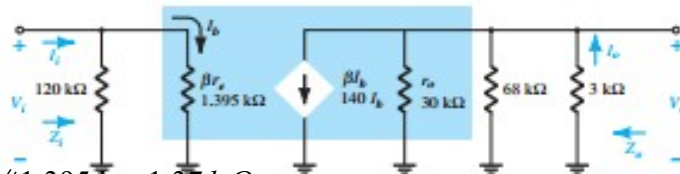b.  $\beta r_e = 140 \cdot 9.92 = 1.39 k \Omega$



$Z_i = R_{F1} \parallel \beta r_e = 120k \parallel 1.395k \approx 1.37 k \Omega$

c. Testing condition  $r_o \geq 10 R_C$  we find  
 $30 k \Omega \geq 10 \cdot 3 k \Omega$  which is satisfied

$Z_o \approx R_C \parallel R_{F2} = 3 k \parallel 68 k = 2.87 k \Omega$

d.  $r_o \geq 10 R_C$  therefore

$A_v = \frac{-R_C \parallel R_{F2}}{r_e} = \frac{-68k \parallel 3k}{9.92} = \frac{-2.87k}{9.92} = -289.3$

**Hybrid Versus  $r_e$  Model:**

The hybrid versus  $r_e$  model for CE and CB transistor configurations are shown in Figs. 12-11 (a) and (b) respectively.

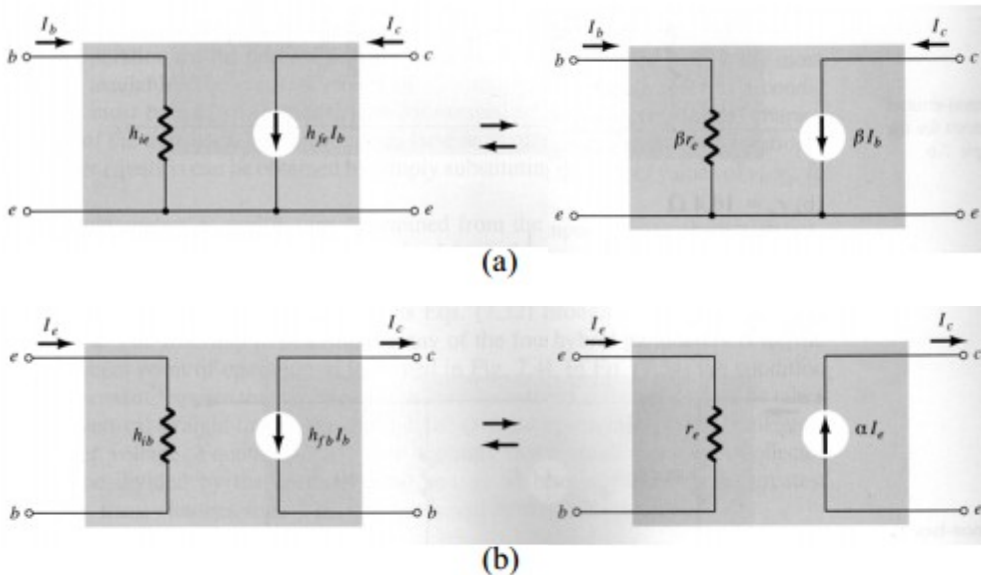


Fig. 12-11

**Approximate Conversion Formulas for Hybrid and  $r_e$  Models:**

The approximate conversion formulas for hybrid and  $r_e$  models for CB and CC configurations are listed in Table 12-4.

Table 12-4

CB Configuration	CC Configuration
$1 \cong h_{fe}$ $r_e \cong r_e$ $h_{ib} \cong h_{ie}$	$h_{ic} \cong h_{ie} \cong \beta r_e$
$1 \cong h_{fe}$ $h_{rb} \cong h_{ie} h_{oe} - h_{re}$	$h_{rc} = 1 - h_{re} \cong 1$
$1 \cong h_{fe}$ $h_{fb} \cong h_{fe}$	$h_{fc} \cong -1 \cong -\beta$
$1 \cong h_{fe}$ $h_{ob} \cong h_{oe}$	$h_{oc} \cong h_{oe} \cong r_o$

**Exercise:**

Given  $I_E = 1.3 \text{ mA}$ ,  $\beta = 100$ , and  $r_o = 40 \text{ k}\Omega$ , sketch:

1. The CE and CB hybrid equivalent models.
2. The CE and CB  $r_e$  equivalent models.