

## Multistage and Compound Amplifiers

### Basic Definitions:


Amplifiers that create voltage, current, and/or power gain through the use of two or more stages (**devices**) are called **multistage (compound)** amplifiers. The circuitry used to connect the output of one stage of a multistage amplifier to the input of the next stage is called the coupling method. In general, there are three coupling methods: **RC coupling**, **direct coupling**, and **transformer coupling**.

### Cascade Amplifiers:

A popular connection of amplifier stages is the cascade connection. Basically, a cascade connection is a series connection with the output of one stage then applied as input to the second stage. A combination of FET and/or BJT stages can be used to provide high gain and high input impedance, as demonstrated by the following example.
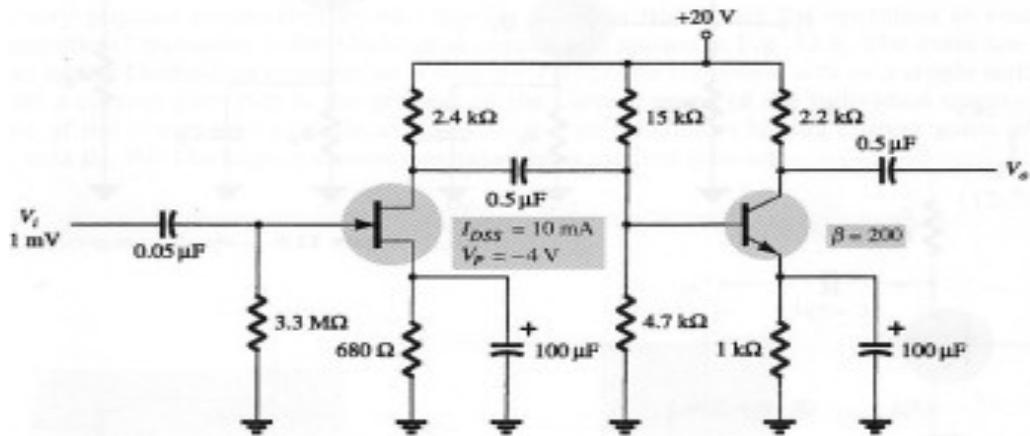
### Example 19-1:

Calculate the voltage gain, output voltage, input impedance, and output impedance for the cascade amplifier of Fig. 19-1. Calculate the output voltage resulting if a 10-k $\Omega$  load is connected to the output.



### Solution:

For the FET amplifier (stage 1),

$$V_{GS} = -1.9 \text{ V}, I_D = 2.8 \text{ mA}, \text{ and } \oplus$$

$$g_m = \frac{2I_{DSS}}{V_P} \left( 1 - \frac{V_{GS}}{V_P} \right) = \frac{2 \cdot 10mS}{-4} \left( 1 - \frac{-1.9}{-4} \right) = 2.6mS.$$

For the BJT amplifier (*stage2*),

$$V_B = 4.7V, V_E = 4.0V, V_C = 11.2V, I_E = 4.0mA,$$

$$r_e = \frac{0.026}{I_E} = \frac{26m}{4m} = 6.5\Omega$$

Since  $r_i \parallel Stage 2 \parallel 15k \parallel 4.7k \parallel 200 \parallel 6.5 \parallel 953.6\Omega$ , the gain of *stage1* (when loaded by *stage2*) is:

$$A_{v1} = -g_m R_D \parallel r_i \parallel Stage 2 \parallel -2.6m \parallel 2.4k \parallel 953.6 \parallel -1.77$$

The voltage gain of *stage2* is:

$$A_{v2} = \frac{-R_C}{r_e} = \frac{-2.2k}{6.5} = -338.46$$

The overall voltage gain is then:

$$A_v = A_{v1} A_{v2} = -1.77 \parallel -338.46 \parallel 599.1$$

The output voltage is then:

$$V_o = A_v V_i = 599.1 \parallel 1mV \approx 0.6V.$$

The input impedance of the amplifier is that of *stage1*,

$$Z_i = R_G = 3.3M\Omega.$$

While the output impedance of the amplifier is that of *stage2*,

$$Z_o = R_C = 2.2k\Omega.$$

If a 10-kΩ load is connected to the output, the resulting voltage across the load is:

$$V_L = \frac{R_L * V_o}{R_L + Z_o} = \frac{10k \parallel 0.6V}{10k + 2.2k} = 0.49V.$$

## Frequency Response of Cascade Amplifiers:

When amplifier stages are cascaded to form a multistage amplifier, the dominant frequency response is determined by the response of the individual stages. In general, there are two cases to consider:

### Different Cutoff Frequencies:

- When the lower-cutoff frequency,  $f_L$ , of each amplifier stage is different, the dominant lower-cutoff frequency,  $f_{L'}$ , equals the cutoff frequency of the stage with highest  $f_L$ .
- When the higher-cutoff frequency,  $f_H$ , of each amplifier stage is different, the dominant higher-cutoff frequency,  $f_{H'}$ , equals the cutoff frequency of the stage with lowest  $f_H$ .
- The overall bandwidth of a multistage amplifier is the difference between the dominant lower-cutoff frequency and the dominant higher-cutoff frequency.

$$BW = f_{H'} - f_{L'}$$

### Equal Cutoff Frequencies:

- When the lower-cutoff frequencies of each stage in a multistage amplifier are all the same, the dominant lower-cutoff frequency is increased by a factor of  $\sqrt{2^{1/n} - 1}$  as shown by the following formula:

$$f_{L'} = \frac{f_L}{\sqrt{2^{1/n} - 1}} \quad n: \text{the number of stages in the multistage amplifier.}$$

- When the higher-cutoff frequencies of each stage are the same, the dominant higher cutoff frequency is reduced by a factor of  $\sqrt{2^{1/n} - 1}$  as shown by the following formula:

$$f_{H'} = f_H \sqrt{2^{1/n} - 1}$$

### Example 19-2:

Fig. 19-2 shows an amplifier consisting of a common-emitter stage driving an emitter follower (a common-collector) stage. The transistors have the following parameter values:  $Q_1$ :  $r_{e1} = 15 \Omega$ ,  $\beta_1 = 180$ ,  $r_{o1} \approx \infty$ , and  $Q_2$ :  $r_{e2} = 25 \Omega$ ,  $\beta_2 = 100$ ,  $r_{o2} \approx \infty$ . Find  $A_{vs} = V_o/V_s$ , and  $f_L$ .

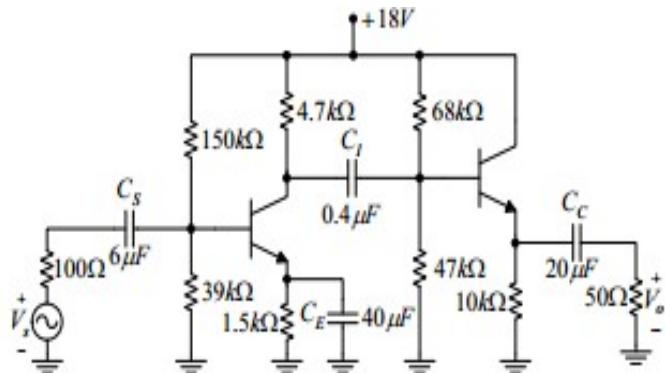


Fig. 19-2

### Solution:

$$r' = R_E \parallel R_L = 10k \parallel 50 \approx 50 \Omega,$$

$$r_i = \frac{1}{\beta_2} r_{e2} = \frac{1}{\beta_2} (r' + r_e) = \frac{1}{\beta_2} (50 + 47k \parallel 100 \parallel 25 \parallel 50) = 5.9 k\Omega,$$

$$A_{v1} = \frac{-R_C \parallel r_i}{r_{e1}} = \frac{-4.7k \parallel 5.9k}{15} = -174.4$$

$$r'_s = \frac{R_1 \parallel R_2 \parallel R_C}{\beta_2} = \frac{68k \parallel 47k \parallel 4.7k}{100} \approx 40 \Omega,$$

$$A_{v1} = \frac{r'}{r'_s r_{e2}} = \frac{50}{40 \parallel 25 \parallel 50} = 0.435$$

$$r_i = \frac{1}{\beta_1} r_{e1} = \frac{1}{\beta_1} 150k = 39k \parallel 180 \parallel 15 = 2.48 k\Omega,$$

$$A_{vs} = \frac{r_i}{r_i \parallel R_s} A_{v1} \cdot A_{v2} = \frac{2.48k}{2.48k \parallel 100} = -174.4 \parallel 0.435 = -72.9$$

$$f_{L_s} = \frac{1}{2\pi (r_i \parallel C_S)} = \frac{1}{2\pi (100 \parallel 2.48k \parallel 6\mu)} = 10.3 \text{ Hz}$$

$$R_{e1} = R_E \parallel r_{e1} = \frac{R_1 \parallel R_2 \parallel R_s}{\beta_1} = \frac{1.5k \parallel 15 \parallel \frac{150k \parallel 39k \parallel 100}{180}}{\beta_1} \approx 15 \Omega,$$

$$f_{L_E} = \frac{1}{2\pi R_{e1} C_1} = \frac{1}{2\pi \cdot 15 \cdot 40 \mu} = 265.3 \text{ Hz.}$$

$$f_{L_1} = \frac{1}{2\pi R_C r_i \cdot Stage\ 2 \cdot C_1} = \frac{1}{2\pi \cdot 4.7 \cdot 5.9 \cdot k \cdot 0.4 \mu} = 37.5 \text{ Hz}$$

$$R_{e2} \parallel R_E \parallel r_{e2} \parallel r_s' \parallel 10k \parallel 25 \parallel 40 \approx 65 \Omega,$$

$$R_L \parallel R_{e2}$$

$$\oplus C$$

$$\oplus C$$


$$2\pi \oplus$$

$$f_{L_c} = \frac{1}{\oplus}$$

$$f_{L_c} = \text{Max.} (f_{L_s}, f_{L_E}, f_{L_1}, f_{L_C}) = 265.3 \text{ Hz.}$$
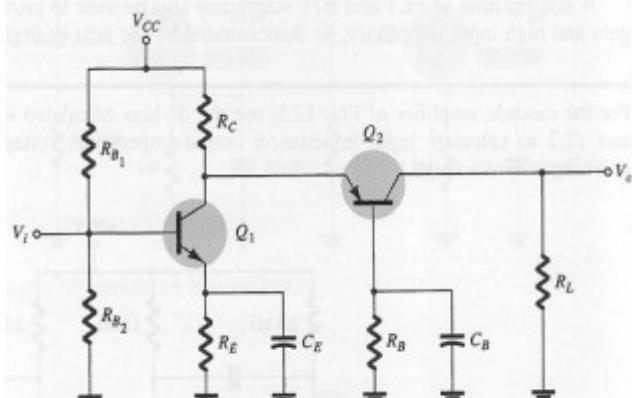
## Cascode Amplifiers:

A cascode connection has one transistor one top of (in series with) another. Fig. 19-3a shows a cascode configuration with common-emitter (CE) stage feeding a commonbase (CB) stage. This arrangement is designed to provide a high input impedance with low voltage gain to insure that the input Miller capacitance is at a minimum with the CB stage providing good high-frequency operation. A practical BJT version of a cascode amplifier is provided in Fig. 19-3b.



(a)

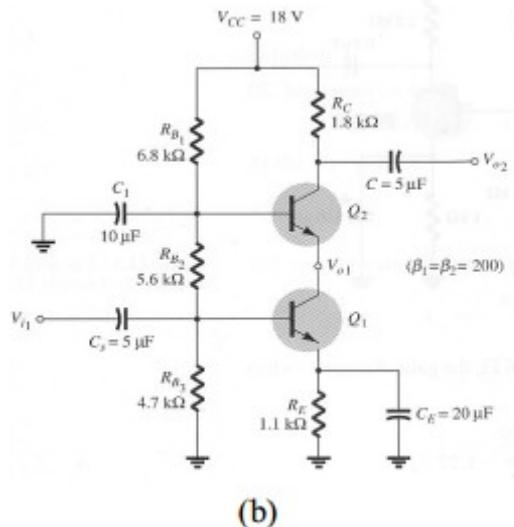


Fig. 19-3

### Example 19-3:

Calculate the voltage gain for the cascode amplifier of Fig. 19-3b.

#### Solution:

From dc analysis,

$$V_{B1} = 4.9\text{ V}, V_{B1} = 10.8\text{ V}, \circ I_{E1} \approx I_{C1} = I_{E2} \approx I_{C2} = 3.8\text{ mA}.$$

The dynamic resistance of each transistor is then:

$$r_{e1} \approx r_{e2} = \frac{0.026}{I_E} = \frac{26m}{3.8m} = 6.8\text{ }\Omega.$$

The voltage gain of stage 1 (common-emitter) is approximately:..

$$A_{v1} = \frac{-r_{e2}}{r_{e1}} - 1$$

The voltage gain of stage 2 (common-base) is:..

$$A_{v2} = \frac{R_C}{r_{e1}} = \frac{1.8k}{6.8} = 265.$$

Resulting in an overall cascode amplifier gain of.

$$A_v = A_{v1} A_{v2} = -10 \cdot 265 = -265.$$


### Cascaded Systems

The two-port systems approach is particularly useful for cascaded systems where:

$$A_{VT} = A_{V1} \cdot A_{V2} \cdot A_{V3} \cdots$$

And the total current gain is given by:

$$A_{iT} = A_{vT} \frac{Z_{i1}}{R_L}$$

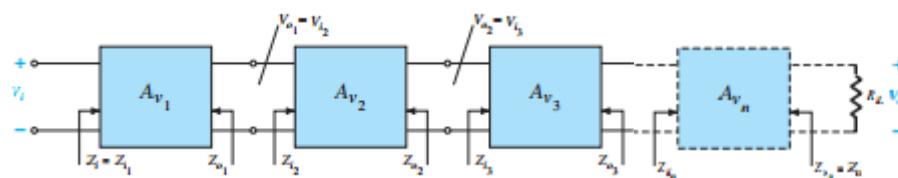

$$A_{iT} = A_{i1} \cdot A_{i2} \cdot A_{i3} \cdots A_{in}$$

$$A_{vT} = A_{iT} \cdot \frac{Z_L}{Z_{i1}}$$

$$A_{pT} = A_{vT} \cdot A_{iT}$$

overall power gain of the system.


### RC-coupled BJT amplifiers:

The name is derived from the capacitive coupling capacitor  $C_c$  and the fact that the load on the first stage is an  $RC$  combination. The input impedance of the second stage acts as a load on the first stage.

Example:

a. Calculate the no-load voltage gain and output voltage of the  $RC$ -coupled transistor amplifiers.

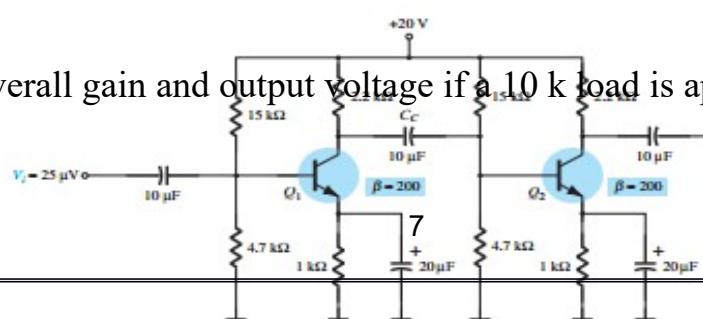b. Calculate the overall gain and output voltage if a  $10\text{ k}\Omega$  load is applied to the second stage.



c. Calculate the input impedance of the first stage and the output impedance of the second stage.

Solution:

$$V_B = 4.7 V, V_E = 4 V, V_C = 11 V, I_E = 4 mA$$

$$r_e = \frac{26 mV}{I_E} = \frac{26 mV}{4 mA} = 6.5 \Omega$$

$$Z_{i2} = R_1 \parallel R_1 \parallel \beta r_e$$

$$A_{v1} = \frac{\frac{R}{2.2 k \parallel 15 k \parallel 4.7 k \parallel 200 \parallel 6.5}}{\frac{R_c \parallel 1 \parallel R_1 \parallel \beta r_e}{\frac{r_e}{6.5 \Omega}}} = -102.3$$

For the unloaded second stage

$$A_{v2 \text{ NL}} = \frac{-R_c}{r_e} = \frac{-2.2 k}{6.5} = -338.46$$

$$A_{vT \text{ NL}} = A_{v1} A_{v2 \text{ NL}} = -102.3 \parallel -338.46 \parallel 34.6 \times 10^3$$

The output voltage :

$$V_o = A_{vT \text{ NL}} V_i = 34.6 \times 10^3 \parallel 25 \mu V = 865 mV$$


b)

$$Z_{i1} = R_1 \parallel R_2 \parallel \beta r_e = 4.4 k \parallel 15 k \parallel 200 \parallel 6.5 = 953.6 \Omega$$

$$Z_{o2} = R_c = 2.2 k \Omega$$

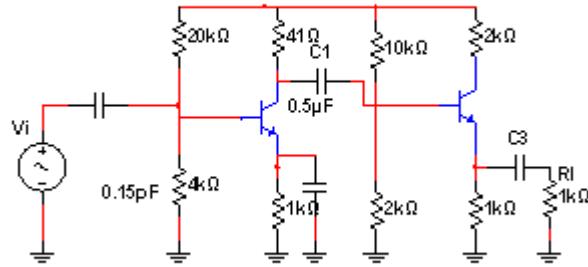Example:

$$Q1=Q2: h_{fe} = \beta = 50, h_{ie} = \beta r_e = 0.5 k\Omega$$



$Z_i$ :

$$Z_{i1} = 20 \parallel 4k \parallel 0.5k = 0.435k\Omega$$

$Z_o$ :

$$Z_o \text{ at } V_i = 0 \text{ is } R_{C2} = 2k\Omega$$

$A_i$ :


$$I_{b1} = \frac{R' I_{i1}}{R' + h_{ie}} \text{ if } R' \ll R_1 \parallel R_2, R = \{R\} \setminus \{3\} \parallel \{R\} \setminus \{4\}$$

$$I_{b1} = \frac{3.333k I_{i1}}{3.33k + 0.5k} = 0.87 I_{i1}$$

$$I_{o1} = \frac{-R_{C1} I_{c1}}{R_{C1} + 0.385k}$$

divider rule

current

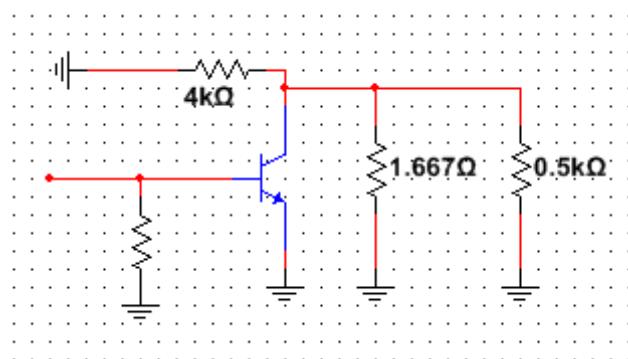

$$\oplus \frac{-4k h_{fe} I_{c1}}{4k \equiv 0.385k} = \frac{-4k h_{fe} I_{b1}}{4.385k} = \frac{-4 \cdot 50 \cdot 0.87 I_{i1}}{4.385k}$$

$$A_{i1} = \frac{I_{o1}}{I_{i1}} = -39.68$$

$$I_{b2} = R^{\{1\}}_{rsub\{12\}} \text{ over } \{R\}^{\wedge} \{h_{ie}\} = \frac{1,667k}{1.667k \equiv 0.5k} = 0.769 I_{i2}$$

$$I_{C2} = h_{fe} I_{b2} = 50 \cdot 0.769 I_{i2} = 38.45 I_{i2}$$


$$I_{o2}$$

$$h$$

$$2k \frac{\oplus fe I_{b2}}{2k \equiv 1k} = \frac{2k \cdot 38.45 I_{i2}}{3k} = 25.63 I_{i2}$$

$$\oplus \frac{-R_{C2} I_{c2}}{R_{C2} \equiv R_L} =$$
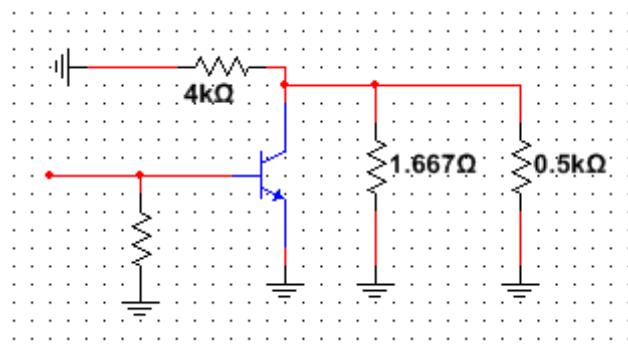
$$A_{i2} = \frac{I_{o2}}{I_{i2}} = 25.63$$



$$A_{iT} = A_{i1} \cdot A_{i2} = -39.68 \cdot 25.63 \approx 1017.$$

$A_V$ :

$$A_V = \frac{h_{fe} R_L}{h_{ie}} = \frac{-R_L}{r_e}, A_{V1} = \frac{-50 \cdot 0.3509k}{0.5k} = -35.09$$

$$A_{V2} = \frac{-50 \cdot R_{C2}}{0.5k} \parallel R_L = \frac{-50 \cdot 0.667k}{0.5k} = -66.7$$

Note:

$$R_{L1} \parallel R_{C1} \parallel R_3 \parallel R_4 \parallel h_{ie} = 0.3509k$$


$$A_{VT} = A_{V1} \cdot A_{V2} = -35.09 \cdot -66.7 \approx 2340.50$$

Or

$$A_{vT} = A_{iT} \cdot \frac{Z_L}{Z_{i1}} = \frac{1017}{0.435} \cdot 1k = 2337.93$$

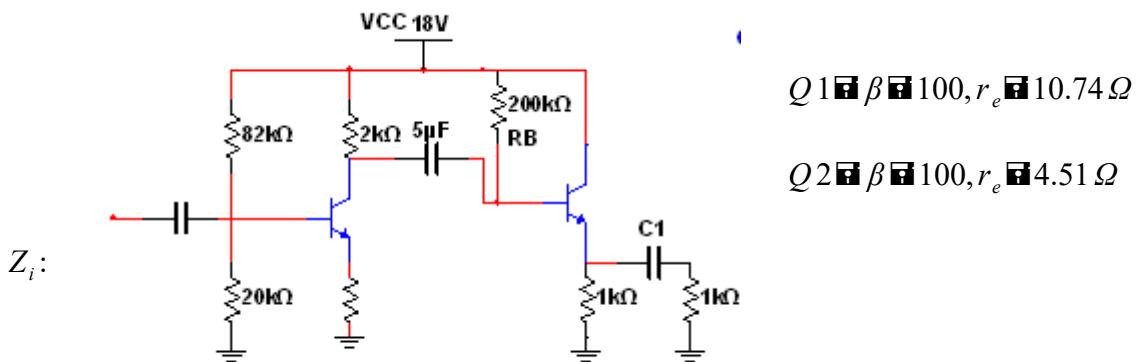Example:

Calculate the input and output impedance  $A_V, A_i$  of the two stage amplifier.



$$Z_i = R_1 \parallel R_2 \parallel \beta r_e = 82k \parallel 20k \parallel 1.074k \Omega \approx \beta r_e = 1.074k \Omega$$

$Z_o$ :


$$Z_o = \frac{R_s}{\beta} \parallel r_e, R_s = 2k \parallel 200k \parallel 2k$$

$$Z_o = \frac{2k}{\beta} \parallel r_e = 20 \parallel 4.51 = 4.51 \Omega$$

$A_V$ :

$$R_C \parallel R_B \parallel \beta R_E \parallel Z_L \quad \text{(1)}$$

$$A_V = \frac{-R_L}{r_{e1}}$$

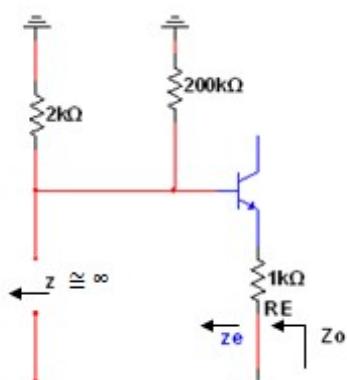

$$2k \parallel 200k \parallel 100 \parallel 1k \parallel 1k$$




$$V_{be2} \approx 0V, V_{be2} \approx V_o \text{ with } A_V = \frac{V_{o2}}{V_{o1}}$$

$$A_{VT} = A_{V1}, A_{V2} = -186.22 \parallel 1 \parallel -186.22$$

$$A_{iT} = A_{vT} = \frac{Z_{i1}}{Z_L} = 186.22 \frac{1.074k}{1k} \approx 200$$

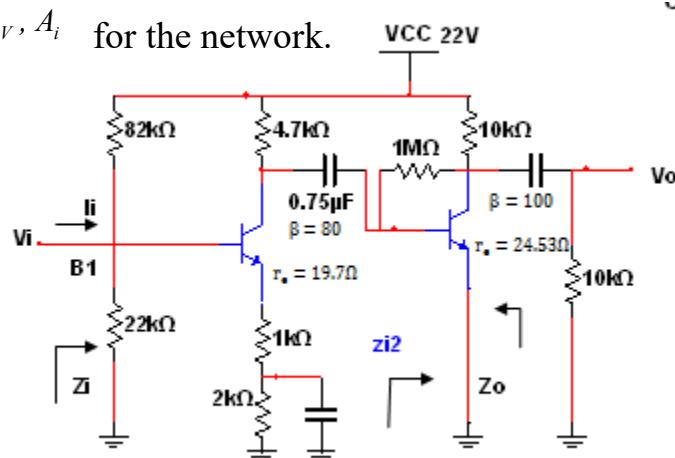Example:

Determine  $Z_i, Z_o, A_v, A_i$  for the network.



$$\begin{aligned} R &= \\ \text{---} \oplus \oplus E_1 &\parallel R_{E2} \parallel 22k \parallel 80 \parallel 3k \parallel 22 \parallel 240k & 22k \\ R' &\parallel R_{B2} \parallel \beta \oplus \end{aligned}$$

$$V_{B1} = \frac{R' * V_{CC}}{R' + R_{B1}} \approx \frac{R_{B2} V_{CC}}{R_{B2} + R_{B1}} = \frac{22k \parallel 22 \parallel 4.65V}{22k \parallel 8.2k} = 4.65V$$

$$V_{E1} = V_{B1} - V_{BE} = 4.65 - 0.7 = 3.95V$$

$$I_{E1} = \frac{V_{E1}}{R_{E1} + R_{E2}} = \frac{3.95}{3k} = 1.32mA$$

$$r_{e1} = \frac{26mV}{I_{E1}} = \frac{26mV}{1.32m} = 19.7\Omega$$

$$Z_i = R_{B1} \parallel R_{B2} \parallel \beta R_{E1} = 82k \parallel 22k \parallel 80k = 14.26k\Omega$$

$Z_o$ :

$$Z_o \text{ at } V_i = 0 \Rightarrow R_{C2} = 2k\Omega$$

$A_V$ :

$$V_{b1} = V_i \oplus A_{V1} \frac{-R_L}{R_{E1} + r_{e1}} - \frac{-R_C \parallel Z_{i2}}{R_{E1} + r_{e1}}$$

$$Z_{i2} = \frac{R_F}{A_{V2}} \parallel \beta r_e, Z_{i2} = \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}$$

$$A_{V2} = \frac{-R_L}{r_{e2}} \parallel \frac{-R_{C2} \parallel Z_L}{r_{e2}} = \frac{-5k}{24.53} = -203.83$$

$$Z_{i2} = \frac{10^6}{203.83} \parallel 100 \parallel 24.53 \parallel 4.906 \parallel 2.453k \parallel 1.6353k\Omega$$

$$A_{V1} = \frac{-94.7k \parallel 1.635k}{1k + 0.0197k} = \frac{-1.213}{1.0197} = -1.19$$


$$A_{VT} = A_{V1} \cdot A_{V2} = -1.19 \parallel -203.83 \parallel 242.56$$

$$A_i : A_{iT} \cdot A_{VT} \cdot \frac{Z_{i1}}{Z_L} = \frac{242.56 \parallel 14.26k}{10k} = 345.81$$

$$A_p = A_{iT} \cdot A_{VT} = 345.81 \parallel 242.56 \parallel 83.9 \parallel 10^3$$

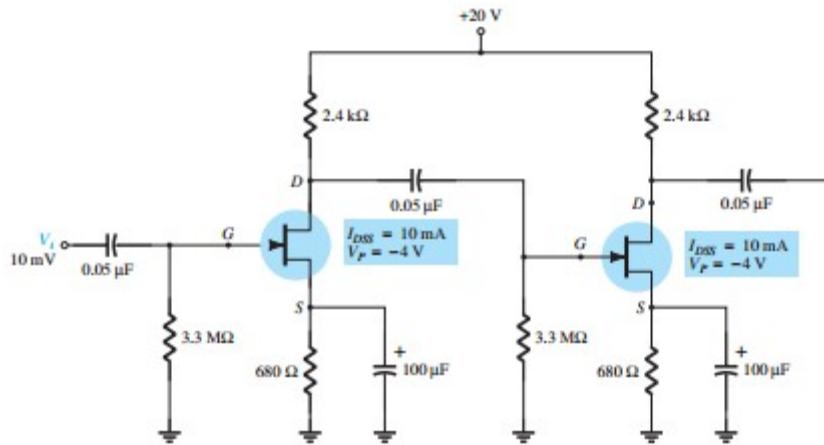Example:

Calculate the dc bias, voltage gain, input impedance, output impedance, for the cascade amplifier shown in Fig. and calculate load voltage if a  $10k\Omega$  load is connected.



Solution:

$$V_{GSQ} = -1.9V, I_{DQ} = 2.8mA \quad g_m = \frac{2I_{DSS}}{V_P} = \frac{2 \times 10mA}{-4V} = 5mS$$

$$g_m = g_{mo} \left( 1 - \frac{V_{GSQ}}{V_P} \right) = 5ms \left( 1 - \frac{-1.9V}{-4V} \right) = 2.6mS$$

$$A_{V2} = g_m R_D = 2.6mS \parallel 2.4k = -6.24$$

For the first stage:

$$A_{V1} = g_m R_D \parallel R_{G2} = 2.4 \text{ } k \parallel 3.3M \parallel 2.4k$$

$$A_V = A_{V1} A_{V2} = -6.24 \parallel -6.24 = 38.4$$

$$V_o = A_V V_i = 38.4 \parallel 10m = 384mV$$

The cascade amplifier input impedance:


$$Z_i = R_G = 3.3M \Omega \quad \text{Remake } Z_i = R_{G1}, Z_o = R_{D2}$$

$$Z_o = R_D = 2.4k\Omega \quad (\text{assuming that } r_d = \infty \Omega)$$

The voltage across a  $10k\Omega$  load is

$$V_o = \frac{R_L}{Z_o + R_L} V_i = \frac{10k}{2.4k + 10k} \parallel 384mV = 310mV$$
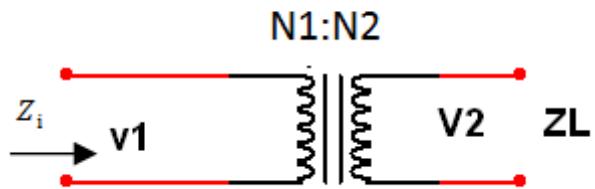
### Transformer-Coupled Transistor Amplifier:




$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = a \quad \text{transformation ratio} \quad \textcircled{1}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1} = \frac{1}{a}$$

$$Z_i = a^2 Z_L$$

Example:

For the network find  $A_v$

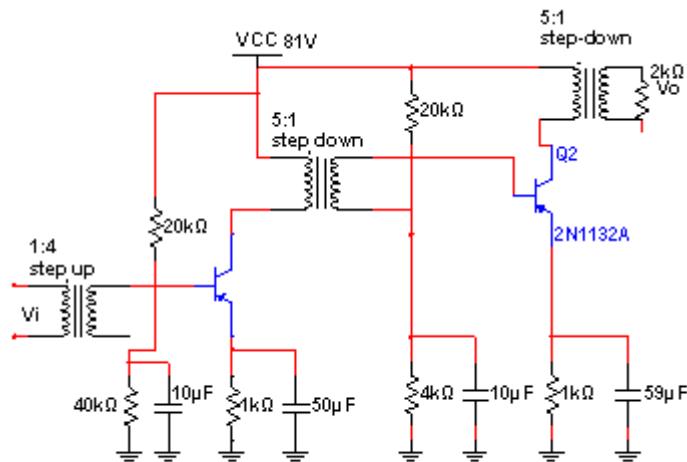


$$h_{fe} = \beta = 50$$

$$h_{ie} = \beta r_e = 2k\Omega$$

$$h_{oe} = 20 \text{ MA} \cdot V$$

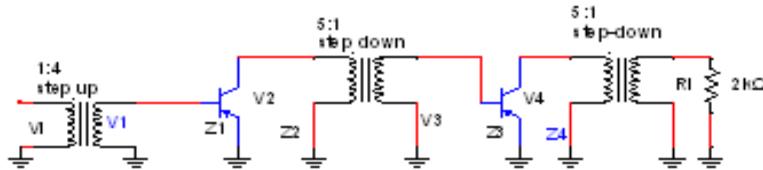For maximum power transfer the impedance  $Z_2, Z_4$  should be equal to the output impedance :



$$Z_o \cong \frac{1}{h_{oe}} \cdot \frac{1}{20\mu} \cdot 50k \Omega \parallel Z_2, Z_4 \parallel Z_0$$

$$Z_i = a^2 Z_L, Z_4 = a^2 R_L = 5^2 * 2k = 50 \parallel Z_2 = 50 \text{ where } Z_1, Z_3 \cong h_{ie} = 2k \Omega.$$

$$V_1 = \frac{N_2}{N_1} V_i = 4 V_i$$

$$A_{v1} = \frac{V_2}{V_1} = \frac{-h_{fe} Z_L}{h_{ie}} = \frac{-h_{fe}}{h_{ie}} \cong \frac{1}{-h_{oe}} \parallel Z_2 \quad \text{so that} \quad -50 \parallel 50k \parallel 50k \quad 2k = -625$$

$$V_2 = -625 V_1 = -625 \parallel 4 V_i \parallel -2500 V_i$$

$$\begin{aligned} & -2500 V \\ & \text{at } i = -500 V_i \\ & V_3 = \frac{N_2}{N_1} V_2 = \frac{1}{5} V_2 = \frac{1}{5} (-625) \end{aligned}$$


$$A_{v2} = \frac{V_4}{V_3} = \frac{-h_{fe} Z_L}{h_{ie}} = \frac{-50 \parallel 50k \parallel 50k}{2k} = -625$$

$$V_4 = -625 V_3 = -625 \parallel -500 V_i \parallel 312.50 * 10^3 V_i$$

$$V_L = \frac{1}{5} V_4 = \frac{1}{5} 312.50 * 10^3 V_i$$

$$A_{vT} = \frac{V_L}{V_i} = 62.50 \times 10^3$$
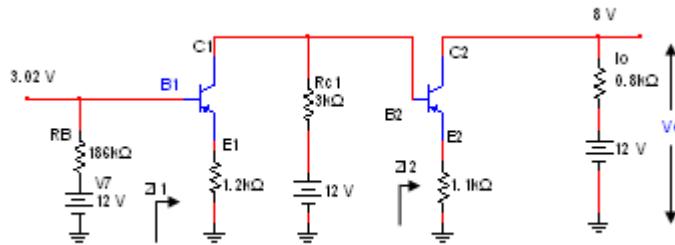
### Direct-Coupled Transistor Amplifiers:



$$\beta_1 = 40, r_{e1} = 13.47 \Omega, \beta_2 = 100, r_{e2} = 5.2 \Omega$$

Dc-conditions:

$$V_{c2} = 8V, I_o = \frac{12 - 8}{0.8k} = 5mA$$

$$I_{c2} \cong I_{E2} = 5mA$$

$$V_{E2} = 5mA * 101k = 5.5V$$

$$V_{BE} = 0.7V$$

$$V_{B2} = V_{c1} = 5.5 - 0.7 = 6.2V$$

$$I_{c2} \cong \beta_2 I_{B2}$$

$$I_{B2} = \frac{I_{c2}}{\beta_2} = \frac{5mA}{3k} = 1.93mA$$

$$I_{3k} \gg I_{B2}$$

$$I_{c1} \cong I_{3k} = 1.93mA$$

$$V_{E2} = 1.93mA * 1.2k = 2.32V$$

$$V_{B1} = V_{E1} = V_{BE1} = 2.32 \approx 0.7 = 3.02 \text{ V}$$

Ac-analysis:

$$Z_{\oplus} = \beta R_E \quad \text{for emitter-follower con.}$$

$$Z_{i1} = \beta_1 R_{E1} = 40 \parallel 1.2k \parallel 48k \Omega$$

$$Z_{i2} = \beta_2 R_{E2} = 100 \parallel 1.1k \parallel 110k \Omega$$

$$A_{v1} = \frac{-R_{L1}}{R_{E1}} = \frac{-R_{c1} \parallel \beta_2 R_{E2}}{R_{E1}} = \frac{3k \parallel 110k}{1.2k} \approx \frac{-3k}{1.2k} = -2.5$$

$$A_{v2} = \frac{-R_{L2}}{R_{E2}} = \frac{-R_{c2}}{R_{E2}} = \frac{-0.8k}{1.1k} = -0.7273$$

$$A_{vT} = A_{v1} A_{v2} = -2.5 \parallel -0.7273 = 1.818$$

$$A_i = A_v \parallel \frac{Z_{i1}}{Z_L} = \frac{1.818 \parallel 48k \parallel 109.08}{0.8k} = 109.08$$

$$A_{PT} = A_v \parallel A_i = 1.819 \parallel 109.08 = 198.3$$

### Example 19-4:

The silicon transistors in Fig. 19-4 have the following parameter values:

$Q_1: \beta_1 = 100, r_{o1} \approx \infty, C_{bc} = 4 \text{ pF}, C_{be} = 10 \text{ pF}$  and  $Q_2: \alpha_2 \approx 1, r_{o2} \approx \infty$ .

Find  $I_{C1}, I_{C2}, V_{C1}, V_{C2}, A_{vs}$ , and  $f_{Hi1}$ .

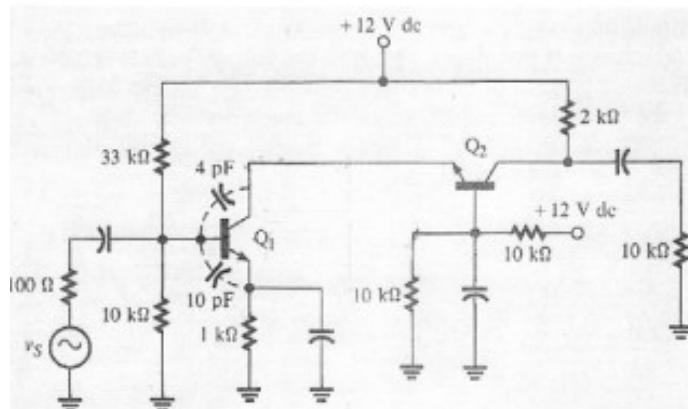


Fig. 19-4

**Solution:**

$$V_{B1} = \frac{10k \parallel 12\Omega}{10k + 33k} = 2.8V, V_{E1} = V_{B1} - 0.7 = 2.8 - 0.7 = 2.1V.$$

$$I_{C1} \approx I_{E1} = \frac{V_{E1}}{R_{E1}} = \frac{2.1}{1k} = 2.1mA, I_{E2} \approx I_{C2}, V_{B2} = \frac{10k \parallel 12\Omega}{10k + 10k} = 6V,$$

$$V_{C1} = V_{E2} = V_{B2} - 0.7 = 6 - 0.7 = 5.3V,$$

$$V_{C2} = V_{CC} - I_{C2} R_{C2} = 12 - 2.1mA \parallel 2k = 7.8V.$$

$$I_{E1} \approx I_{E2} \Rightarrow r_{e1} \approx r_{e2} = \frac{0.026}{I_E} = \frac{0.026}{2.1m} = 12.4\Omega,$$

$$A_{v1} = \frac{-r_{e2}}{r_{e1}} = -1, \quad A_{v2} = \frac{R_C \parallel R_L}{r_{e1}} = \frac{2k \parallel 10k}{12.4} = 134.4.$$

$$r_i = Stage 1 \parallel 33k \parallel 10k \parallel 100 \parallel 12.4 = 1.07k\Omega,$$

$$A_{vs} = \frac{r_i \parallel Stage 1 \parallel R_s}{r_i \parallel Stage 1 \parallel R_s} A_{v1} \cdot A_{v2} = \frac{1.07k \parallel 100}{1.07k \parallel 100} \parallel 134.4 = -123.$$

$$R_{TH_i} \parallel r_i \parallel \text{Stage 1} \parallel R_s \parallel 1.07k \parallel 100 \parallel 91.5 \Omega.$$

$$C_{i1} \parallel C_{be} \parallel C_{Mi} \parallel C_{be} \parallel C_{be} \parallel 1 - A_{v1} \parallel 10 pF \parallel 4 pF \parallel 2 \parallel 18 pF,$$

$$f_{Hi1} = \frac{1}{2\pi R_{TH_i} C_{i1}} = \frac{1}{2\pi \parallel 91.5 \parallel 18 pF} = 96.7 MHz.$$

## Darlington Amplifiers:

A very popular connection of two BJTs for operation as one "superbeta" transistor is the Darlington connection as shown in Fig. 19-5. The main feature of the Darlington connection is that the composite transistor acts as a single unit with current gain that is the product of the current gains of the individual transistors. That is

$$\beta_D = \beta_1 \beta_2 = \beta^2$$

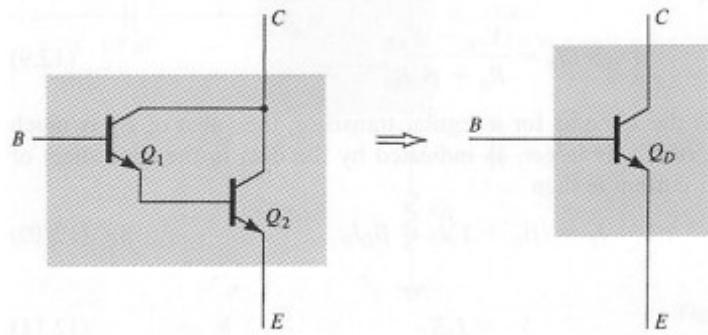


Fig. 19-5

### Example 19-5:

For the Darlington emitter-follower circuit shown in Fig. 19-6a, determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_E$ ,  $V_B$ ,  $V_C$ ,  $Z_b$ ,  $Z_i$ ,  $Z_o$ ,  $A_v$ , and  $A_v$ . Use  $\beta_D = 8000$ ,  $V_{BE} = 1.6$  V, and  $r_i = 5$  k $\Omega$ .

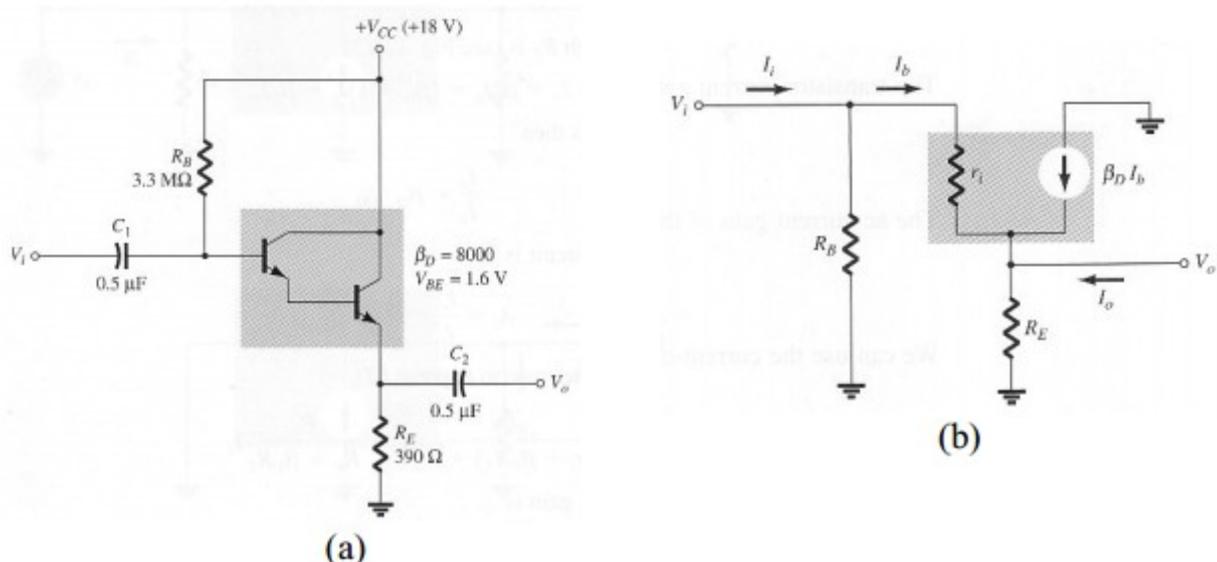


Fig. 19-6

### Solution:

From dc analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta_D R_E} = \frac{18 - 1.6}{3.3M + 8000 \times 390} = 2.56 \mu A$$

$$I_E = \beta_D I_B \approx \beta_D I_B = 8000 \times 2.56 \mu A = 20.48 mA,$$

$$V_E = I_E R_E = 20.48 m \times 390 = 8 V,$$

$$V_B = V_E - V_{BE} = 8 - 1.6 = 9.6 V, \text{ (Ans)}$$

$$V_C = V_{CC} = 18 V.$$

From ac equivalent circuit of Fig. 19-6b:

$$Z_b = r_i + \beta_D R_E = 5k + 8000 \times 390 = 3.125 M \Omega,$$

$$Z_i = R_B \parallel Z_b = 3.3M \parallel 3.125M = 1.605 M \Omega,$$

$$Z_o = R_E \parallel r_i \parallel \frac{r_i}{\beta_D} \approx \frac{r_i}{\beta_D} \quad [\text{Derive}]$$


$$\frac{5k}{8000} = 0.625,$$

$$A_i = \frac{\beta_D R_B}{R_B + Z_b} = \frac{8000 \times 390}{3.3M + 3.125} = 4109, \text{ (Ans)}$$

$$A_i = \frac{R_E + \beta_D R_E}{r_i + R_E + \beta_D R_E} = \frac{390 + 8000}{5k + 390 + 8000} = \frac{390}{8490} \approx 0.0998 \approx 1.$$
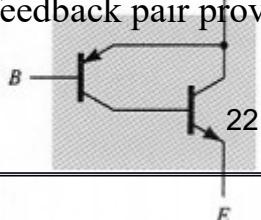
### Feedback Pair Amplifiers:

The feedback pair connection (see Fig. 19-7) is a two-transistor circuit that operates like the Darlington circuit. Notice that the feedback pair uses a *pnp* transistor driving an *npn* transistor, the two devices acting effectively much like one *pnp* transistor. As with a Darlington connection, the feedback pair provides very high current gain (the product



---

of the transistor current gains). A typical application uses a Darlington connection and a feedback pair connection to provide complementary transistor operation.

Fig. 19-7

### Example 19-6:

For the feedback pair connection amplifier circuit shown in Fig. 19-8:

1. Calculate the dc bias currents and voltages to provide  $V_o(\text{dc})$  at one-half the supply voltage.
2. Calculate the ac circuit values of  $Z_i$ ,  $Z_o$ ,  $A_i$ , and  $A_v$ . Assume that  $r_{i1} = 3 \text{ k}\Omega$ .

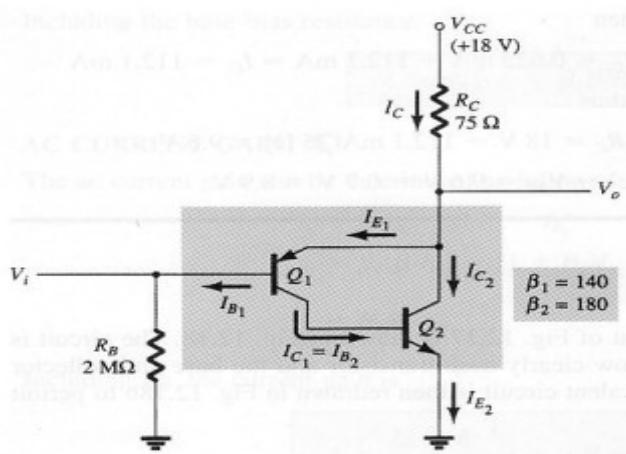


Fig. 19-8

### Solution:

From the  $Q_1$  bias-emitter loop, one obtains

$$V_{CC} - I_C R_C - V_{EB1} - I_{B1} R_B = 0, \quad V_{CC} - \beta_1 \beta_2 I_{B1} R_C - V_{EB1} - I_{B1} R_B = 0 \quad \square$$

$$I_{B1} = \frac{V_{CC} - V_{EB1}}{R_B + \beta_1 \beta_2 R_C} = \frac{18 - 0.7}{2M \cdot 140 \cdot 180 \cdot 75} = 4.45 \mu A.$$

The base  $Q_2$  current is then

$$I_{B2} = I_{C1} = \beta_1 I_{B1} = 140 \cdot 4.45 \mu A = 0.623 mA,$$

resulting in a  $Q_2$  collector current of

$$I_{C2} = \beta_2 I_{B2} = 180 \cdot 0.623 mA = 112.1 mA,$$

and the current through  $R_C$  is then

$$I_C = I_{E1} = I_{C2} = 0.623 \text{ mA} = 112.1 \text{ mA} \approx I_{C2} = 112.1 \text{ mA}.$$

The dc voltage at the output is thus

$$V_o = V_{CC} - I_C R_C = 18 - 112.1 \text{ mA} \cdot 75 \Omega = 9.6 \text{ V},$$

$$\text{And } V_i = V_{EB1} = 9.6 - 0.7 = 8.9 \text{ V}.$$

From the ac equivalent circuits of Fig. 19-9a and b:

$$Z_i \approx R_B \parallel r_{i1} = \beta_1 \beta_2 R_C$$

$$\therefore 2M \parallel \frac{3k}{140 \parallel 180} = 180 \parallel 974 \text{ k}\Omega.$$

$$Z_o = R_C \parallel r_{i1} \parallel r_{i1} \beta_1 \parallel r_{i1} \beta_1 \beta_2 = \frac{r_{i1}}{\beta_1 \beta_2}$$

$$\therefore \frac{3k}{140 \parallel 180} = 0.12 \text{ }\Omega.$$

$$A_v = \frac{\beta_1 \beta_2 R_B}{R_B \parallel Z_i}$$

$$\therefore \frac{140 \parallel 180 \parallel 2M}{2M \parallel 974 \text{ k}} = 16950.$$

$$A_v = \frac{\beta_1 \beta_2 R_C}{\beta_1 \beta_2 R_C \parallel r_{i1}}$$

$$\therefore \frac{140 \parallel 180 \parallel 75}{140 \parallel 180 \parallel 75 \parallel 3k} = 0.9984 \approx 1.$$

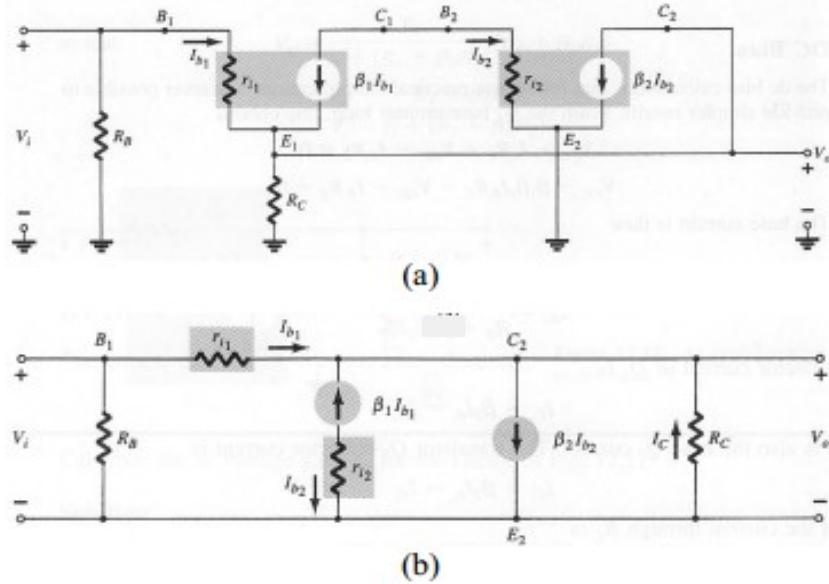


Fig. 19-9

**Exercises:**

1. The transistors in Fig. 19-10 have the following parameter values:  $Q_1$ :  $g_{m1} = 4 \text{ mS}$ ,  $r_{d1} \approx \infty$ , and  $Q_2$ :  $r_{e2} = 30 \Omega$ ,  $r_{o2} \approx \infty$ . Find  $A_{vs}$ .

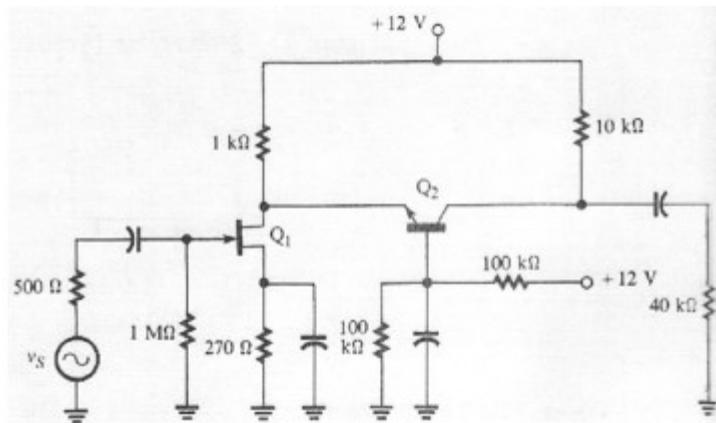


Fig.19-10

2. Fig. 19-11 shows a common-emitter stage driving a Darlington pair connected as an emitter follower. The  $\beta$ -values for the silicon transistors are  $\beta_1 = 200$ ,  $\beta_2 = 100$ , and  $\beta_3 = 100$ . Find  $A_{vs}$ .

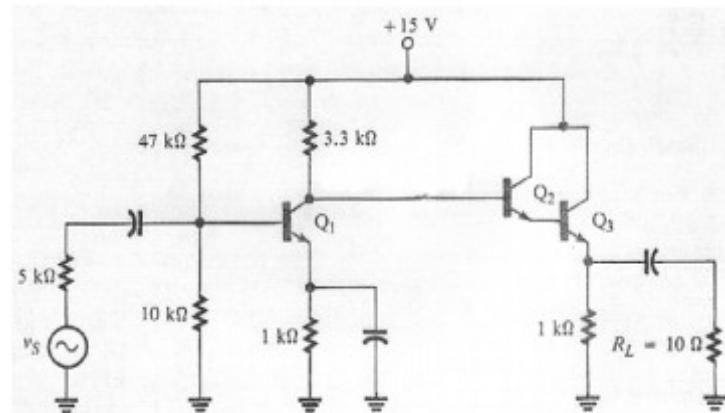


Fig. 19-11