

Diode Switching Circuits

:Basic Concepts

Diode switching circuits typically contain two or more diodes, each of which is connected to an independent voltage source. Understanding the operation of a diode switching circuits depends on determining which diodes, if any, are forward biased and which, if any, are reverse biased. The key to this determination is remembering that **a diode is forward biased only if its anode is positive with respect to its cathode** (see Fig. 2-1). One of the very important applications of diode switching circuits is logic gates .

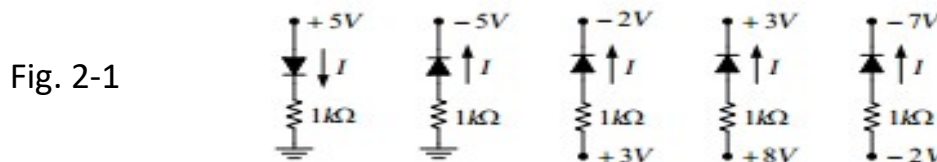



Fig. 2-1

Logic Gates:

Diode can be used to form logic gates, which perform some of logic operations required in digital computers

OR Gate:

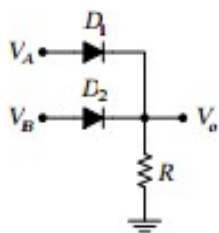It has output when there a signal in any input channels (see Fig. 2-2).




Input voltage		State of diodes		Output voltage
V_A	V_B	D_1	D_2	V_o
0	0	off	off	0
0	1	off	on	1
1	0	on	off	1
1	1	on	on	1

Fig. 2-2

AND Gate:

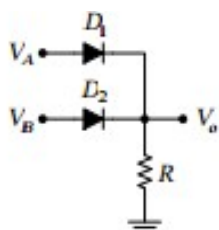It has output only when all inputs are present (see Fig. 2-3).



Input voltage	State of diodes	Output
---------------	-----------------	--------

				voltage
V_A	V_B	D_1	D_2	V_o
0	0	on	on	0
0	1	on	off	0
1	0	off	on	0
1	1	off	off	1

Fig. 2-3

Example 2-1:

Determine which diodes are forward biased and which are reverse biased in the circuit shown in Fig. 2-4. Assuming a 0.7-V drop across each forward-biased diode, determine the output voltage V_o .

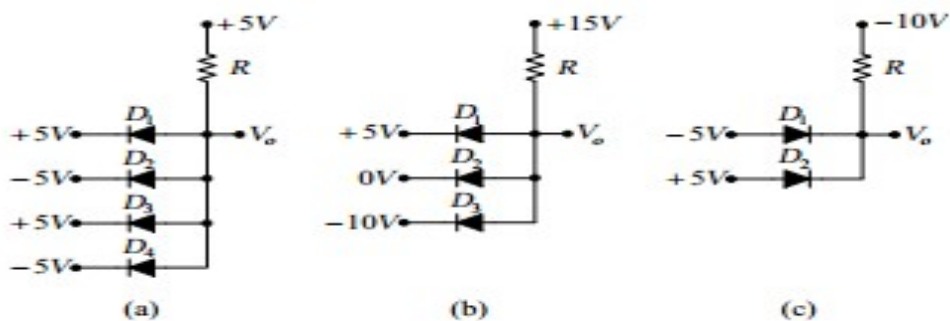


Fig. 2-4

Solution:

In (a) the net forward-biasing voltage between supply and input for each diode is

$$D_1 \circ D_3: 5 - 5 = 0V$$

$$D_2 \circ D_4: 5 - (-5) = 10V$$

Therefore, $D_2 \circ D_4$ are forward biased and $D_1 \circ D_3$ are reverse biased.

$$V_o = -5 - 0.7 = -4.3V.$$

While in (b) the net forward-biasing voltage between supply and input for each diode is

$$D_1: 15 - 5 = 10V,$$

$$D_2: 15 - 0 = 15V,$$

$$D_3: 15 - 10 = 5V.$$

Therefore, D_3 is forward biased and D_1, D_2 are reverse biased.

$$V_o = 10 - 0.7 = 9.3V.$$

Finally, in(c) the net forward-biasing voltage between supply and input for each diode is

$$D_1: -5 - 10 = -15V,$$


$$D_2: 5 - 10 = -5V.$$

Therefore, D_2 is forward biased and D_1 is reverse biased.


$$V_o = 5 - 0.7 = 4.3V.$$

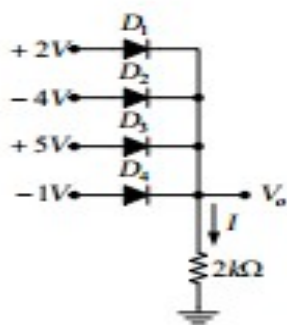Exercises:


Determine V_o and I for each circuit in Fig. 2-5. Assume that each diodes in these circuits has a forward voltage drop of 0.7 v.




(a)

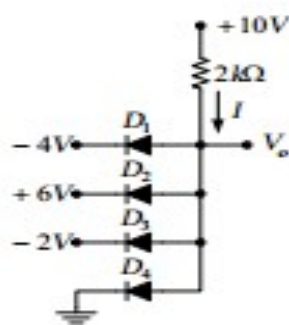

(b)

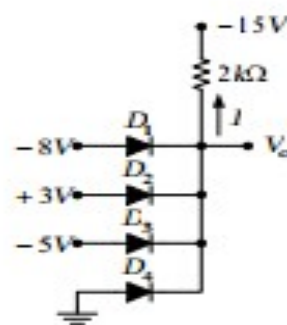


(c)

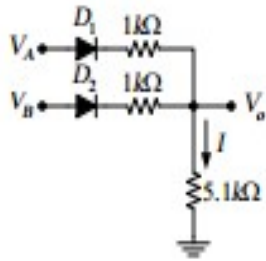

1. $V_A = 0V, V_B = 0V$
2. $V_A = 5V, V_B = 5V$
3. $V_A = 0V, V_B = 5V$

(d)

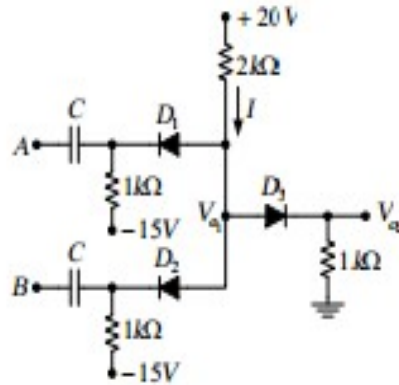

1. No pulses at either A or B
2. A 30V positive pulse at A or B and
3. Positive pulses (30V) at both A and B.

(e)