

Zener Diodes and Applications

Zener Diodes:

Diodes which are designed with plate power-dissipation capabilities to operate in the breakdown region may be employed as voltage-reference or constant-voltage devices. Such are known as *avalanche, breakdown, or zener diodes*. The zener diode is made for operation in the breakdown region. By varying the doping level, a manufacturer can produce zener diodes with breakdown voltages from 2 to 250V.

When the applied reverse voltage reaches the breakdown value, minority carries in the depletion layer are accelerated and reach high enough velocities to dislodge valence electrons from outer orbits. The newly liberated electrons can then gain high enough velocities to free other valence electrons. In this way, we get an avalanche of free electrons. Avalanche occurs for reverse voltages greater than 6V or so.

The zener effect is different. When a diode is heavily doped, the depletion layer is very narrow. Because of this, the electric field across the depletion layer is very intense. When the field strength reaches approximately 3×10^7 V/m, the field is intense enough to pull electrons out of valence orbits. The creation of free electrons in this way is called zener breakdown (also known as high-field emission).

The zener effect is predominant for breakdown voltages less than 4V, the avalanche effect is predominant for breakdown voltages greater than 6V, and both effect are present between 4 and 6V. originally, people thought the zener effect was the only breakdown mechanism in diodes. For this reason, the name "zener diode" came into widespread use before the avalanche effect was discovered. All diodes optimized for operation in the breakdown region are therefore still called zener diodes.

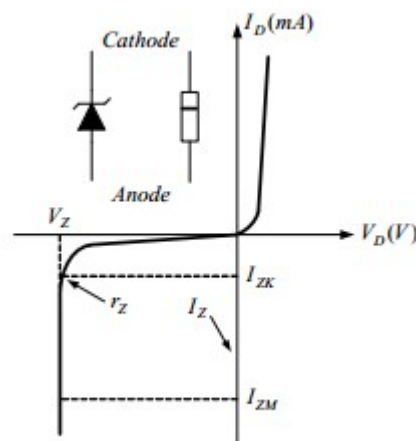


Fig. 7-1

Fig. 7-1 shows the schematic symbol and the current-voltage curve of a zener diode. Negligible reverse current flows until we reach the breakdown voltage V_z . In a zener diode, the breakdown has a very sharp knee, followed by an almost vertical increase in current. Note that the voltage is approximately constant, equal to V_z over most of breakdown region. Data sheets usually the value of V_z at a particular knee current I_{zk} which is beyond the knee (see Fig. 7-1).

The power dissipation of a zener diode equals the product of its voltage and current. In symbols,

$$P_z = V_z \cdot I_z$$

As long as P_z is less than the power rating P_z^{max} , the zener diode will not be

destroyed. Commercially available zener diodes have power ratings from 0.25W to more than 50W. Data sheets often specify the maximum current a zener diode can handle

without exceeding its power rating. This maximum current is designed I_z^{max} (see

Fig.7-1).

The relation between I_z^{max} and power rating is given by

$$I_z^{max} = \frac{P_z^{max}}{V_z}$$

When a zener diode is operating in the breakdown region, a small increase in voltage produces a large increase in current. This implies that a zener diode has a small dynamic resistance (r_z , see Fig. 7-1). We can calculate this zener resistance by

$$r_z = \frac{\Delta v}{\Delta i}$$

The complete equivalent circuit of the zener diode in the zener region includes a small

dynamic resistance r_z and dc battery equal to the zener potential V_z ,

as shown in Fig. 7-2a. for all applications to follow, however, we shall assume as a first approximation that the external resistance are much larger in magnitude than the zener-equivalent resistor and that the equivalent circuit is simply the dc battery that equal to

V_z as indicated in Fig. 7-2b.

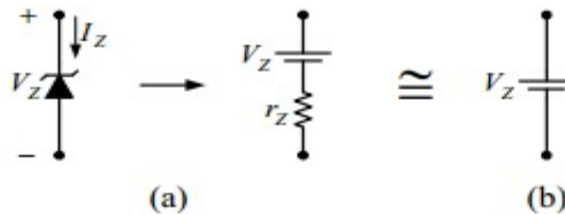


Fig. 7-1

Zener Diode:

these diodes have adequate power dissipation capabilities to operate in the breakdown region. These are used as voltage reference, and constant voltage devices. These are called avalanche, breakdown or zener diodes.

Zener may have breakdown voltage 2 to 200V depending upon level of doping.

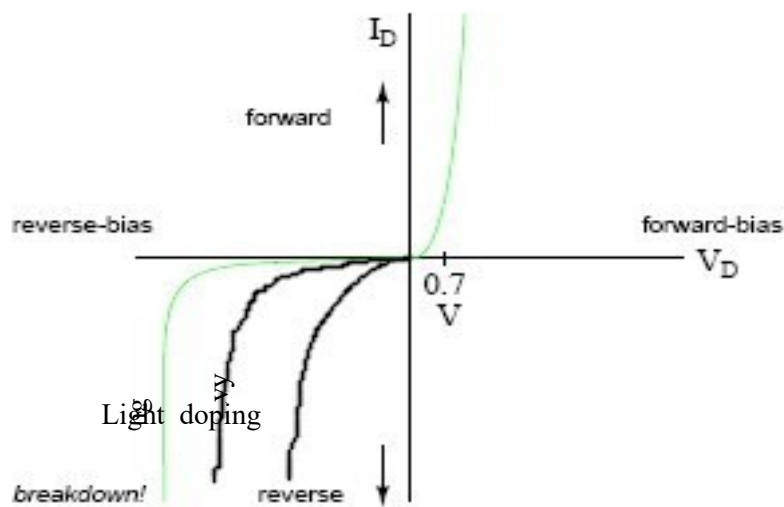


Fig. 7-2: V-I characteristics

Avalanche Breakdown:

When the applied reverse voltage reaches the breakdown value, minority carriers in the depletion layer are accelerated and reach high enough velocity to dislodge valence electrons from outer orbits. These newly liberate electrons further free valence electrons. In this way avalanche of free electrons is obtained. Avalanche occurs for reverse voltage greater than 6V.

Zener Breakdown:

With heavily doping the depletion layer becomes narrow and electric field intensity across the depletion layer is very intense of the order of 300KV/cm, enough to pull electrons out of valence orbits. The free electron creation of this way is called zener breakdown or high field emission.

This effect is prominent for breakdown voltages less than 4V.

Both avalanche and zener effect are present between 4V and 6V.

Zener impedance:

$$Z_z = \frac{\Delta v}{\Delta i} \rightarrow \text{called dynamic impedance}$$

In breakdown region, zener diode has small impedance in voltage produces large change in current. The change in zener voltage with temp.

$$\Delta V_z = T_c \times \Delta T \times V_z$$

Where

T_c : temperature coefficient


ΔT : change in temp.

V_z : zener voltage

Then

$$T_c = \frac{\Delta V_z}{V_z} \times 100 \text{ } ^\circ\text{C}^{-1}$$

Where

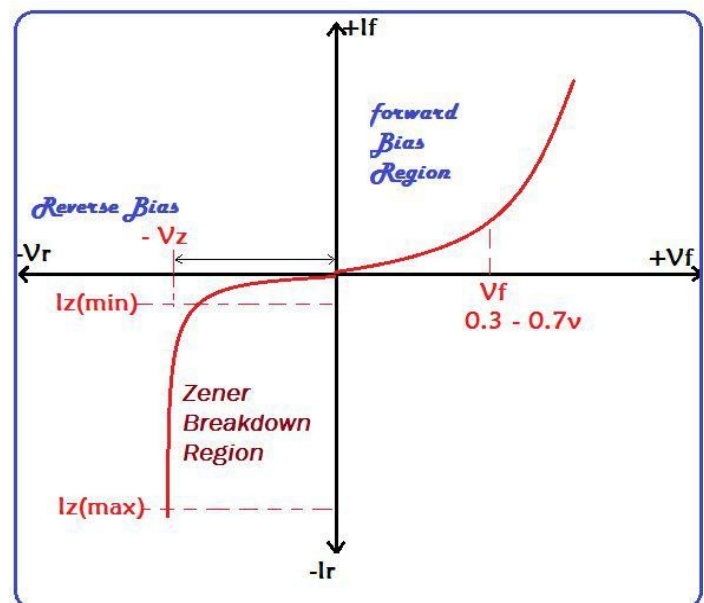

T_1 : is the new temperature level

T_o : is room temperature in an enclosed cabinet ($25 C^\circ$)

Fig. 7-3

T_c : is the temperture coefficient

V_z : is the nominal zener potential at $25 C^\circ$

Example7-1:

Analyze the 10V zener diode if the zener diode if the temperature is increased to $100 C^\circ$ and typical temperature coefficient is $0.072 C^\circ$.

Solution:

$$\Delta V_z = \frac{T_c \times V_z}{100} (T_1 - T_o) = \frac{0.072\% C^\circ \times 10 V}{100} (100 - 25) C^\circ$$

$$\Delta V_z = 0.54 V$$

The resulting potential zener is now

$$V_z = V_z + \Delta V_z = 10.54 V$$

The power dissipation of zener diode $P_z = V_z \cdot I_z$

The maximum current in zener

- max \oplus
- \oplus
- max \oplus
- \oplus
- Z \oplus
- P \oplus
- Z \oplus
- I \oplus

Zener Approximation:


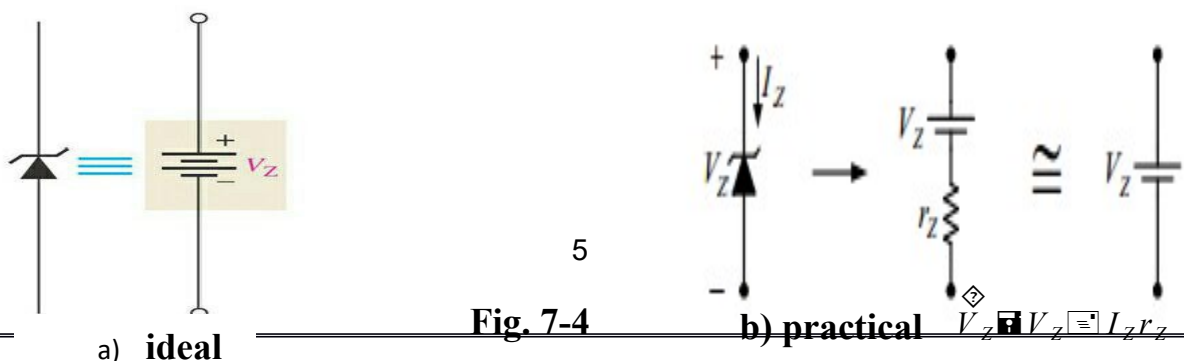
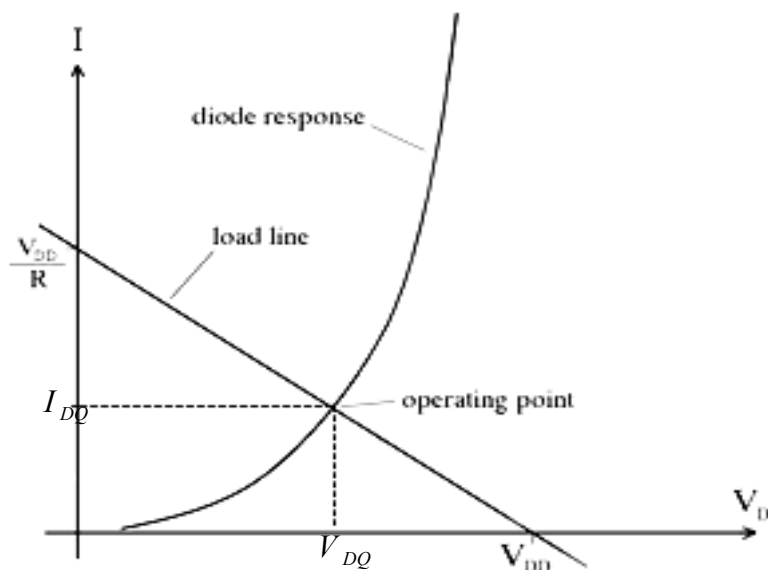


Fig. 7-4

Load-Line Analysis:

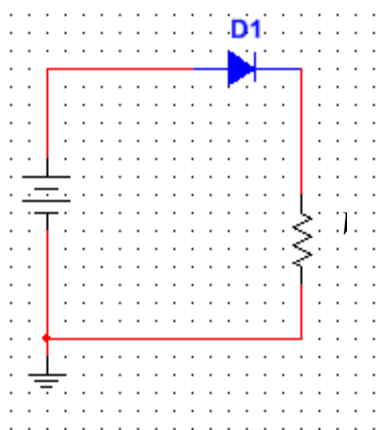



$$E - V_D - V_R = 0 \quad \text{KVL}$$

$$E = V_D + I_D R$$

$$\text{when } V_D \gg 0 \Rightarrow I_D \approx \frac{E}{R} \wedge I_D \approx I_S e^{V_D / \eta V_T - 1}$$

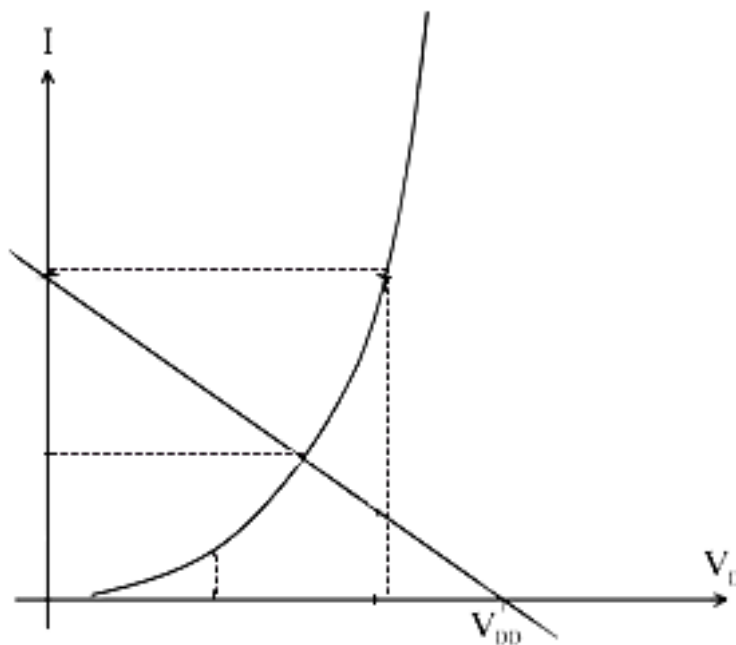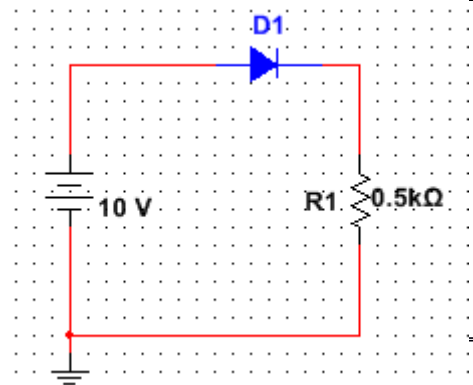Example7-1:

For the series diode configuration e
 Deter



20

18.5mA

a) $I_D = \frac{E}{R}$, at $V_D = 0 \Rightarrow I_D = \frac{10V}{0.5k\Omega} = 20mA$

$V_D = E$ at $I_D = 0 \Rightarrow V_D = 10V$

$V_{DQ} = 0.78V$

$I_{DQ} = 18.5mA$

b) $V_R = I_R R = 18.5mA \cdot 1k\Omega = 18.5V$

0.5 0.8

The DC Zener Regulator:


Equation of load current across load:

$$R = \frac{V - V_Z}{I_L - I_Z}$$

$$I_{Zmin} \leq I_Z \leq I_{Zmax}$$

Q-point is chosen such that

$$I_Z = 20 I_{Zmax}$$

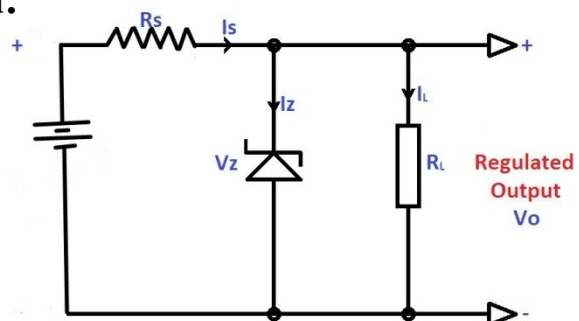

$$\begin{aligned} & \max \\ & Z \\ & I_L \approx 0.2 I \\ \therefore R &= \frac{V - V_Z}{I} \end{aligned}$$

And

$$r_z = \frac{\Delta v}{\Delta i} \quad (\text{ideally } r_z = 0)$$

Fig. 7-5


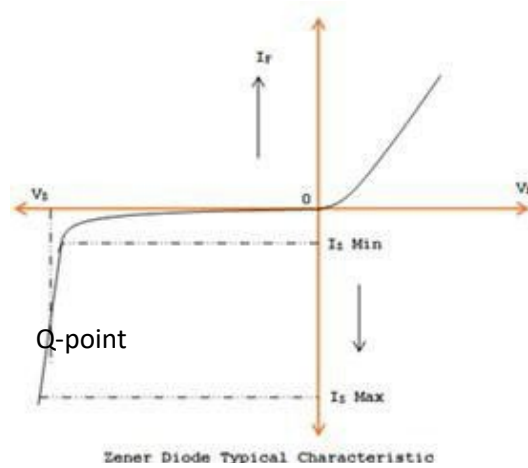
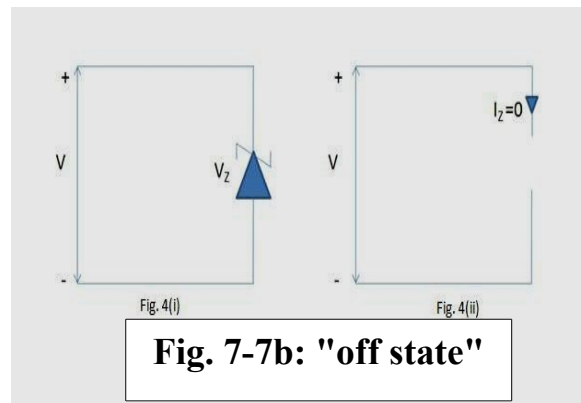


Fig. 7-6

1. V_i, R_L Fixed

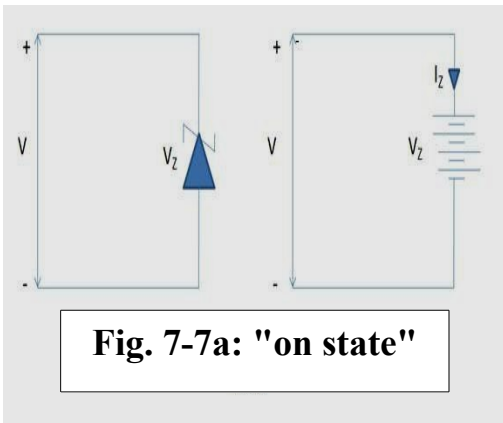

The simplest of Zener diode regulator networks appears in Fig. 7-8 .

The applied dc voltage is fixed, as is the load resistor.

If $V \geq V_Z$ the Zener diode is on.

If, $V < V_Z$ the Zener diode is off.


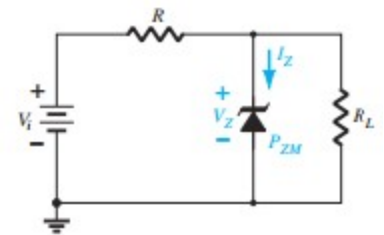


Fig. 7-8

At off state:

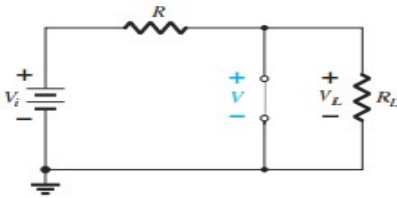

$$V_L = V_Z = \frac{V_i R_L}{R_L + R}$$




At on state:

$$V_L = V_Z$$

$$I_R = I_Z + I_L$$

$$I_Z = I_R - I_L, \quad I_L = \frac{V_L}{R_L} \quad \& \quad I_R = \frac{V_R}{R} = \frac{V_i - V_Z}{R}$$

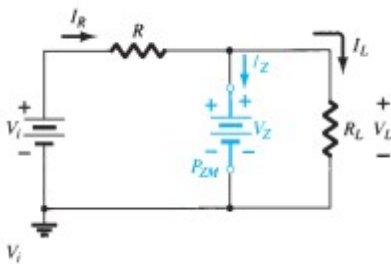

Example 7-2:

- (a) For the Zener diode network of Fig.7-9, determine V_L , V_R , I_Z , and P_Z
- (b) Repeat part (a) with $R_L = 3 \text{ k}$

Solution:

(a)

$$V_L = \frac{V_i R_L}{R_L + R}$$

$$V_L = \frac{16 \text{ V} \times 1.2 \text{ K} \Omega}{1 \text{ k} \Omega + 1.2 \text{ K} \Omega} = 8.73 \text{ V}$$


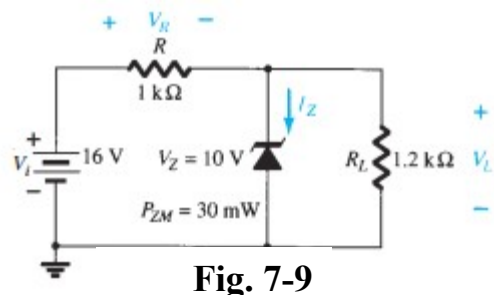


Fig. 7-9

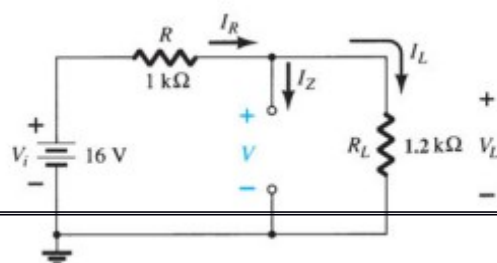

$$V_L = V = 8.73 V$$

$$I_Z = 0$$

$$V_R = V_i - V_L = 16 - 8.73 = 7.27 V$$

$$P_Z = V_Z \cdot I_Z = 0 W$$

(b)

$$V = \frac{V_i R_L}{R_L + R} = \frac{16 \times 3}{1 + 3} = 12 V$$

Since $V = 12V$ is greater than $V_Z = 10$, the diode is in the "on state". Then :

$$V_L = V_Z = 10 V$$


$$V_R = V_i - V_Z = 16 - 10 = 6 V$$

$$I_L = \frac{V_Z}{R_L} = \frac{10}{3} = 3.33 mA$$

$$I_R = \frac{V_R}{R} = \frac{6}{1} = 6 mA$$

$$I_Z = I_R - I_L = 6 mA - 3.33 mA = 2.67 mA$$
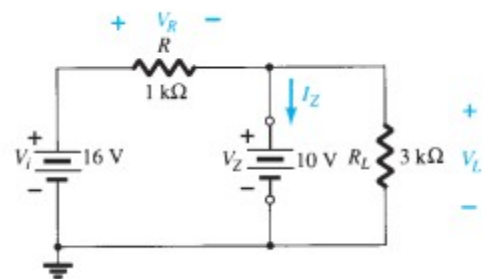
$$P_Z = V_Z \cdot I_Z = 10 \times 2.67 = 26.7 mW$$




2. Fixed V_i , Variable RL

To determine the minimum load resistance of Fig. 7-10 that will turn the Zener diode on, simply calculate the value of R_L that will result in a load voltage

$$V_L = V_Z$$

$$V_L = V_Z = \frac{V_i R_L}{R_L + R}$$

Then

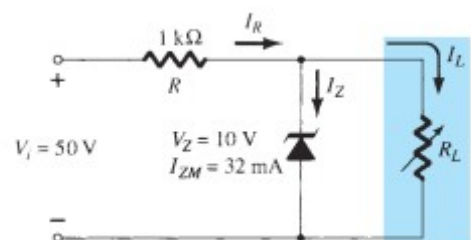

$min \oplus$
 \oplus
 $L \oplus$
 $R \oplus$

Fig. 7-10

Any load resistance value greater than the $\frac{min \oplus}{R \oplus}$ that the Zener diode is in the "on" state and the diode can be replaced by its V_Z source equivalent.

$max \oplus$
 \oplus
 $min \oplus$
 \oplus
 $L \oplus$
 $R \oplus$
 $L \oplus$
 $I \oplus$

The diode is in the "on state & V_R is fixed ($V_R = V_i - V_Z \oplus$) and I_R remains fixed at $I_R = \frac{V_R}{R}$.

Then

$$I_Z = I_R - I_L$$

Minimum I_Z when I_L maximum, I_R constant.

Maximum I_Z when I_L minimum, I_R constant.

$$I_{L \min} = I_R - I_{Z \max}$$

$$R_{L \min} = \frac{V_Z}{I_{L \min}}$$

Example 7-3:

- (a) For the network of Fig. 7-11 , determine the range of R_L and I_L that will result in V_{RL} being maintained at 10 V.
 (b) Determine the maximum wattage rating of the diode.

solution:

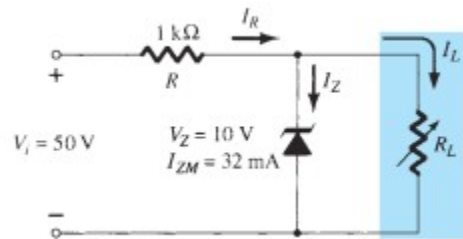


Fig. 7-11

$$a) \quad R_{L \text{ min}} = \frac{V_Z R}{V_i - V_Z} = \frac{10 \times 1}{50 - 10} = 250 \Omega$$

$$V_R = V_i - V_Z = 50 - 10 = 40 V$$

$$I_R = \frac{V_R}{R} = \frac{40}{1} = 40 mA$$

$$I_{L \text{ min}} = I_R - I_{Z \text{ max}} = 40 - 32 = 8 mA$$

$$R_{L \text{ max}} = \frac{V_Z}{I_{L \text{ min}}} = \frac{10}{8} = 1.25 K \Omega$$

A plot of V_L versus R_L appears in Fig.7-12

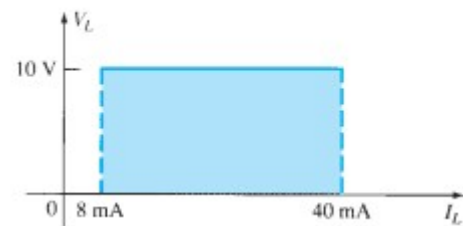
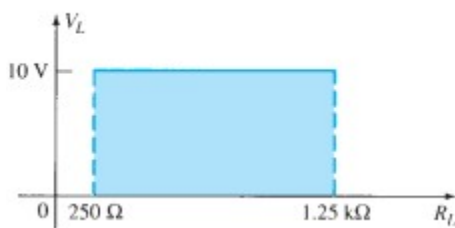


Fig. 7-12

b)

$$P_{Z \text{ max}} = V_Z \cdot I_{Z \text{ max}} = 10 V \times 32 mA = 320 mW$$

3. Fixed R_L , Variable V_i

For fixed values of R_L in Fig. 7-13, the voltage V_i must be sufficiently large to turn the Zener diode on. The minimum turn-on voltage $V_{i \min} = V_Z + I_L R_L$

$$V_L = V_Z + \frac{V_i R_L}{R_L + R}$$

$$V_{i \min} = \frac{R_L + R}{R_L} V_Z$$

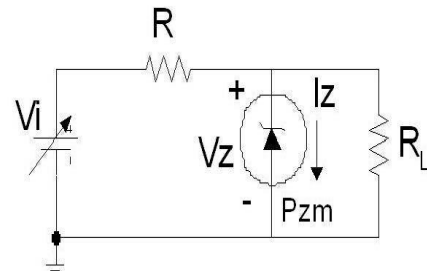


Fig. 7-13

The maximum value of V_i is limited by the maximum Zener current $I_{Z \max}$. Since $I_{Z \max} = I_R - I_L$

$$I_{R \max} = I_{Z \max} + I_L$$

Since I_L is fixed at $\frac{V_Z}{R_L}$ and $I_{Z \max}$ is the maximum value of I_Z , the maximum V_i is defined by:

$$V_{i \max} = I_{R \max} R + V_Z$$

$$V_{i \max} = I_{R \max} * R + V_Z$$

Example 7-4:

Determine the range of values of V_i that will maintain the Zener diode of Fig. 7-14 in the “on” state.

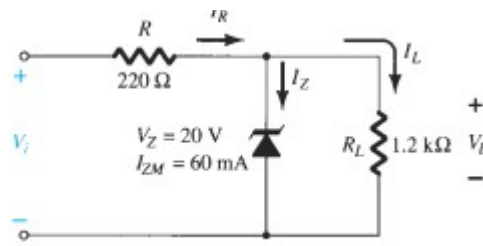


Fig. 7-14

Solution:

$$V_{i \text{ min}} = \frac{R_L + R}{R} V_Z = \frac{1200 \Omega + 220 \Omega}{1200 \Omega} \cdot 20 V = 23.67 V$$

$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{20 V}{1.2 K \Omega} = 16.67 mA$$

$$I_{R \text{ max}} = I_{Z \text{ max}} + I_L = 6 mA + 16.67 mA$$

$$I_{R \text{ max}} = 22.67 mA$$

$$V_{i \text{ max}} = I_{R \text{ max}} R + V_Z$$

$$V_{i \text{ max}} = 22.67 mA \cdot 0.22 K \Omega + 20 V$$

$$V_{i \text{ max}} = 36.87 V$$

A plot of V_L versus V_i is provided in Fig. 7-15 .

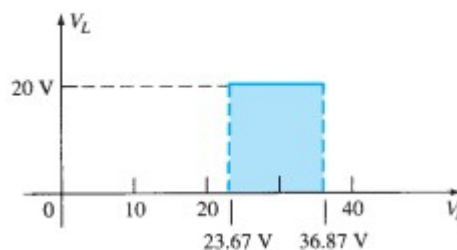


Fig. 7-15

Rectifiers


It has convert ac waveform to dc signal. The process of conversion is called rectification.

Types:

1. Half-Wave Rectifier.
2. Full-Wave Rectifier.
 - a. Full-Wave Bridge Rectifier.
 - b. Center-Tapped Transformer.

Half Wave Rectifier:

It provides rectification for half wave

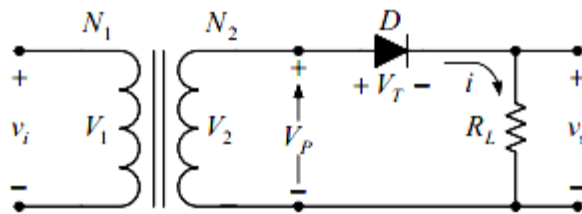

If $V_i \gg V_r$ (diode offset voltage), then linear approximation of diode characteristics is used.

$$V_i \approx V_m \sin \omega t \approx V_m \sin \alpha$$

$$i \approx I_m \sin \omega t \approx I_m \sin \alpha$$

$$i \approx I_m \sin \alpha, \text{ when } 0 \leq \alpha \leq \pi$$

$$i \approx 0, \text{ when } \pi \leq \alpha \leq 2\pi$$


$$I_m \approx \frac{V_m}{R_f + R_L}$$

$$I_{dc} \approx \text{average value}$$

=area under the curve

=average current passing through R_L
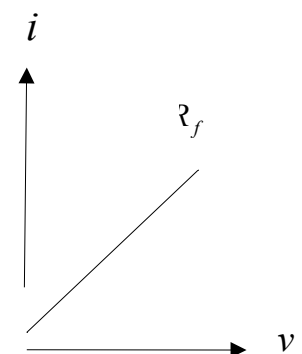
$$P_o \approx \text{average output power}$$



$$P_o = V_{dc} \cdot \frac{I_m}{\pi} R_L = \frac{I_m^2}{\pi^2} R_L$$

Efficiency of rectification

$$\eta = \frac{P_o}{P_i} = \frac{\frac{I_m^2}{\pi^2} R_L}{\frac{I_m^2}{2} R_L} = \frac{2}{\pi^2} \approx 40.6\%$$


$$\eta = \frac{P_o}{P_i} = \frac{\frac{I_m^2}{\pi^2} R_L}{\frac{I_m^2}{2} R_L} = \frac{2}{\pi^2}$$

For $R_L \gg R_f \Rightarrow R_f \approx 0, \eta = \frac{4}{\pi^2} \Rightarrow \eta_{percent} = \frac{4}{\pi^2} \times 100 \approx 40.6$

Peak inverse voltage (PIV):

For every diode, there is a maximum voltage to which it can be subjected. It called peak inverse voltage (PIV).

$$PIV \geq V_m$$

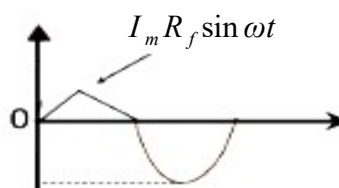

Regulation:

The regulator is defined in percentage.

$$\text{Regulation} = \frac{V_{No\ load} - V_{Full\ load}}{V_{Full\ load}} \times 100$$

- At no load $V_{dc} = \frac{V_m}{\pi}$.

- At full load $V_{dc} = I_{dc} \cdot R_f + \frac{V_m}{\pi} - I_{dc} \cdot R_f$

Example 7-5 :

Find the regulation for the following circuit $V_{No\ load} = 12\text{ V}$.

Solution:

$$V_{Full\ load} = 12 - 0.1 \cdot 20$$

$$= V_{dc} - I_{dc} \cdot R_f$$

$$= 12 - 2$$

$$= 10\text{V}$$

$$\%Reg = \frac{12 - 10}{10} \times 100 = 20$$

Ripple factor (r) :

It is a measure of fluctu ability component (ac component) and is defined as:

$$r = \frac{\text{rms value of ac wave}}{\text{average value of wave}} = \frac{I_{rms}}{I_{dc}} = \frac{V_{rms}}{V_{dc}}$$

Where I_{rms} and V_{rms} denote the rms value of ac component in current and voltage respectively.

$$i - I_{dc}$$

$$\frac{1}{2\pi} \int_0^{2\pi} (i - I_{dc})^2 d\alpha$$

$$= \frac{1}{2\pi} \int_0^{2\pi} (I_m \sin \alpha - I_{dc})^2 d\alpha$$

$$= \frac{1}{2\pi} \int_0^{2\pi} (I_m^2 \sin^2 \alpha - 2I_m I_{dc} \sin \alpha + I_{dc}^2) d\alpha$$

$$= \frac{1}{2\pi} \left[I_m^2 \int_0^{2\pi} \sin^2 \alpha d\alpha - 2I_m I_{dc} \int_0^{2\pi} \sin \alpha d\alpha + I_{dc}^2 \int_0^{2\pi} 1 d\alpha \right]$$

$$= \frac{1}{2\pi} \left[I_m^2 \pi - 0 + I_{dc}^2 2\pi \right]$$

$$= \frac{1}{2} I_m^2 - I_{dc}^2$$

$$\therefore r = \sqrt{\frac{I_m^2}{I_{dc}^2} - 1}$$

For half wave rectifier (HWR)

$$\frac{I_{rms}}{I_{dc}} = \frac{I_m \sqrt{2}}{I_m \pi} = 1.57$$

$$\therefore r = \sqrt{1.57^2 - 1} = 1.21$$

The result indicates that the rms ripple factor voltage exceeds the dc output voltage in HWR. It is poor circuit for converting ac to dc


Note:

- min
- L
- R

$$V_R \neq 0 \Rightarrow V_{NL} - V_{FL} \approx 0$$

Full Wave Rectifier (FWR):

With center-tap transformer

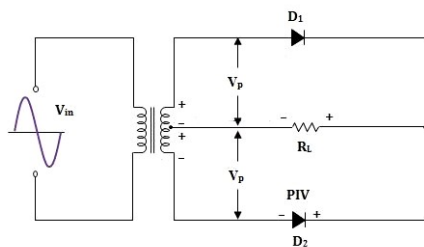

$$I_{dc} = \frac{2I_m}{\pi}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$





$$V_{dc} = \frac{2I_m}{\pi} \cdot R_L = I_{dc} \cdot R_L$$

$$P_o = I_{dc}^2 \cdot R_L = \left(\frac{2I_m}{\pi}\right)^2 \cdot R_L$$

$$P_i = I_{rms}^2 \cdot (R_f + R_L)$$

$$\eta = \frac{P_o}{P_i} = 81.2\% \quad \text{twice that for HWR}$$

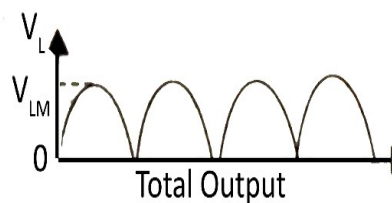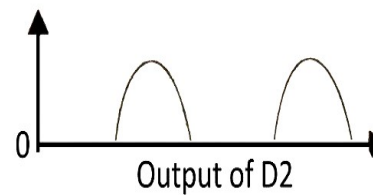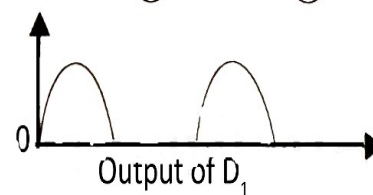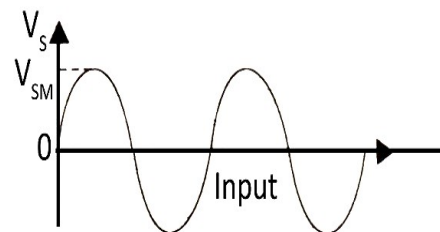Current ratio $\left(\frac{I_{dc}}{I_{rms}}\right)$



single-phase center-tap output wave

$$\frac{I_{rms}}{I_{dc}} = \frac{I_m \sqrt{2}}{2 I_m \pi} = 1.11$$

Ripple factor $r = \sqrt{1.11^2 - 1} = 0.482$


So ripple factor has dropped from 1.21 in HWR to 0.482 in FWR.

PIV for FWR

As it is clear from the circuit that when diode is conducting, the voltage across the other is $2V_m$, $PIV \geq 2V_m$.

FWR with two diodes needs a center tapped transformer.

Bridge Rectifier (Full-Wave):

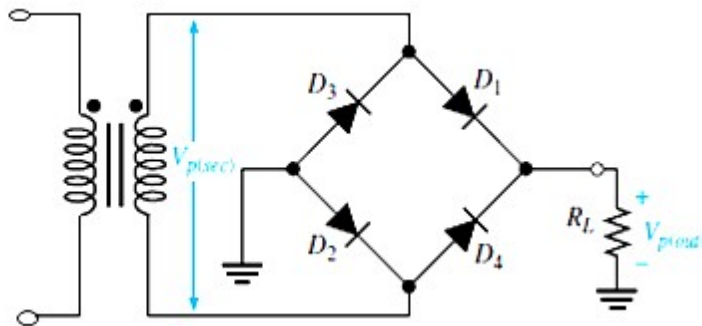

$$V_D = \frac{2V_P}{\pi}$$

$$f_{out} = 2f$$

$$PIV = V$$

Advantages:

- 1- It needs no center tapped transformer.
- 2- All four diodes are mounted on a single package.
- 3- $PIV \geq 2V_m$ for each diode.
- 4- This circuit is very commonly used.

Operation:

- For positive half, D_1 & D_3 conduct
- For negative half, D_2 & D_4 conduct

Current in R_L is in the same direction during both positive and negative half cycles.



$$I_{dc} = \frac{2I_m}{\pi}$$

$$V_{dc} = \frac{2V_m}{\pi} = 0.636V_m$$




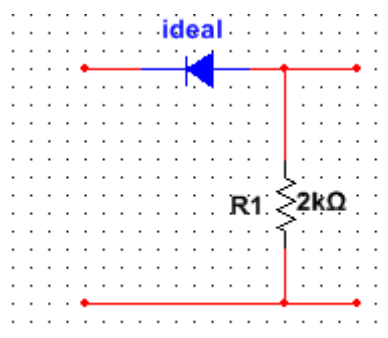
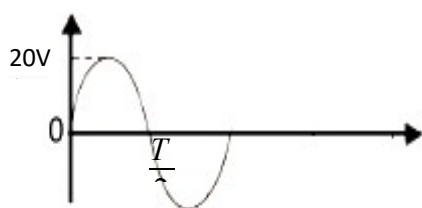
Example 7-6:

- a- Sketch the output V_o and determine the dc level of the output for the network of Fig.
- b- Repeat part(a) if the diode is replaced by a silicon diode.




Solution:

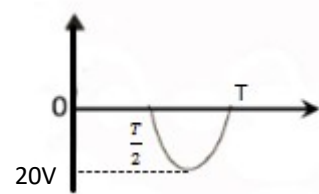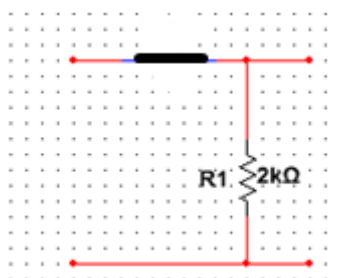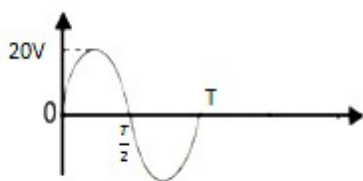a- $V_{dc} = \frac{I_m R_L}{\pi} = 0.318 V_m = 0.318 \times 20 = 6.36 V$




b- $V_{dc} = \frac{I_m R_L}{\pi} = 0.318 V_m = 0.318 \times 19.3 = 6.14 V$
 $V_{dc} = 0.318 V$

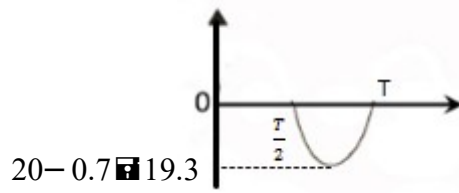

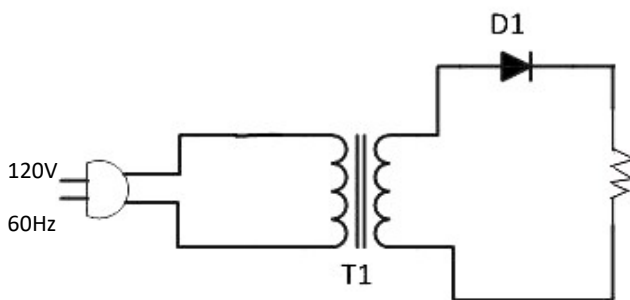Example7-7:

For the circuit shown below find V_{dc} & PIV.



Solution:

$$V_p = \sqrt{2} V_{rms} = \sqrt{2} \times 120 = 170 V$$



$$V_m = \frac{N_1}{N_2} V_p = \frac{1}{4} * 170 = 42.5 V$$

$$V_{dc} = \frac{V_m}{\pi} = \frac{42.5}{\pi} = 13.5 V$$




$$PIV = V_m = 42.5 V$$

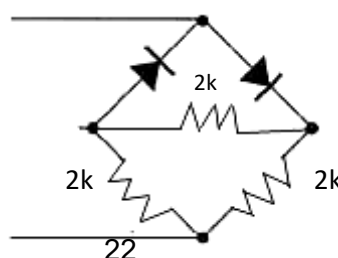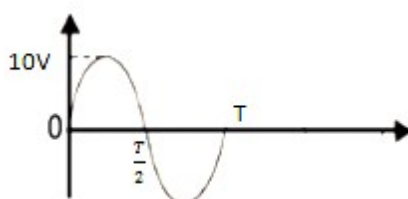Example 7-8:

Determine the output waveform for the network of Fig.7- . and calculate the output dc level and the required PIV of each ideal diode.





Solution:

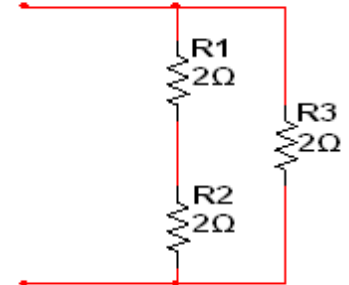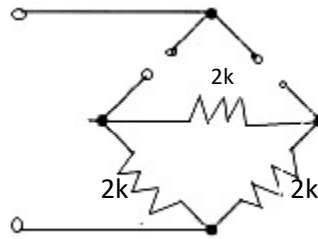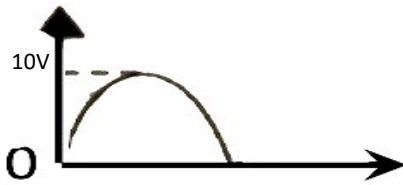

- max ⊕
- ⊕
- max ⊕
- ⊕
- i ⊕
- ⊕
- o ⊕
- ⊕
- V ⊕


$$V_{dc} = \frac{2V_m}{\pi} = \frac{2 \times 10}{\pi} = 0.636 \times 10 = 6.36 \text{ V}$$

$$PIV = V_o = 10 \text{ V}$$

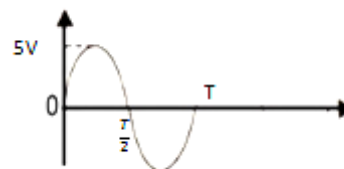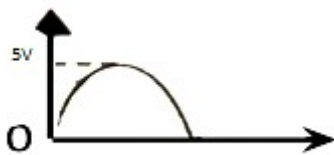


Home Work:

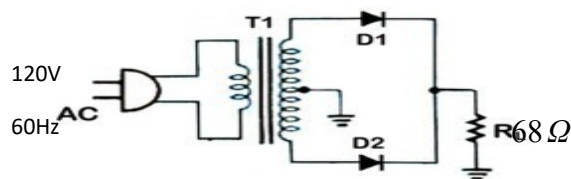1-For the circuit shown in Fig. . find V_{dc} ,PIV.



2- a- For the circuit shown in Fig. ,find V_{dc} , f_o , PIV

b-Repeat part (a) if the ideal diodes is replaced by silicon diodes.

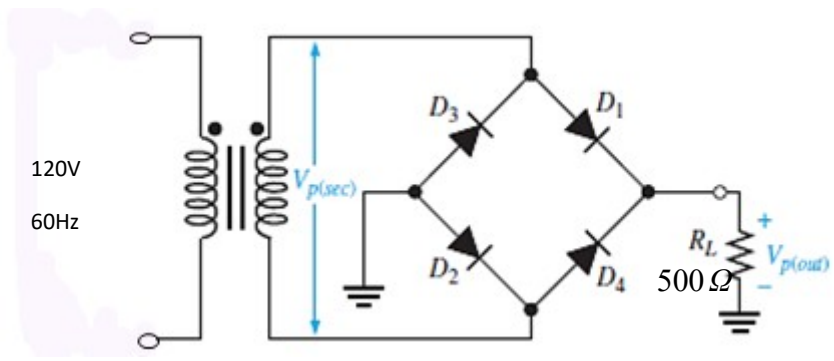


Example 7-9:

For the power supply shown in Fig. $I_{FL} = 0.5 A$. find voltage regulation and minimum load resistance.

Solution:

$$V_R = \frac{30 - 20}{20} \times 100 = 50$$


- min ⊕
- ⊕
- L ⊕
- R ⊕

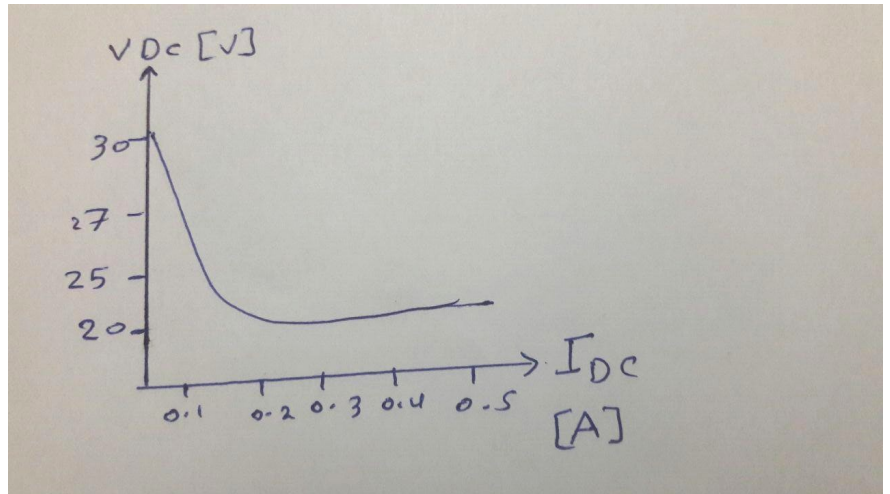


Home work:

For the following figure. Find V_R , R_L , L , R

- min ⊕
- ⊕
- L ⊕
- V_R ⊕ R ⊕

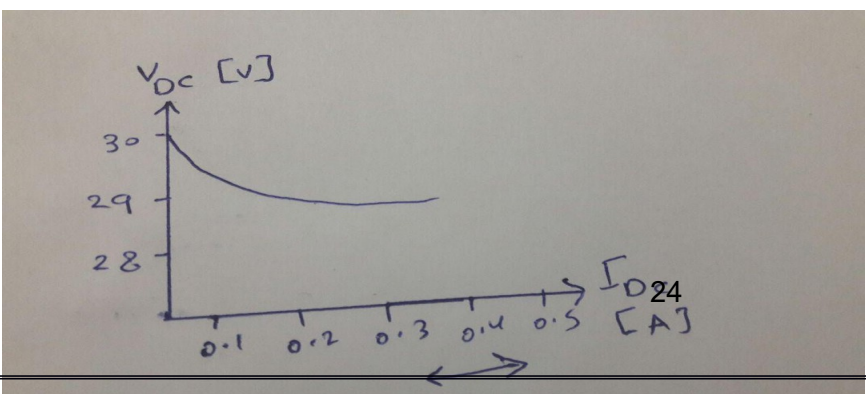

Zener Regulator:

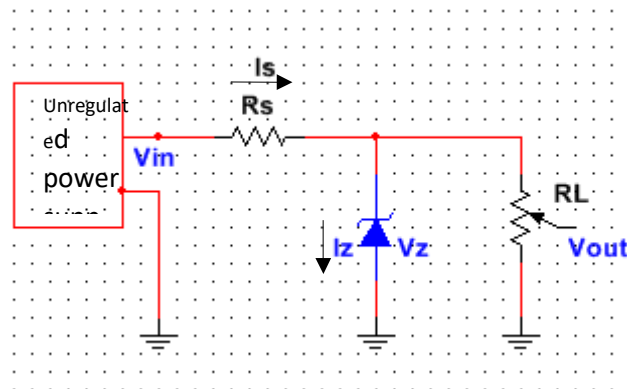

$$V_o \approx V_Z \pm I_Z \cdot Z_Z$$

max ⊕

⊕

min ⊕

⊕

- V_o

⊕

max ⊕

⊕

L ⊕

i ⊕

V_s ⊕

s ⊕

R_s ⊕

max ⊕

⊕

s ⊕

R_s ⊕

R_s : limited resistance

$$I_s \approx \frac{V_i - V_o}{R_s}$$

$$I_Z \approx I_s - I_L$$

$$V_o = V_Z$$


$$I_L = \frac{V_o}{R_L}$$

Open CCT. $I_Z = 0, I_S = I_L = I$

Example 7-10:

For the following circuit . find minimum and maximum current &

- max
- min
- Z
- Z
- I

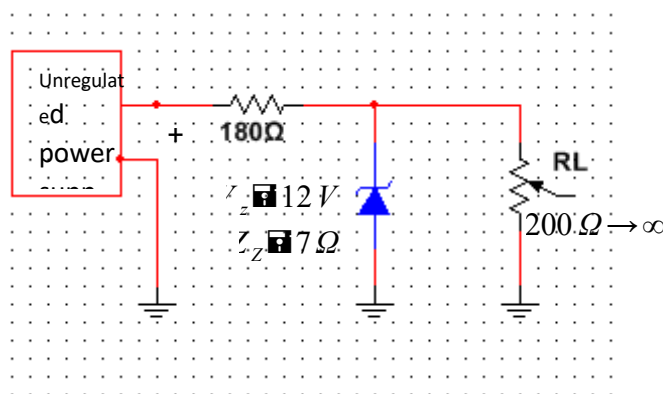

Solution:

$$I_s = \frac{V_i - V_o}{R_s} = \frac{25 - 12}{180} = 72 \text{ mA}$$

min ⊕
 ⊕
 L ⊕
 I ⊕

max ⊕
 ⊕
 L ⊕
 I ⊕

Where is V_o , I_s constant

min ⊕
 ⊕
 Z ⊕
 I ⊕

max ⊕
 ⊕
 Z ⊕
 I ⊕

Home work:

Zener regulator have input voltage vary from 15V to 20V and load current vary from 20mA to 100mA. Find the limited resistor to be connected in series if the voltage $V_z = 10 \text{ V}$.

Zener Diode Application:

1. AC Voltage Regulator [Limiters or Clippers]:

Two back-to-back zeners can be used as an as regulator or a simple square-wave generator as shown in Examples 7-1 and 7-2 respectively.

Example 7-1:

Sinusoidal ac regulator, see Fig. 70-3.

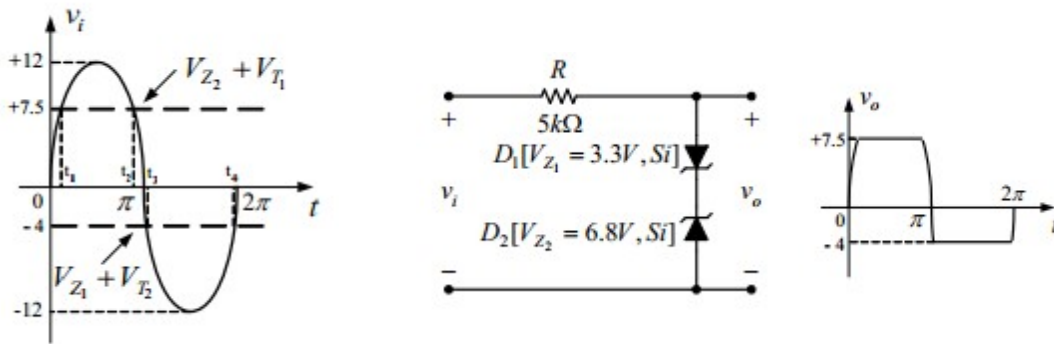


Fig. 7-1

For $t \in [0 \rightarrow t_1] \quad t_2 \rightarrow \pi : D_1 \text{ ON} \quad D_2 \text{ OFF} \Rightarrow V_o = V_i$.

For $t \in [t_1 \rightarrow t_2] ; D_1 \text{ ON} \quad D_2 \text{ breakdown} \Rightarrow V_o = V_{Z2} \approx V_{T1}$.

For $t \in [\pi \rightarrow t_3] \quad t_4 \rightarrow 2\pi ; D_2 \text{ ON} \quad D_1 \text{ OFF} \Rightarrow V_o = V_i$.

For $t \in [t_3 \rightarrow t_4] ; D_2 \text{ ON} \quad D_1 \text{ breakdown} \Rightarrow V_o = V_{Z1} \approx V_{T2}$.

Example 7-2:

Simple square-wave generator, see Fig. 7-4.

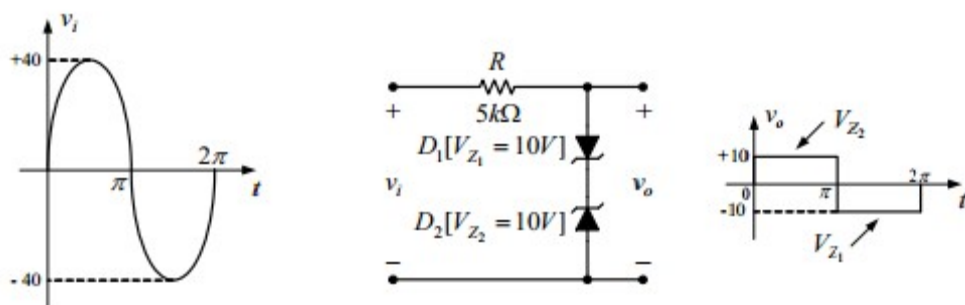


Fig. 7-4

2. DC Voltage Reference:

Two or more reference levels can be established by placing zener diodes in series as shown in Fig. 7-5. As long as V_i is greater than the sum of $V_{z1} + V_{z2}$, both diodes will be in the breakdown state and the three reference voltages will be available.

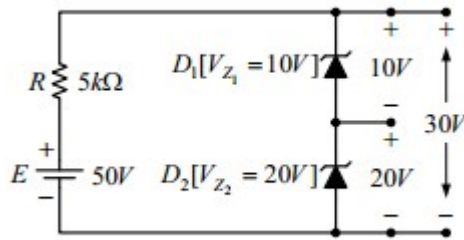


Fig. 7-5

3. DC Voltage Regulators:

a. Fixed R_L , Variable V_i :

For the regulator circuit shown in Fig.7-6;

$$I_L \frac{V_Z}{R_L} \text{ constant } \textcircled{7-2a}$$

min ⊕
 ⊕
 s ⊕
 I ⊕
 min ⊕
 ⊕
 min ⊕
 ⊕
 s ⊕
 i ⊕
 V ⊕

⦿7-2b⦿

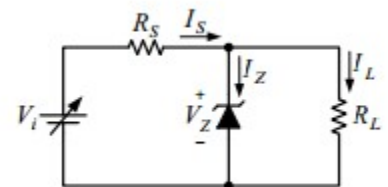


Fig. 7-6

max \oplus
 \oplus
 s \oplus
 I \oplus

$7 - 2c$ \otimes

max \oplus
 \oplus
 max \oplus
 \oplus
 s \oplus
 i \oplus
 V \oplus


b. Fixed V_i , Variable R_L :

For the regulator circuit shown in Fig. 7-7;

$$I_s \uparrow \frac{V_i - V_Z}{R_S} \uparrow \text{constant} \downarrow$$

$$\begin{matrix} \text{min} \uparrow \\ L \uparrow \\ I \uparrow \end{matrix}$$
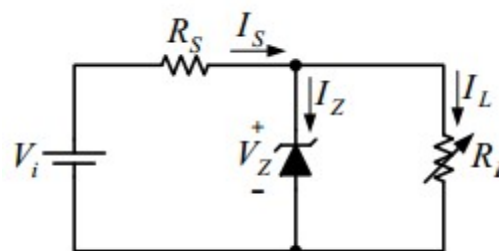
$$\begin{matrix} \text{min} \uparrow \\ L \uparrow \\ I \uparrow \\ L \uparrow \text{max} \downarrow \frac{V_Z}{R} \uparrow \end{matrix}$$



$$\begin{matrix} \text{max} \uparrow \frac{I_s - I_{ZK}}{L} \uparrow \\ I \uparrow \\ \text{max} \uparrow \\ R_{L \text{ min}} \uparrow \frac{V_Z}{L} \uparrow \\ I \uparrow \\ \frac{V_Z}{L} \uparrow \end{matrix}$$

c. Variable V_i and R_L :

For the regulator circuit shown in Fig.7- ;



$min \oplus$
 \oplus
 $max \oplus$
 $L \oplus$
 $s \oplus$
 $I_{ZK} \boxtimes I \oplus$


$min \oplus$
 \oplus
 $min \oplus$
 \oplus
 $-V_Z$
 $i \oplus$
 $V \oplus$
 $s \oplus$
 $I \oplus$

$max \oplus$
 \oplus
 $L \oplus$
 $I \oplus$

$max \oplus$
 \oplus
 $min \oplus$
 $L \oplus$
 $s \oplus$
 $I_{ZM} \boxtimes I \oplus$

$max \oplus$
 \oplus
 $max \oplus$
 \oplus
 $-V_Z$
 $i \oplus$
 $V \oplus$
 $s \oplus$
 $I \oplus$


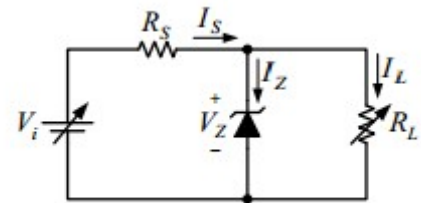
$min \oplus$
 \oplus
 $L \oplus$
 $I \oplus$



Tunnel Diode:

A p-n junction diode has an impurity concentration of about 1 part in 10^8 , where the depletion layer width is of the order of 5micros (5×10^{-4} cm).

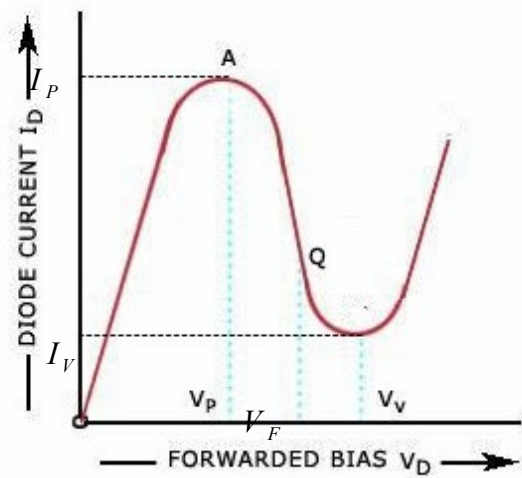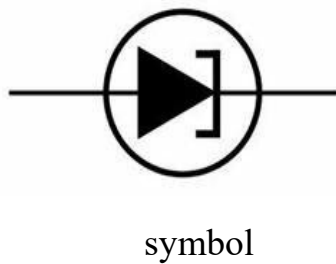If the connection of impurity atoms is greatly increased, say 1 part in 10^3 , the device characteristics are completely changed as shown in Fig.7-. This kind of diode is called Tunnel diode



V-I characteristic

I_V – valley current

V_V – valley voltage

V_F – peak forward voltage

I_P – peak forward voltage

V_P – voltage of I_P

At this point

$$\frac{dI}{dV} = 0$$


After V_P $\frac{dI}{dV}$ is negative

$0 \oplus V_P \rightarrow$ controlled by zener breakdown.

$V_P \oplus V_V \rightarrow$ tunneling phenomenon.

$V_V \oplus V_P \rightarrow$ normal operation of p- n junction diode.

Equivalent circuit:

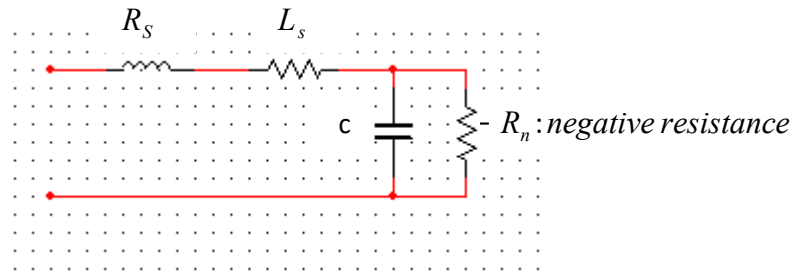

R_s : series ohmic resistance .

L_s : series inductance.

C : junction capacitance.

$-R_n$: has a minimum at the point of inflection between I_P and V_V .

Typical values at $I_P \approx 10 \text{ mA}$, $L_s \approx 5 \text{ nH}$, $-R_n \approx -30 \Omega$, $c \approx 20 \text{ PF}$, $R_s \approx 1 \Omega$.

Applications:

- 1- Negative resistance device.
- 2- High speed switch in logic circuit.
- 3- Low voltage rectifiers at reverse bias.
- 4- High frequency (micro wave) oscillator.

Advantage:

- 1- Low cost.
- 2- Low noise.
- 3- Simplicity
- 4- High speed.
- 5- Environmental immunity.
- 6- Low power.

Disadvantages:

- 1- Low output voltage swing.
- 2- No isolation between input and output.

Notes:

I_P : determined by impurity concentration (the resistivity) & the junction area.

V_P, I_P not very temp sensitive.

Tunnel diode – excellent conductor in reverse direction.

	Ge	GaAs	si
I_P, V_P	8	15	3.5
V_P, V	0.055	0.15	0.065
V_V, V	0.35	0.50	0.42
V_F, V	0.50	1.10	0.70

Typical tunnel diodes parameter.


Photo Electric Semiconductor Diode:

Light sensors (photo diode)

$$I = I_s \left(1 - e^{-\frac{V}{V_T}} \right)$$

I_o : reverse saturation current.

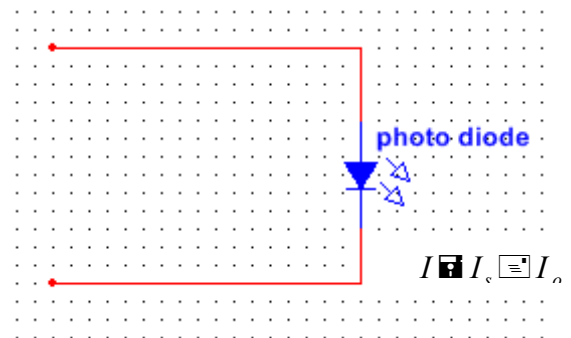
I_S : short circuit current and is proportional to light intensity.



- It is a light sensitive diode.
- Light controls the operation of diode.
- It convert light into electric current.
- When light (photons) strike the semiconductor material, electrons and holes are generated.


E: light illumination unit in foot-candle

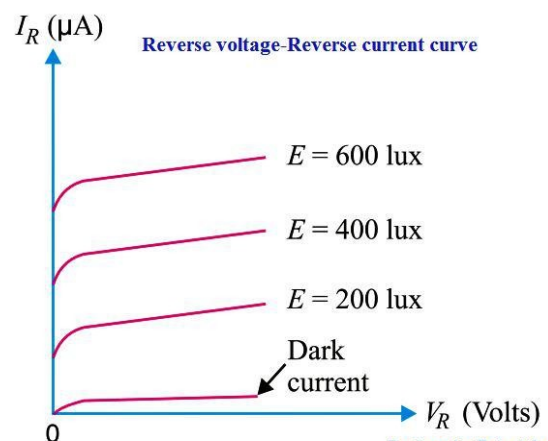- Curve except for dark current do not pass through the origin
- Slope of curves for voltage greater then few volts corresponding to dynamic




resistance of the order of few $\mu\Omega$ to
 hundreds of $\mu\Omega$.

Circuit Model:

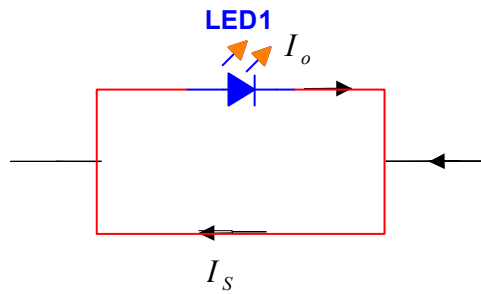


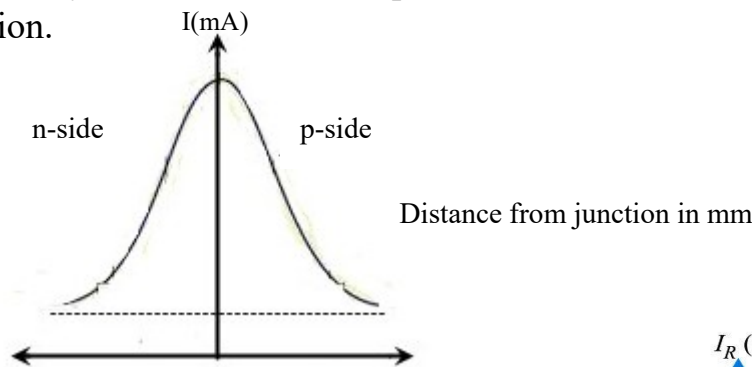(sensitivity of a semiconductor photodiode as a function of a the light spot from the junction.



Specification of a typical photo diode.

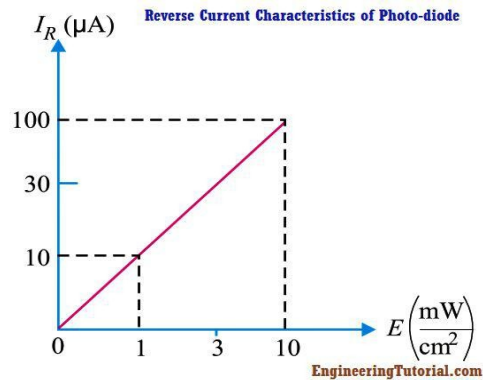- Dark current = $2 \mu A$.
 - Temp coefficient , I_o double every $10^\circ C$.
 - Small size (tenth of an inch).
 - Characteristic of drift with age.
 - Frequency response $\oplus 1 \mu Hz$.
- $I_R \propto mE$, m=slope.




Application:

1- Speed control of a very small motor.

$I \propto f \propto \text{light} , V \text{ constant}$, if V is constant.

$I \propto f \propto \text{photo light}$

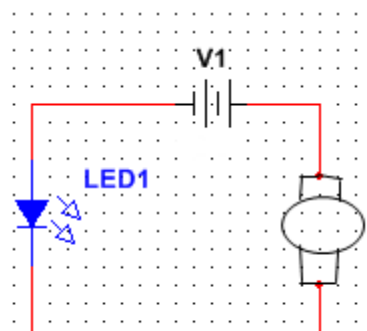

M

2- Photo diode as a control element .
 R is for sensitivity adjustment


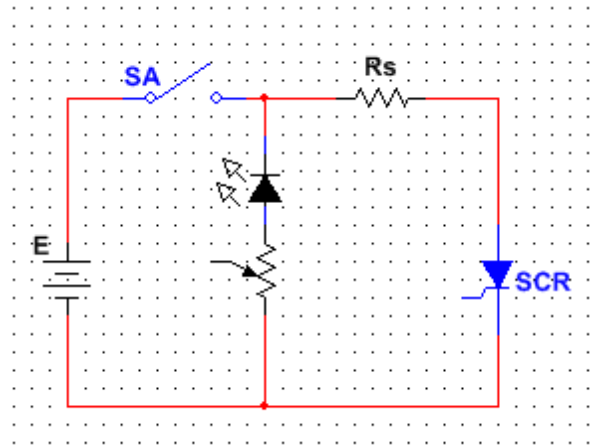



Photo diode:

Is a reverse-biased silicon or germanium pn junction in which reverse current increase when the junction is exposed to light.


Shottky Diodes:

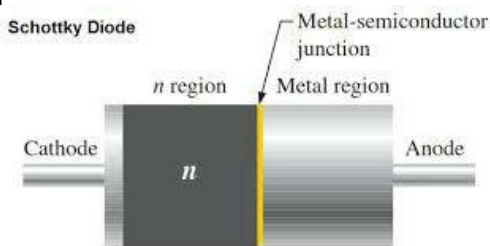

schottky

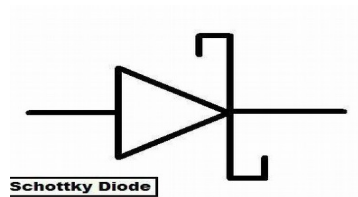


symbol

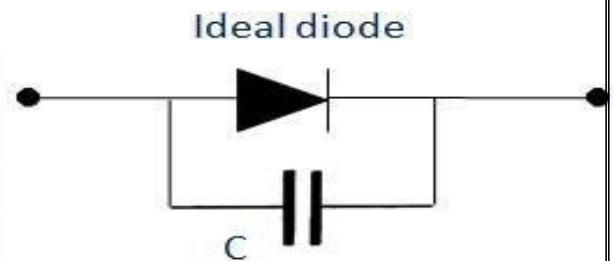

Approximate equivalent circuit

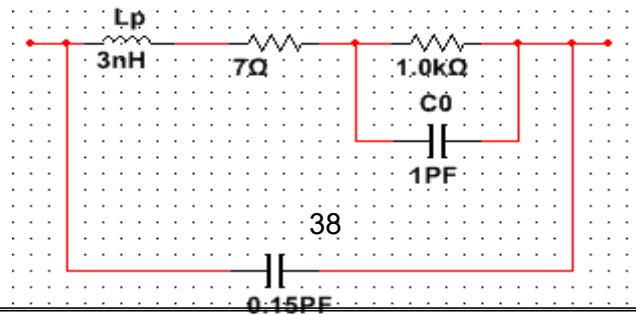- This metal is cold or silver or platinum
- The equivalent circuit for the schottky diode with typical values appear in by below.




- Schottky diodes are effective at frequency approaching 20GHz.

Applications:

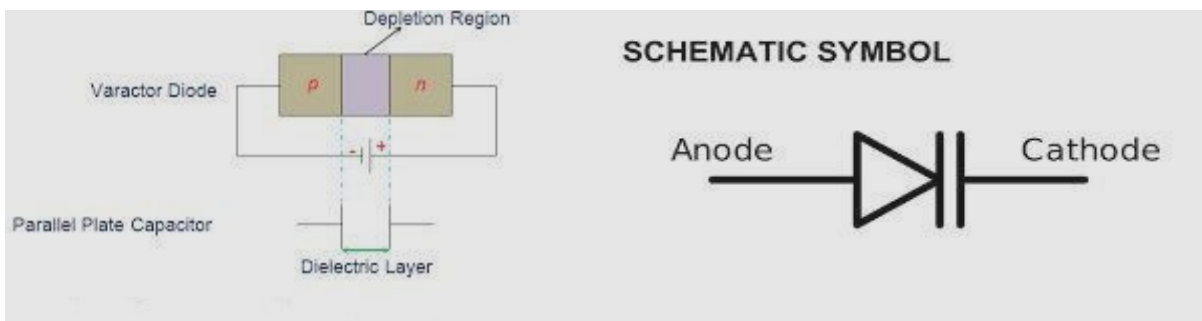1. Digital electronics
2. Integral circuit (TTL schottky)

Varactor Diode:

A junction diode which acts as variable capacitor under changing reverse bias is known as a varactor diode .



For normal operation a varactor diode is always reverse biased. The capacitance of varactor diode is found as ,

$$C_T = \epsilon \frac{A}{W_d}$$

Where :


C_T : total capacitance of the junction .

ϵ : permittivity of the semiconductor material .

A : cross-sectional area of the junction.


W_d : width of the depletion layer.

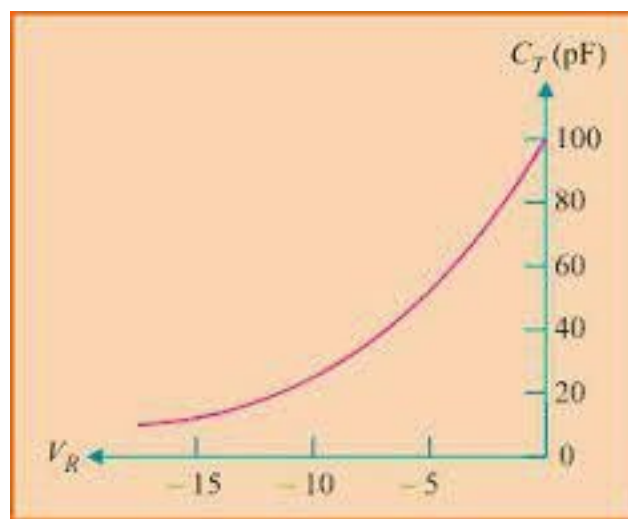When reverse voltage across a varactor diode is increased, the width W_d of the depletion layer increases. Therefore, the total junction capacitance C_T of the junction decreases.



Application of Varactor Diode:

For normal operation, a varactor diode is always operated under reverse bias. In fact this condition is met in the circuit shown. The resistance R_w in the circuit is the winding resistance of the inductor. This winding resistance is in series with the potentiometer R_1 . The R_1 and R_w form a voltage divider that is used to determine the amount of reverse bias across the varactor diode D_1 and therefore its capacitance. By adjusting the setting of R_1 we can vary the diode capacitance. This in turn varies the resonant frequency of the LC circuit.

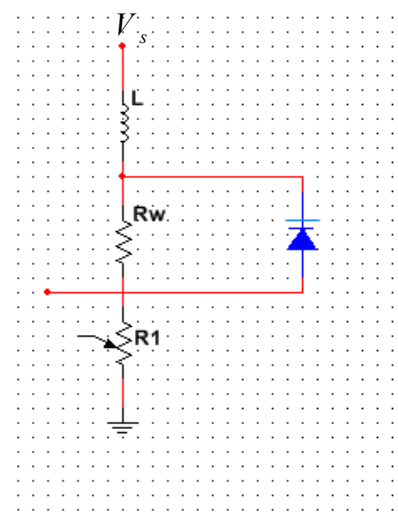



$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

If the amount of varactor reverse bias is decreased. The value of C of the varactor increases. The increases in C will cause the resonant frequency of the circuit to decrease and vice-versa.

Light Emitting Diode (LED)

A light emitting diode is a diode that gives off visible light when forward biased.


LED is forward biased, the electrons from the n-type material cross the pn junction and recombine with holes in the p-type material. Recall that these electrons are in the conduction band and at a higher energy level than the holes in the valence band. When recombination takes place, the recombining electrons, release energy in the form of heat and light. In germanium and silicon diodes, almost the entire energy is given up in the form of heat and emitted light is insignificant. However in materials like gallium arsenide, the number of photons of light energy is sufficient to produce quite intense visible light.

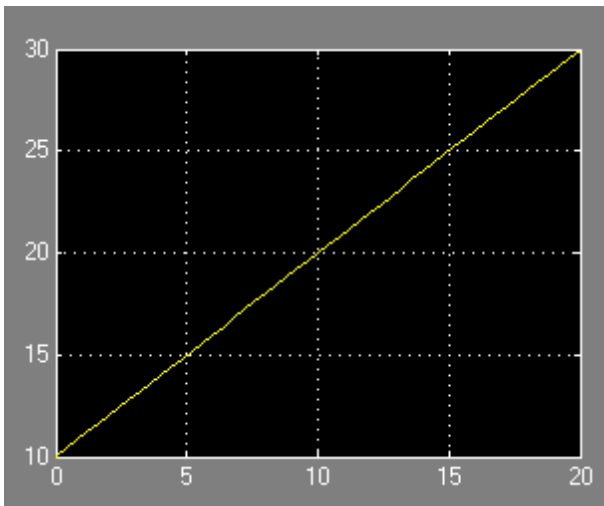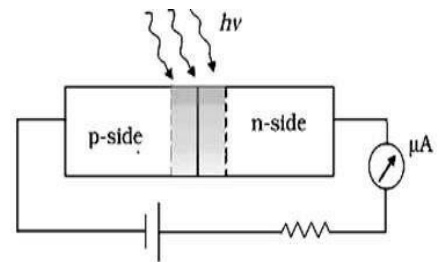

LED voltage and current:

$$V = I R_s + V_S - V_D$$

$$I_F = \frac{V_S - V_D}{R_s}$$

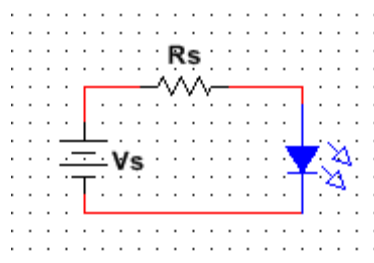


Advantages of LED:

The light emitting diode(LED) is a solid-state light source

- 1- low voltage
- 2- longer life(more than 20 years)
- 3- fast ON-OFF switching



protecting LED against reverse bias:

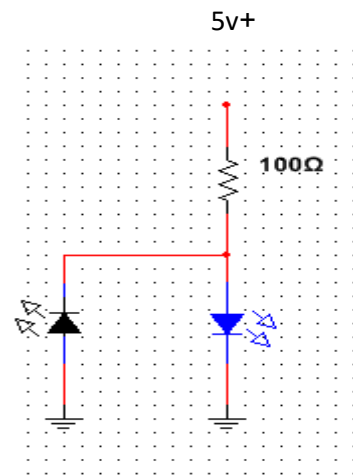one way to protect a LED is to connect a rectifier diode in parallel with LED as shown. If reverse voltage greater than the reverse voltage rating of LED is accidentally applied. The rectifier diode will be turned on. This protects the LED from damage.



Multicolor LEDs:


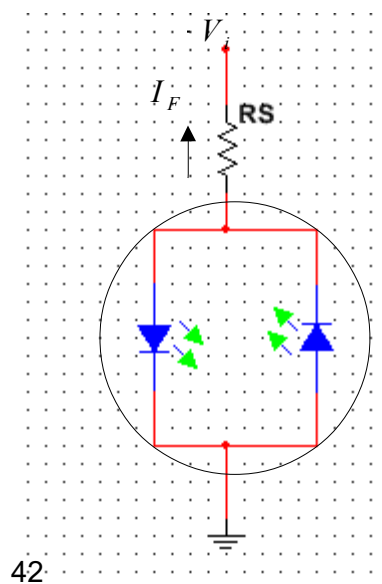
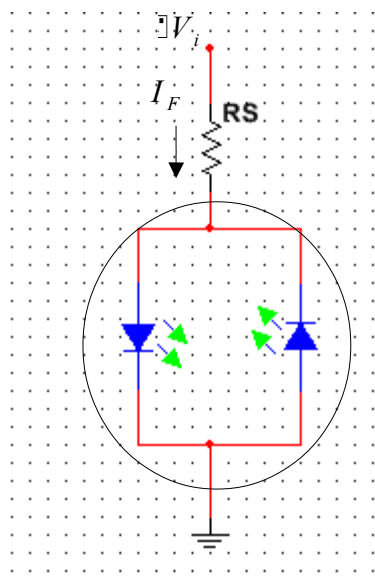
A LED that emits one color when forward biased and another color when reverse biased is called a Multicolor LED.





Multicolor LEDs are typically red when biased in one direction and green when biased in the other. If a multicolor LED is switched fast enough between two polarities, the LED will produce a third color. A red\ green will produce yellow.

Applications of LEDs:

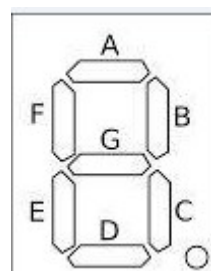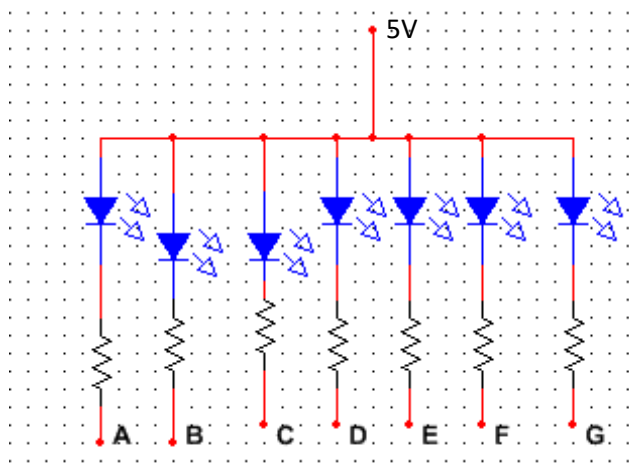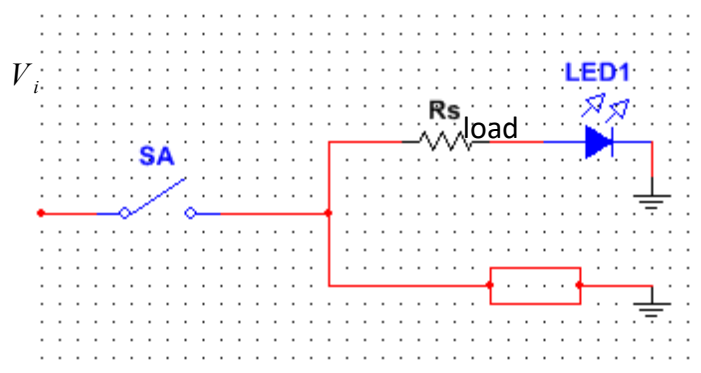- 1- As a power indicator
- 2- Seven-segment display




AND-OR GATS:

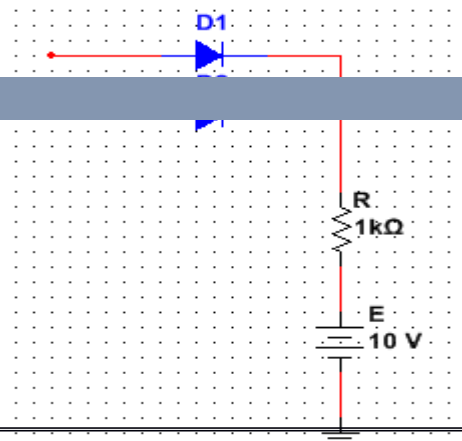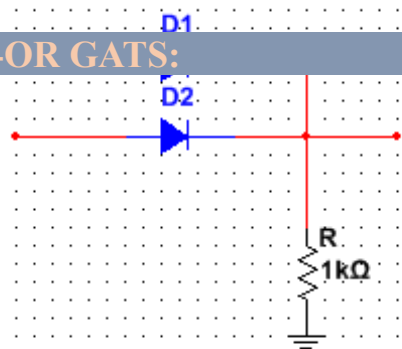


Shockley diode:

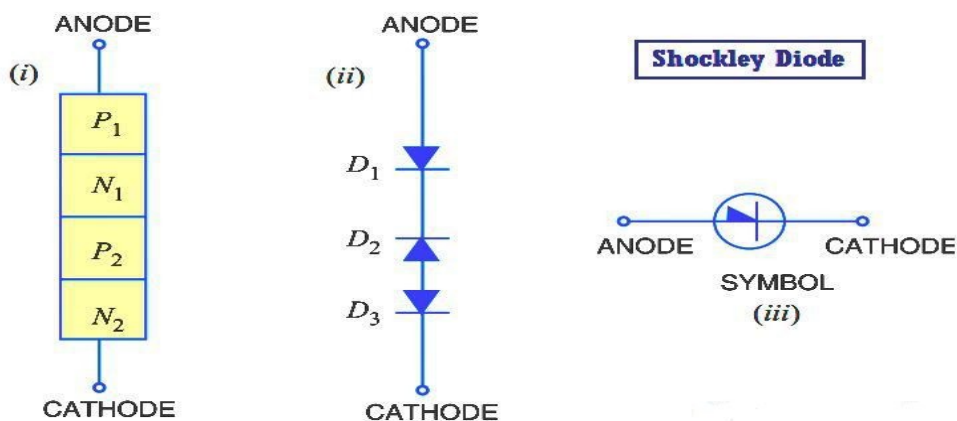Shockley diode is a PNPN device having two terminals as shown in Fig.



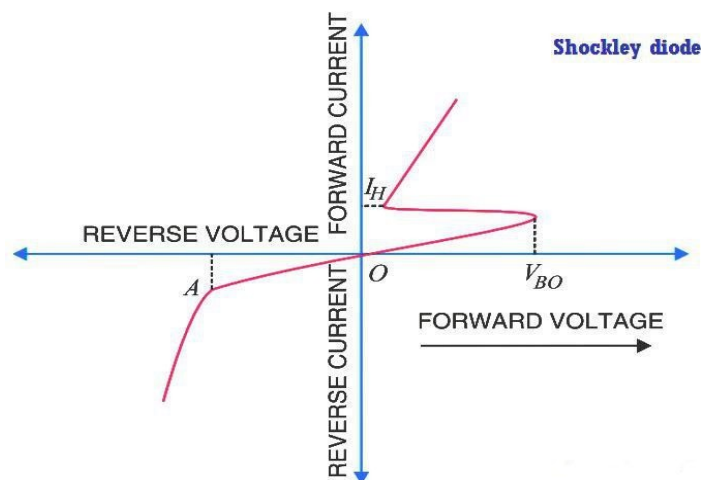
This device acts as a switch and consists of four alternate p-type and n-type layers in single crystal.



Forward $D_1 \parallel D_3$ but D_2 reverse biased to $V \approx V_{B0}$ then D_2 in reverse breakdown. From now onwards. The shockly diode behaves as a conventional forward biased diode. At reverse $D_1 \parallel D_3$ in reverse & D_2 forward to point A breakdown $D_1 \parallel D_3$.

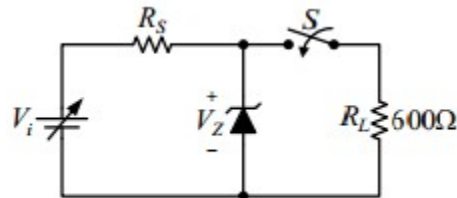Example 7-3:

The reverse current in a certain 12 V, 2.4 W zener diode must be at least 5 mA to ensure that the diode remains in breakdown. The diode is to be used in the regulator circuit shown in Fig. 7-9, where V_i can vary from 18 V to 24 V. Find a suitable value for R_s and the minimum rated power dissipation that R_s should have.



Solution:

$$I_{ZK} = 5 \text{ mA}, I_{ZM} = \frac{P_Z}{V_Z} = \frac{2.4}{12} = 200 \text{ mA}.$$

min \oplus
 \oplus
 $L \oplus$
 $I \oplus$

max \oplus
 \oplus
 $L \oplus$
 $I \oplus$

min \oplus
 \oplus
 $s \oplus$
 $I_{ZK} = I \oplus$

max \oplus
 \oplus
 $s \oplus$
 $I_{ZM} = I \oplus$

$$\begin{aligned}
 & \min \oplus \\
 & \oplus \\
 & -V_Z \\
 & \oplus \\
 & \min \oplus \\
 & \oplus \\
 & s \oplus \\
 & i \oplus \\
 & V \oplus \\
 & R_{s \max} \oplus \oplus
 \end{aligned}$$

$$\begin{aligned}
 & \max \oplus \\
 & \oplus \\
 & -V_Z \\
 & \oplus \\
 & \max \oplus \\
 & \oplus \\
 & s \oplus \\
 & i \oplus \\
 & V \oplus \\
 & R_{s \min} \oplus \oplus
 \end{aligned}$$

Thus, we require $60 \Omega \leq R_s \leq 240 \Omega$.

Choosing or calculating


$$\begin{aligned}
 & \max \oplus \\
 & \oplus \\
 & s \oplus \\
 & R_{s \min} \cdot R \\
 & R_s \sqrt{\quad} \oplus
 \end{aligned}$$

$$\begin{aligned}
 & \max \oplus \\
 & \oplus \\
 & -V_Z \\
 & i \oplus \\
 & V \oplus \\
 & I_{s \max} \oplus \oplus
 \end{aligned}$$


$$P_{R_s} \geq I_{s \max}^2 \cdot R_s \geq 100 \cdot 10^{-3} \cdot 120 \geq 1.2 \text{ W} .$$

Exercises:


1-Sketch the output (v_o) for the circuit of Fig. 7-10 for the input shown (v_i) when $|V_m|$ equal to (i) 5 V, and (ii) 15 V.

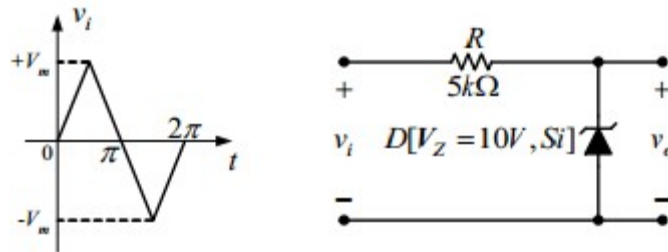

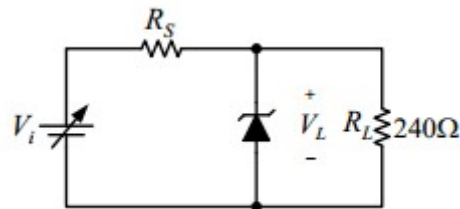2-Design the voltage regulator circuit of Fig. 7-11 to maintain V_L at 12 V across R_L with V_i that will vary between 16 and 20 V. That is, determine the proper value of R_S and the power rating of the zener diode (P_Z).



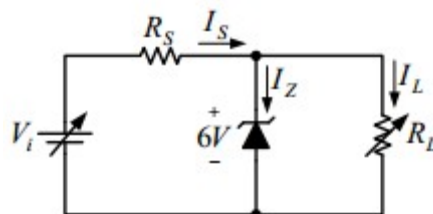3-The 6-V zener diode in Fig. 7-12 has a maximum rated power dissipated of 690 mW. Its reverse current must be at least 3 mA to keep it in breakdown. Find a suitable value for R_S if V_i can vary from 9 V to 12 V and R_L can vary from 500 Ω to 1.2 kΩ.



4-If R_S in Exercise 3 is set equal to its maximum permissible value, what is the maximum permissible value of V_i ?

5-If R_S in Exercise 3 is set equal to its minimum permissible value, what is the minimum permissible value of R_L ?

6-If R_S in Exercise 3 is set equal to 120 Ω, what is the minimum rated power dissipated that R_S should have?

